

# CONTENTS

	PAGE
CHAPTER 1	
MEET THE ELECTRON . . . . .	1
CHAPTER 2	
ELECTRON ESCAPE FROM SOLIDS — EMISSION . . . . .	12
Thermal emission . . . . .	13
Photoemission . . . . .	15
Secondary Emission . . . . .	17
High-Field Emission . . . . .	18
CHAPTER 3	
ELECTRICITY FROM LIGHT . . . . .	21
Photoemissivity . . . . .	21
Photovoltaic Devices . . . . .	26
The Multiplier Phototube . . . . .	30
CHAPTER 4	
ELECTRICITY INTO LIGHT . . . . .	33
The Cathode-Ray Oscilloscope . . . . .	40
The Electron Microscope . . . . .	48
Electronic Lamps . . . . .	53
CHAPTER 5	
TWO-ELEMENT TUBES . . . . .	60
Classification of Two-Element Tubes . . . . .	60
Kenotrons . . . . .	62
Properties of a Gas Discharge . . . . .	68
Introduction of Gas in Thermionic Tubes . . . . .	73
Phanotrons . . . . .	76
Gas Pressure and Operating Temperature . . . . .	79
CHAPTER 6	
THREE-ELEMENT PLIOTRONS . . . . .	83
The Function of the Triode . . . . .	83
Grid Control of Space Charge . . . . .	83
Triode Characteristics . . . . .	88
CHAPTER 7	
MULTIGRID PLIOTRONS . . . . .	99
Tetrodes . . . . .	99
Interelectrode Capacitance . . . . .	103

	PAGE
Pentodes . . . . .	104
Beam Power Tubes . . . . .	106
Variable-Mu Tubes . . . . .	110
Multielement Tubes . . . . .	112
CHAPTER 8	
THYRATRONS . . . . .	116
Cathodes . . . . .	118
Anodes . . . . .	118
Grids . . . . .	118
Control Characteristics . . . . .	123
Shield-Grid Thyratrons . . . . .	125
CHAPTER 9	
FROM ALTERNATING TO DIRECT CURRENT. . . . .	131
Single-Phase Rectifier Circuits . . . . .	132
Three-Phase Rectifier Circuits . . . . .	141
Multiphase Rectifier Circuits . . . . .	149
Voltage Doubler . . . . .	150
Filters . . . . .	154
Table of Rectifier Circuit Characteristics . . . . .	164
CHAPTER 10	
MERCURY-POOL TUBES . . . . .	168
Mercury-Arc Rectifiers . . . . .	169
Ignitrons . . . . .	171
Excitrons . . . . .	187
CHAPTER 11	
AMPLIFICATION . . . . .	195
Principles of Amplification . . . . .	195
Amplifier Operation . . . . .	197
Untuned Multistage Amplifiers . . . . .	209
Representation of Amplifier Characteristics . . . . .	210
Manner of Coupling Amplifiers . . . . .	213
Push-Pull Amplifiers . . . . .	220
Tuned Amplifiers . . . . .	223
Tuned Voltage Amplifiers . . . . .	223
Tuned Power Amplifiers . . . . .	225
CHAPTER 12	
PRINCIPLES OF OSCILLATION . . . . .	231
A-C Circuits Containing Resistance, Inductance, and Capacitance . . . . .	232
Oscillator Principles . . . . .	237
Oscillator Circuits . . . . .	245
Oscillator Operation . . . . .	248
Frequency Stability with Crystal-Controlled Oscillators. . . . .	252
Dynatron Oscillator . . . . .	255
Beat-Frequency Oscillators . . . . .	256

## CHAPTER 13

MODULATION AND DETECTION OF CARRIER WAVES . . . . .	262
Producing Amplitude-Modulated Carrier Waves . . . . .	265
Demodulation or Detection of Amplitude-Modulated Waves . . . . .	269
Producing Frequency-Modulated Carrier Waves . . . . .	272
Demodulation of Frequency-Modulated Carrier Waves . . . . .	274
Suppressing the Carrier Wave — Single-Sideband Transmission . . . . .	277
Industrial Applications of Carrier . . . . .	280

## CHAPTER 14

HEATING BY HIGH FREQUENCY . . . . .	288
Induction Heating . . . . .	291
Radio-Frequency Generators and Applications . . . . .	291
Calculations for Induction Heating . . . . .	296
Where Induced Currents Flow . . . . .	296
Calculation of Equipment Necessary for Induction Heating . . . . .	299
Heating by Proximity — Flat Nonmagnetic Plate . . . . .	306
Typical Examples of Induction Heating . . . . .	322
Dielectric Heating . . . . .	339
Computing the Radio-Frequency Generator Requirements . . . . .	342
Voltage Limitations . . . . .	342
Frequency Limitations . . . . .	343
Impedance Matching . . . . .	343

## CHAPTER 15

BASIC CIRCUITS OF ELECTRONIC CONTROL . . . . .	355
D-C Supply for Anode and Grid Potentials . . . . .	355
Pliotrons — for Proportional Control of Direct Current . . . . .	359
Thyratrons — for Instantaneous Control of Direct Current . . . . .	359
Thyratrons — for Proportional Control of Alternating Current . . . . .	362
Circuits for Shifting the Phase of the Grid Voltage . . . . .	366
Peaking Transformer . . . . .	369
Thyratron Control by Peaking Transformer . . . . .	371
Inverse-Parallel Connection of Thyatrons for Control of Alternating Current . . . . .	372
Circuits for Electronic Timing . . . . .	375
Circuits for Regulating Current and Voltage . . . . .	376
Thyratron Inverters from Direct to Alternating Current . . . . .	379
Thyratron-Circuit Details . . . . .	380

## CHAPTER 16

INDUSTRIAL APPLICATION OF ELECTRONIC CONTROL . . . . .	388
Electronic Timing . . . . .	388
Photoelectric Relays . . . . .	392
Resistance-Welding Controls . . . . .	402
Electronic Motor Control . . . . .	430

	PAGE
CHAPTER 17	
ELECTRONIC REGULATORS . . . . .	443
Static Regulators . . . . .	445
Astatic Regulators . . . . .	453
Astatic Voltage Regulators . . . . .	464
Antihunting Circuits . . . . .	469
APPENDIX . . . . .	489
INDEX . . . . .	495