

Contents

CHAPTER 1

Electric Circuit Variables	1
1.1 Introduction	1
1.2 Electric Circuits and Current	1
1.3 Systems of Units	5
1.4 Voltage	7
1.5 Power and Energy	7
1.6 Circuit Analysis and Design	11
1.7 How Can We Check ... ?	13
1.8 Design Example—Jet Valve Controller	14
1.9 Summary	15
Problems	15
Design Problems	19

CHAPTER 2

Circuit Elements	20
2.1 Introduction	20
2.2 Engineering and Linear Models	20
2.3 Active and Passive Circuit Elements	23
2.4 Resistors	25
2.5 Independent Sources	28
2.6 Voltmeters and Ammeters	30
2.7 Dependent Sources	33
2.8 Resistive Transducers	37
2.9 Switches	41
2.10 How Can We Check ... ?	43
2.11 Design Example—Temperature Sensor	44
2.12 Summary	46
Problems	47
Design Problems	55

CHAPTER 3

Resistive Circuits	56
3.1 Introduction	56
3.2 Kirchhoff's Laws	57
3.3 Series Resistors and Voltage Division	66

3.4	Parallel Resistors and Current Division	71
3.5	Series Voltage Sources and Parallel Current Sources	77
3.6	Circuit Analysis	81
3.7	Analyzing Resistive Circuits Using MATLAB	86
3.8	How Can We Check ... ?	89
3.9	Design Example—Adjustable Voltage Source	91
3.10	Summary	94
	Problems	95
	Design Problems	112

CHAPTER 4

	Methods of Analysis of Resistive Circuits	116
4.1	Introduction	116
4.2	Node Voltage Analysis of Circuits with Current Sources	117
4.3	Node Voltage Analysis of Circuits with Current and Voltage Sources	123
4.4	Node Voltage Analysis with Dependent Sources	128
4.5	Mesh Current Analysis with Independent Voltage Sources	130
4.6	Mesh Current Analysis with Current and Voltage Sources	135
4.7	Mesh Current Analysis with Dependent Sources	139
4.8	The Node Voltage Method and Mesh Current Method Compared	141
4.9	Circuit Analysis Using MATLAB	144
4.10	Using PSpice to Determine Node Voltages and Mesh Currents	146
4.11	How Can We Check ... ?	148
4.12	Design Example—Potentiometer Angle Display	151
4.13	Summary	154
	Problems	155
	PSpice Problems	167
	Design Problems	167

CHAPTER 5

	Circuit Theorems	169
5.1	Introduction	169
5.2	Source Transformations	169
5.3	Superposition	176
5.4	Thévenin's Theorem	180
5.5	Norton's Equivalent Circuit	187
5.6	Maximum Power Transfer	191
5.7	Using MATLAB to Determine the Thévenin Equivalent Circuit	194
5.8	Using PSpice to Determine the Thévenin Equivalent Circuit	197

5.9	How Can We Check . . . ?	200
5.10	Design Example—Strain Gauge Bridge	201
5.11	Summary	203
	Problems	204
	PSpice Problems	214
	Design Problems	215

CHAPTER 6

The Operational Amplifier		219
6.1	Introduction	219
6.2	The Operational Amplifier	219
6.3	The Ideal Operational Amplifier	221
6.4	Nodal Analysis of Circuits Containing Ideal Operational Amplifiers	223
6.5	Design Using Operational Amplifiers	228
6.6	Operational Amplifier Circuits and Linear Algebraic Equations	233
6.7	Characteristics of Practical Operational Amplifiers	238
6.8	Analysis of Op Amp Circuits Using MATLAB	245
6.9	Using PSpice to Analyze Op Amp Circuits	247
6.10	How Can We Check . . . ?	248
6.11	Design Example—Transducer Interface Circuit	250
6.12	Summary	252
	Problems	252
	PSpice Problems	263
	Design Problems	264

CHAPTER 7

Energy Storage Elements		265
7.1	Introduction	265
7.2	Capacitors	266
7.3	Energy Storage in a Capacitor	273
7.4	Series and Parallel Capacitors	276
7.5	Inductors	278
7.6	Energy Storage in an Inductor	283
7.7	Series and Parallel Inductors	285
7.8	Initial Conditions of Switched Circuits	286
7.9	Operational Amplifier Circuits and Linear Differential Equations	290
7.10	Using MATLAB to Plot Capacitor or Inductor Voltage and Current	296
7.11	How Can We Check . . . ?	298
7.12	Design Example—Integrator for Battery Charge Estimation	299

7.13	Summary	302
	Problems	303
	Design Problems	315

CHAPTER 8

The Complete Response of *RL* and *RC* Circuits..... 317

8.1	Introduction	317
8.2	First-Order Circuits	317
8.3	The Response of a First-Order Circuit to a Constant Input	320
8.4	Sequential Switching	333
8.5	Stability of First-Order Circuits	335
8.6	The Unit Step Source	337
8.7	The Response of a First-Order Circuit to a Nonconstant Source.....	341
8.8	Differential Operators	346
8.9	Using PSpice to Analyze First-Order Circuits	347
8.10	How Can We Check ... ?.....	350
8.11	Design Example—A Computer and Printer	354
8.12	Summary	356
	Problems	358
	PSpice Problems	368
	Design Problems.....	369

CHAPTER 9

The Complete Response of Circuits with Two Energy Storage Elements 370

9.1	Introduction	370
9.2	Differential Equation for Circuits with Two Energy Storage Elements	371
9.3	Solution of the Second-Order Differential Equation—The Natural Response	375
9.4	Natural Response of the Unforced Parallel <i>RLC</i> Circuit.....	377
9.5	Natural Response of the Critically Damped Unforced Parallel <i>RLC</i> Circuit	380
9.6	Natural Response of an Underdamped Unforced Parallel <i>RLC</i> Circuit	381
9.7	Forced Response of an <i>RLC</i> Circuit	384
9.8	Complete Response of an <i>RLC</i> Circuit	387
9.9	State Variable Approach to Circuit Analysis.....	390
9.10	Roots in the Complex Plane	395
9.11	How Can We Check ... ?.....	396
9.12	Design Example—Auto Airbag Igniter	398
9.13	Summary	400
	Problems	402
	PSpice Problems	411

CHAPTER 10

Sinusoidal Steady-State Analysis	414
10.1 Introduction	414
10.2 Sinusoidal Sources	415
10.3 Phasors and Sinusoids	419
10.4 Impedances	424
10.5 Series and Parallel Impedances	430
10.6 Mesh and Node Equations	436
10.7 Thévenin and Norton Equivalent Circuits	444
10.8 Superposition	448
10.9 Phasor Diagrams	451
10.10 Op Amps in AC Circuits	452
10.11 The Complete Response	454
10.12 Using MATLAB to Analyze AC Circuits	461
10.13 Using PSpice to Analyze AC Circuits	463
10.14 How Can We Check . . . ?	465
10.15 Design Example—An Op Amp Circuit	468
10.16 Summary	470
Problems	471
PSpice Problems	486
Design Problems	488

CHAPTER 11

AC Steady-State Power	489
11.1 Introduction	489
11.2 Electric Power	489
11.3 Instantaneous Power and Average Power	490
11.4 Effective Value of a Periodic Waveform	494
11.5 Complex Power	497
11.6 Power Factor	504
11.7 The Power Superposition Principle	512
11.8 The Maximum Power Transfer Theorem	515
11.9 Coupled Inductors	516
11.10 The Ideal Transformer	524
11.11 How Can We Check . . . ?	531
11.12 Design Example—Maximum Power Transfer	532
11.13 Summary	534
Problems	536
PSpice Problems	549
Design Problems	550

CHAPTER 12

Three-Phase Circuits	551
12.1 Introduction	551
12.2 Three-Phase Voltages	552
12.3 The Y-to-Y Circuit	555
12.4 The Δ -Connected Source and Load	564
12.5 The Y-to- Δ Circuit	566
12.6 Balanced Three-Phase Circuits	568
12.7 Instantaneous and Average Power in a Balanced Three-Phase Load	571
12.8 Two-Wattmeter Power Measurement	574
12.9 How Can We Check ... ?	577
12.10 Design Example—Power Factor Correction	580
12.11 Summary	582
Problems	582
PSpice Problems	587
Design Problems	587

CHAPTER 13

Frequency Response	588
13.1 Introduction	588
13.2 Gain, Phase Shift, and the Network Function	588
13.3 Bode Plots	600
13.4 Resonant Circuits	617
13.5 Frequency Response of Op Amp Circuits	624
13.6 Plotting Bode Plots Using MATLAB	626
13.7 Using PSpice to Plot a Frequency Response	628
13.8 How Can We Check ... ?	630
13.9 Design Example—Radio Tuner	634
13.10 Summary	636
Problems	637
PSpice Problems	648
Design Problems	651

CHAPTER 14

The Laplace Transform	653
14.1 Introduction	653
14.2 Laplace Transform	654
14.3 Pulse Inputs	660
14.4 Inverse Laplace Transform	663
14.5 Initial and Final Value Theorems	670

14.6	Solution of Differential Equations Describing a Circuit.....	672
14.7	Circuit Analysis Using Impedance and Initial Conditions.....	674
14.8	Transfer Function and Impedance.....	684
14.9	Convolution.....	690
14.10	Stability.....	694
14.11	Partial Fraction Expansion Using MATLAB.....	697
14.12	How Can We Check ... ?.....	702
14.13	Design Example—Space Shuttle Cargo Door.....	704
14.14	Summary.....	707
	Problems.....	708
	PSpice Problems.....	720
	Design Problems.....	721

CHAPTER 15

Fourier Series and Fourier Transform..... 723

15.1	Introduction.....	723
15.2	The Fourier Series.....	724
15.3	Symmetry of the Function $f(t)$	732
15.4	Fourier Series of Selected Waveforms.....	737
15.5	Exponential Form of the Fourier Series.....	739
15.6	The Fourier Spectrum.....	747
15.7	Circuits and Fourier Series.....	751
15.8	Using PSpice to Determine the Fourier Series.....	754
15.9	The Fourier Transform.....	759
15.10	Fourier Transform Properties.....	762
15.11	The Spectrum of Signals.....	766
15.12	Convolution and Circuit Response.....	767
15.13	The Fourier Transform and the Laplace Transform.....	770
15.14	How Can We Check ... ?.....	772
15.15	Design Example—DC Power Supply.....	774
15.16	Summary.....	777
	Problems.....	778
	PSpice Problems.....	784
	Design Problems.....	784

CHAPTER 16

Filter Circuits..... 785

16.1	Introduction.....	785
16.2	The Electric Filter.....	785
16.3	Filters.....	786

16.4	Second-Order Filters	789
16.5	High-Order Filters	797
16.6	Simulating Filter Circuits Using PSpice	803
16.7	How Can We Check . . . ?	807
16.8	Design Example—Anti-Aliasing Filter	809
16.9	Summary	812
	Problems	812
	PSpice Problems	817
	Design Problems	820

CHAPTER 17

Two-Port and Three-Port Networks		821
17.1	Introduction	821
17.2	T-to- Π Transformation and Two-Port Three-Terminal Networks	822
17.3	Equations of Two-Port Networks	824
17.4	Z and Y Parameters for a Circuit with Dependent Sources	827
17.5	Hybrid and Transmission Parameters	829
17.6	Relationships Between Two-Port Parameters	831
17.7	Interconnection of Two-Port Networks	833
17.8	How Can We Check . . . ?	836
17.9	Design Example—Transistor Amplifier	837
17.10	Summary	839
	Problems	840
	Design Problems	843

APPENDIX A

Getting Started with PSpice	845
------------------------------------	------------

APPENDIX B

MATLAB, Matrices, and Complex Arithmetic	853
---	------------

APPENDIX C

Mathematical Formulas	865
------------------------------	------------

APPENDIX D

Resistor Specifications and Monte Carlo Analysis	869
---	------------

References	873
-------------------	------------

Index	875
--------------	------------