

Contents

SECTION I *Problems and Solutions*

1 *Circuit Components*

1.01	Resistance of a Line	3
1.02	Length of a Desired Resistance	3
1.03	Constantan Shunt	3
1.04	Nichrome Shunt	4
1.05	Calculating the Wire Gauge	4
1.06	Temperature Considerations	5
1.07	High-Frequency Resistance	6
1.08	Comparing High-Frequency and Direct-Current Resistance	6
1.09	Capacitor Across Alternating-Current Line	7
1.10	Capacitors in Parallel	7
1.11	Combining Variable Capacitors	7
1.12	Power Factor of Mica Capacitor	8
1.13	Shunt Resistance	8
1.14	Paper Capacitor	9
1.15	Capacitors in Parallel	9
1.16	Three Capacitors in Series	10
1.17	Voltage Rating of Capacitors	10
1.18	Charge of a Capacitor	10
1.19	Ten-Plate Capacitor	11
1.20	Removing Plates	11
1.21	Combined Inductors	12
1.22	Coupling Coefficient	12
1.23	Unity Coupling Coefficient	13
1.24	Single-Layer Coil	13

1.25	Three-Layer Coil	14
1.26	Diameter of a Coil	14
1.27	Impedance-Matching Transformer	15
1.28	Shunt Compensation	15
1.29	Effect of Coil Shape	16
1.30	Doubling the Number of Turns	16
1.31	Transformer Efficiency	16
1.32	Three-Phase Transformer	17
1.33	Step-Down Transformer	17
1.34	Increasing the Voltage Rating	18
1.35	Primary Current	18
1.36	Transformer Design	19
1.37	Primary Impedance	20
1.38	Loud-Speaker Transformer	20
1.39	Voltage Regulation of a Transformer	21

2 *Direct-Current Circuits*

2.01	Filament Resistance	22
2.02	Current of Commercial Light Bulb	22
2.03	Voltage Drop across Line-Cord Resistor	22
2.04	Resistance of Light Bulb	23
2.05	Filament Rheostat	23
2.06	Heater Element	24
2.07	Voltmeter Hookup	24
2.08	Bleeder Resistor	24
2.09	Grid Bias	25
2.10	Resistors in Parallel	25
2.11	Series Circuit	26

2.12	Panel Lamp	27	3.14	Phase Difference	54
2.13	Substituting Odd Resistors	27	3.15	Resistance and Capacitance in Parallel	55
2.14	Bias Resistor	28	3.16	Capacitance and Induc- tance in Parallel	56
2.15	Voltage Divider	28	3.17	Resistance and Inductance in Parallel	57
2.16	Voltage Divider with Load Drain	29	3.18	Resistance, Capacitance, and Inductance in Parallel	58
2.17	Bleeder Design	30	3.19	Methods of Solving Paral- lel Circuits	59
2.18	Bleeder Voltage under No- Load	31	3.20	Resistance in Both Branches	63
2.19	Series-Parallel Circuit	32	3.21	Series-Parallel Network	65
2.20	Series-Parallel Circuit	35	3.22	Resonant Frequency	67
2.21	Batteries in Parallel	36	3.23	Voltage at Resonance	68
2.22	Unbalanced Bridge—Solu- tion by Kirchhoff's Law	39	3.24	Resonant Capacitance	68
2.23	Delta-Star Transformation	41	3.25	Effective Resistance	69
2.24	Thévenin's Theorem	43	3.26	Parallel Resonance	69
2.25	Thévenin's Theorem Ap- plied to Bridge Network	44	3.27	Q of Tank Circuit	71
2.26	Thévenin's Theorem for Network Containing Two Sources of Electromotive Force	46	3.28	Series Radio-Frequency Resistance	72
3	<i>Alternating Current Circuits</i>		3.29	Tank Capacitor	72
3.01	Wavelength	47	3.30	Loaded Tank Circuit	73
3.02	Frequency	47	3.31	Inductance and Capaci- tance of Loaded Tank	74
3.03	Period	47	3.32	Audio-Frequency High- Pass Filter	74
3.04	Instantaneous Current	48	3.33	Radio-Frequency High- Pass Filter	75
3.05	Instantaneous Voltage	48	3.34	Low-Pass Filter	75
3.06	Pulsating Direct Current	48	3.35	Wave Filter	76
3.07	Alternating and Direct Currents Combined	48	3.36	Wave Rejector	77
3.08	Phase Considerations	49	3.37	Kirchhoff's Law for Alter- nating Currents	78
3.09	Motor Input Current	50	3.38	Impedance of Bridge Net- work	80
3.10	Resistance and Capaci- tance in Series	51	3.39	General Solution of the Delta-Star Transforma- tion	81
3.11	Resistance and Inductance in Series	51	3.40	Delta-Star Transformation for Alternating Currents	83
3.12	Resistance, Capacitance, and Inductance in Series	52			
3.13	j -Notation in a Series Cir- cuit	53			

CONTENTS

xi

3.41	Thévenin's Theorem for Alternating Currents	84	5.02	High-Frequency Response	105
3.42	<i>M</i> -Derived Filter	85	5.03	Low-Frequency Response	106
4	<i>Vacuum-Tube Fundamentals</i>		5.04	General Solution of the Medium-Frequency Response	108
4.01	Electron Emission	87	5.05	Medium-Frequency Response Using the Formula for Voltage Amplification at Medium Frequencies	109
4.02	Two-Electrode Tube Emission	88	5.06	General Solution of the High-Frequency Response	110
4.03	Triode Plate Current	88	5.07	High-Frequency Response Using the Formula for Voltage Amplification at High Frequencies	112
4.04	Amplification Factor	89	5.08	General Solution of the Low-Frequency Response	112
4.05	Plate Resistance	90	5.09	Low-Frequency Response Using the Formula for Voltage Amplification at Low Frequencies	115
4.06	Transconductance	90	5.10	Replacement of the Coupling Capacitor	116
4.07	Determining Tube Constants	91	5.11	Leaky Coupling Capacitor	117
4.08	Output Voltage	91	5.12	Grid-Leak Resistor	117
4.09	Voltage Amplification	92	5.13	Cathode Resistor and Capacitor	118
4.10	Increasing the Load Resistance	92	5.14	Line Amplifier	118
4.11	Load Line	93	5.15	Decibel Loss	119
4.12	No-signal Plate Voltage and Plate Current	94	5.16	Percentage of Modulation at Stated Decibel Input	119
4.13	Maximum and Minimum Plate Voltage	94	5.17	Input for Stated Gain	120
4.14	Plate Voltage	94	5.18	Triode Power Sensitivity	121
4.15	Grid Bias	94	5.19	Pentode Power Sensitivity	121
4.16	Conversion Calculations for Beam Power Tube	95	5.20	Transmitting Triode Power Sensitivity	122
4.17	Conversion Calculations for Triode	96	5.21	Class A. Graphical Determination of the Power Output	122
4.18	Triode Power Output	97	5.22	Graphical Determination of the Second-Harmonic Distortion	122
4.19	Pentode Power Output	97			
4.20	Maximum Power Output	98			
4.21	Undistorted Power Output	98			
4.22	Plate Efficiency	98			
4.23	Approximate Load Resistance	99			
4.24	Plate Efficiency	100			
4.25	Stage Amplification	101			
5	<i>Amplifiers</i>				
5.01	Medium-Frequency Response	103			

5.23	Response of Transformer-Coupled Amplifier	123	6	<i>Oscillators</i>	
5.24	Transformer Coupling. Low-Frequency Response	125	6.01	Hartley Oscillator	144
5.25	Transformer Coupling. High-Frequency Response	125	6.02	Colpitts Oscillator	144
5.26	Impedance Coupling	127	6.03	Tuned-Plate Oscillator	145
5.27	Decibel Gain	129	6.04	Frequency Tolerance	146
5.28	Power Gain	129	6.05	Armstrong Oscillator	146
5.29	Audio-Frequency and Radio-Frequency By-pass Capacitors	130	6.06	Crystal-Controlled Oscillator	147
5.30	Radio-Frequency Choke	130	6.07	Q of a Crystal	148
5.31	Pentode Bias Resistor	131	6.08	Frequency Stability of a Crystal	149
5.32	Push-Pull Bias Resistor	131	6.09	Temperature Coefficient	149
5.33	Screen Dropping Resistor	132	6.10	Effect of Temperature on Frequency Multipliers	150
5.34	Plate Efficiencies of Classes A, B, and C Amplifiers	132	6.11	Capacitance Coupling of Radio-Frequency Amplifier	150
5.35	Class A. Maximum Root-Mean-Square Signal Input	133	6.12	Grid and Plate Tank Circuit	151
5.36	Class AB ₂ . Coupling of the Driver Tube	133	6.13	Oscillator Tank Circuit Design	152
5.37	Phase Inverter	134	7	<i>Transmitters</i>	
5.38	Class B. Tube Selection	136	7.01	Continuous-Wave Telegraphy. Grid Keying	154
5.39	Class B. Grid Bias	136	7.02	Grid Keying with Click Filter	155
5.40	Class C. Grid Bias	137	7.03	Current Increase through Modulation	155
5.41	Class C. Total Space Current	138	7.04	Current During Modulation	157
5.42	Class C. Grid Driving Power	138	7.05	Power for Modulation	157
5.43	Class C. Root-Mean-Square Signal Output	139	7.06	Comparing Different Degrees of Modulation	158
5.44	Class C. Active Part of the Cycle	139	7.07	Bandwidth During Modulation	158
5.45	Class C. Operating Bias	140	7.08	Ratio of Peak Currents	159
5.46	Class C. Grid Impedance	140	7.09	Ratio of Peak Powers	159
5.47	Class C. Tank Circuit Design	141	7.10	Sideband Power	160
5.48	Matching Class A to Class C	142	7.11	Power Reduction in Sidebands	160

CONTENTS

xiii

7.12	Peak Voltage During Modulation	160	8.05	Image Frequency	176
7.13	Modulator Input	161	8.06	Interference	176
7.14	Modulation Reading from Ammeter	162	8.07	Mixer-Oscillator Frequency	177
7.15	Channel Widths	162	8.08	Intermediate Frequency	177
7.16	Resistance of Cooling System	162	8.09	Oscillator Coil and Capacitor	177
7.17	Transmitter Power Loss	163	8.10	Detector Efficiency	178
7.18	Interference Caused by Modulation	164	8.11	Power Consumed by Detector	179
7.19	Modulation Power for Stated Tube	164	8.12	Loading Effect	179
7.20	Modulation Impedance	164	8.13	Television Detector Efficiency	180
7.21	Impedance Matching	165	8.14	Diode Versus Plate Detection	180
7.22	Oscillator Frequency Tolerance	166	8.15	Volume Control	181
7.23	Grid Modulation. Carrier Power	166	8.16	Automatic Volume Control	182
7.24	Grid Modulation Versus Plate Modulation	167	8.17	Tuning Eye	183
7.25	Frequency Modulation. Deviation from Carrier	167	8.18	Negative Feedback	183
7.26	Frequency-Modulation Index	167	8.19	Reduction of Distortion	184
7.27	Phase Splitting in Reactance-Tube Circuit	168	8.20	Frequency Distortion	184
7.28	Frequency Division	169	8.21	Negative Feedback for Transformer Coupling	186
7.29	Audio Frequency in Frequency Modulation	169	8.22	Negative Feedback for Resistance Coupling	186
7.30	Channel Width for High-Fidelity Music	170	8.23	Negative Feedback for Push-Pull Circuit	188
7.31	Frequency Modulation in the Broadcast Band	170	8.24	Infinite Attenuation	189
			8.25	Tone Control. Bass Attenuation	189
			8.26	Tone Control. Treble Attenuation	190
			8.27	Loudspeaker Power	191
			8.28	Output Transformer Efficiency	192
			8.29	Miller Effect	192
8	<i>Receivers</i>		9	<i>Power Supplies</i>	
8.01	Bandsread Capacitors	172	9.01	Half-Wave Rectifier. Capacitor Input	194
8.02	Band Spreading with Permeability Tuning	174	9.02	Per Cent Ripple of Half-Wave Rectifier	195
8.03	Possible Frequency Combinations	175			
8.04	Tracking Range	175			

9.03	Full-Wave Rectifier. Capacitor Input	196	9.29	Substitution of a 14C5 Tube for a 25L6 Tube	224
9.04	Per Cent Ripple. Full-Wave Rectifier	197	9.30	Substituting 6-Volt Tubes for 12-Volt Tubes	225
9.05	Full-Wave Rectifier. Fourier Analysis	198	9.31	Using a Selenium Rectifier for Substitution	226
9.06	Choke Input. Ripple Calculations	199	10	<i>Antennas and Transmission Lines</i>	
9.07	Filter Formulas	202	10.01	Hertz Antenna in Inches	227
9.08	Critical Inductance	203	10.02	"End Effect" in Antennas	227
9.09	Regulation by Bleeder	203	10.03	Resonant Frequency	228
9.10	Improving the Voltage Regulation by Bleeder	204	10.04	Height in Wavelengths	228
9.11	Swinging Choke	206	10.05	Height in Feet	229
9.12	Filter Design for Stated Per Cent Ripple	207	10.06	Antenna Current for Reduced Power	229
9.13	Equivalent Load Resistance	208	10.07	Antenna Current for Stated Power	229
9.14	Resistance-Capacitance Decoupling Filter	209	10.08	Effect of Current Increase	230
9.15	Mercury-Vapor Rectifier	211	10.09	Antenna power	230
9.16	Plate-to-Plate Voltage	211	10.10	Two-Wire Transmission Line	231
9.17	Voltage Divider Design	212	10.11	Concentric Line	231
9.18	Vibrator Power Supply	214	10.12	Power to Transmission Line	232
9.19	Vibrator Time Efficiency	215	10.13	Transmission Line Current	232
9.20	Glow-Discharge Tube. Voltage Regulation	215	10.14	Concentric Transmission Line Peak Voltage	233
9.21	Filament Supply for a-c/d-c Superheterodyne	216	10.15	Loss in Long Transmission Line	232
9.22	A-Supply for Tuned-Radio-Frequency Receiver with Pilot	217	10.16	Attenuation in Decibels	234
9.23	Sound-Track Power Supply	218	10.17	Efficiency of Transmission	235
9.24	Repair of "Burnt-Out" 35Z5	220	10.18	Attenuation of Coaxial Line	235
9.25	Open Pilot Lamp	220	10.19	Line Loss	236
9.26	Three-Way Portable	221	10.20	Length of Line	236
9.27	Burn-Out in Turned Off Receivers	222	10.21	Characteristic Impedance	236
9.28	A-Supply for Phonograph Amplifier	223	10.22	Determining Characteristic Impedance by Open-	

	ing and Short-Circuiting the Load End	237	11.22	Universal Time-Constant Chart	268
10.23	Field Strength of Non- Resonant Wire	238	11.23	Integrated Output	270
10.24	Pattern of Resonant Wire	240	11.24	Differentiated Output	273
10.25	Directional Array	244	11.25	Voltage Distribution Across Capacitors	274
10.26	Quarter-Wave Line Matching	249	11.26	Counter Circuit	276
11	<i>Television</i>		11.27	Counting Voltage after a Stated Number of Pulses	277
11.01	Speed of Scanning Beam	251	11.28	Counting Voltage after an Infinite Number of Pulses	278
11.02	Rate of Transmission of Picture Elements	251	11.29	Using the Counting-Volt- age Formula	279
11.03	Horizontal Scanning and Retrace	252	11.30	Incremental Voltage Caused by a Given Pulse	279
11.04	Vertical Scanning and Retrace	253	11.31	Maximum Number of Pulses	280
11.05	Number of Inactive Lines	254	11.32	Number of Pulses for Stated Voltage	281
11.06	Number of Picture Ele- ments per Frame	254	11.33	Filter-Time Constant of Video Power Supply	281
11.07	Television Broadcast Band	257	11.34	Focus and Centering	283
11.08	Television Horizon	257	11.35	Video Amplifier Plate- Load Resistor	284
11.09	Television Area	258	11.36	High-Frequency Compens- ation by Shunt Peaking	284
11.10	Distance between Relay Stations	258	11.37	High-Frequency Compens- ation by Series Peaking	289
11.11	Kinescope Electrostatic Deflection	259	11.38	Series-Shunt Compensa- tion	291
11.12	Magnetic Deflection	259	11.39	Low-Frequency Compens- ation	293
11.13	Illumination of Mosaic	260	11.40	Cathode Follower	295
11.14	Image-Orthicon Electron Multiplier	261	11.41	General Solution of the Cathode Follower	296
11.15	Orthicon Sensitivity	262	11.42	Cathode Follower Output Impedance	297
11.16	Object Size at Stated Dis- tance from Screen	262	11.43	Fourier Analysis of a Saw- Tooth Wave	298
11.17	Critical Viewing Distance for Picture Elements	264	11.44	Using the Sigma Notation of Fourier Series	299
11.18	Critical Viewing Distance for Scanning Lines	264			
11.19	Differentiating Circuit	265			
11.20	Integrating Circuit	266			
11.21	Two-Section Integrator	267			

11.45	Reflective Projection System	300	12.06	Calibrating an Ohmmeter	323
11.46	Countdowns for Stated Number of Lines	302	12.07	Measuring Resistance with a Voltmeter	324
11.47	Scoping the Pulse-Timing Unit	303	12.08	Measuring Inductance with Voltmeter and Ammeter	325
11.48	Measuring High-Frequency Television Pulses	304	12.09	Measuring Capacitance with the Slide-Wire Bridge	326
11.49	Measuring Low-Frequency Television Pulses	305	12.10	Capacitance-Resistance Bridge	327
11.50	Vertical "Burst"	306	12.11	Inductance of a Radio-Frequency Coil	329
11.51	Camera Viewing Angle	307	12.12	Wien Bridge	330
11.52	Gamma Response	308	12.13	Extending the Range of a Voltmeter	332
11.53	Gamma-Unity Response	309	12.14	Extending the Range of an Ammeter	332
11.54	Figure of Merit of a Triode Voltage Amplifier	310	12.15	Volt-Milliammeter	333
11.55	Figure of Merit of Pentode Voltage Amplifiers	310	12.16	Vacuum-Tube Voltmeter	334
11.56	Video Output Tubes	311	12.17	Measuring Voltages with a Milliammeter	335
11.57	Upper Frequency Limit of Amplifiers	312	12.18	Meter Shunt	336
11.58	Direct and Reflected Signals	313	12.19	Measuring Capacitance with a Voltmeter	337
11.59	Direct-Current Restoration	314	12.20	Measuring Inductance with a Voltmeter	337
11.60	Line-Pattern Testing of the Horizontal Oscillator	316	12.21	Measuring Resistance with a Vacuum-Tube Voltmeter	339
11.61	Line-Pattern Testing of the Vertical Oscillator	317	12.22	Q of a Radio-Frequency Coil	339
11.62	Television Receiver Intermediate and Oscillator Frequencies	317	13	<i>Industrial and Control Circuits</i>	
11.63	Installing a Television Antenna	318	13.01	Thyratron Frequency Limits	341
12	<i>Measurements</i>		13.02	Saw-Tooth Wave Applied to Thyratron	341
12.01	Wheatstone Bridge	319	13.03	Delayed Firing	342
12.02	Slide-Wire Bridge	319	13.04	Neon Relaxation Oscillator	343
12.03	Kelvin Bridge	320			
12.04	Measuring Small Resistances	322			
12.05	Ohmmeter Hookup	323			

13.05	Frequency of Neon Oscillator	344	13.11	Welding Time of an Ignitron	347
13.06	Practical Discharge Time in Terms of RC-Seconds	345	13.12	Cycle-Duration of Required Welds	348
13.07	Discharge Time in Seconds	346	13.13	Duty of a Welder Ignitron	349
13.08	Timing Resistor	346	13.14	Phototube Current Amplification	349
13.09	Ignitron Demand Current	346			
13.10	Ignitron. Loss to Cooling System	347			

SECTION II *Problems for Further Practice* 354

SECTION III *Some Important Tools for Radio Mathematics* 392

1	<i>Powers of 10</i>	393	3	<i>The j-Operator</i>	397
2	<i>Introduction to the Slide Rule</i>	395	4	<i>Polar Vectors</i>	405

SECTION IV *Formulas and Tables* 412

1	<i>Electronic Formulas</i>	413	3.4	Reactance and Impedance	423
1	<i>Circuit Components</i>	413	3.5	Resonant Circuits	424
1.1	Resistors	413	3.6	Filters	426
1.2	Capacitors	415	3.7	Circuit Theorems	428
1.3	Inductors and Transformers	416	4	<i>Electronic Fundamentals</i>	428
2	<i>Direct-Current Circuits</i>	419	4.1	Electron Emission	428
2.1	Ohm's Law	419	4.2	Tube Parameters	430
2.2	Circuit Theorems	419	5	<i>Amplifiers</i>	430
2.3	Batteries	421	5.1	Voltage Amplifiers	430
3	<i>Alternating-Current Circuits</i>	422	5.2	Power Amplifiers	431
3.1	Ohm's Law	422	5.3	Graphical Analysis	432
3.2	Instantaneous Values	422	5.4	Frequency Response of Resistance-Coupled Amplifier	433
3.3	Average and Effective Values	423	5.5	Gain in Decibels	433

6	<i>Oscillators</i>	434	8	<i>Receivers</i>	436
6.1	Tuned-Plate Oscillator	434	8.1	Detectors	436
6.2	Armstrong Oscillator	434	9	<i>Power Supplies</i>	436
6.3	Hartley Oscillator	434	9.1	Capacitor Input	436
6.4	Colpitts Oscillator	434	9.2	Choke Input	437
7	<i>Transmitters</i>	435	10	<i>Antennas and Transmission Lines</i>	437
7.1	Amplitude Modulation	435	11	<i>Transient Circuits</i>	439
7.2	Frequency Modulation	435	11.1	Charge of a Capacitor	439
2	<i>Tables</i>	441	12	<i>Constants Worth Remembering</i>	440
I	<i>Copper Wire Table, American Wire Gauge (B. and S.)</i>	441	III	<i>Common Logarithms</i>	443
II	<i>Specific Resistances and Temperature Coefficients</i>	442	IV	<i>Natural Sines, Cosines, Tangents and Cotangents</i>	445
			V	<i>Vector Conversion Table</i>	449
APPENDIX					
	<i>Reference List</i>	463		<i>General Index</i>	471
	<i>Answers to Section II</i>	465		<i>Mathematical Index</i>	483