

TABLE OF CONTENTS

CHAPTER I. WHAT IS MEANT BY SIGNAL TRACING?—1. The Signal Is the Common Denominator—3. Operating Voltages and Resistances Are Not Fundamental—4. The Advantages of Signal Tracing—5. Functional or Dynamic Test During Operation—6. Independent of Tube Types—7. Independent of Circuit Design—10. Control Voltage Testing—20. Audio Circuits—26.

CHAPTER II. SIGNAL AMPLIFICATION—28. Types of Amplifiers—29. Amplifying Property of the Vacuum Tube—30. Plate Current—33. Plate Resistance—37. Mutual Conductance—38. Process of Amplification—38. Plate-Current Variation and Signal Voltage—42. Phase Relations—43. Tetrode and Pentode Amplifiers—44. Factors Controlling Amplification—46. Transfer of Signal Voltage from Triode Tube to Load—49. Amplification in Tetrodes and Pentodes—53. Series and Parallel Connection of Load Impedances—55. Signal Distribution In Voltage Amplifiers—56. Amplification in Tube and Transformer—68. Audio-Frequency Amplifiers—69. Defective Amplifier Operation—75. Distortion—77. Multi-Stage Voltage Amplifiers—93. Signal Tracing in Power Amplifiers—95. Coupling to Speaker—97. Signal Levels—98. Push-Pull Operation—100. Classes of Amplifiers—103. Class B Amplifier—104.

CHAPTER III. DETECTION—107. The Diode Detector—107. Typical Diode Detector—113. Contact Potential—114. Full-Wave Detector Circuit—115. Capacity-Coupled Diode—117. Triode and Multi-Element Detectors—119. The Linear or Plate Detector—120. Tetrode and Pentode Detectors—125. The Grid-Leak Detector—127. Infinite Impedance Detector—129. Diode and Multi-Element Detectors—130.

CHAPTER IV. COUPLING DEVICES—132. Series Resonant Circuits—133. The Parallel-Resonant Circuit—134. The Simple Tuned

Transformer—135. The Double-Tuned Transformer—136. Selectivity Requirements—141. Variable Selectivity Circuits—143. Antenna Coupling Circuits—143. Image Suppression Circuits—145. Radio-Frequency Coupling Devices—147. I-F Systems—149. Audio-Frequency Coupling Circuits—154. Choke Coupling—155. Interstage Transformer Coupling—156. Direct Coupling—157. Voltage Measurements—159.
CHAPTER V. SIGNAL TRACING IN OSCILLATOR CIRCUITS—160. Fundamental Oscillator Circuits—161. A Typical Oscillator Test—165.
CHAPTER VI. SIGNAL TRACING IN MIXER CIRCUITS—172. Mixer Action—173. Gain in the Mixer—174. The Triode Mixer—175. Tetrode Mixer—179. Modern Mixer Circuits—180. Mixer Circuit Troubles—185. Signal Tracing in Converter Circuits—186. A Tetrode Autodyne Converter—187. Pentagrid Converters—189.
CHAPTER VII. SIGNAL TRACING IN CONTROL CIRCUITS—193. Delayed AVC—196. Quiet AVC—197. Controlling Gain—199. Basic Control Circuit—203. Delayed AVC Systems—209. Quiet AVC Systems—213. Signal Tracing in Automatic Frequency Control Circuits—217. Automatic Volume Expansion—225. Automatic Bass Amplifier—230. Signal Tracing In Inverse Feedback Circuits—232. Effect of Inverse Feedback on Amplifier Gain—236.
CHAPTER VIII. PUBLIC ADDRESS SYSTEMS—239.
CHAPTER IX. LOCALIZING DEFECTS BY SIGNAL TRACING. Preliminary Tests—246. The Signal Source—247. Signal Tracing in Inoperative Receivers—248. Sectional Trouble Localization—251. Tracing the A-F Signal in Inoperative Receivers—251. Signal Tracing in Weak Receivers—253. Tracing the A-F Signal in Weak Receivers—257. Tracing Noise—259. Tracing Hum—260. Tracing Distortion—261. Distortion Tracing (A-F Circuits)—263. Tracing Oscillation—265. Tracing Audio Oscillation—266. Signal Tracing in Phase Inverter Circuits—267. Signal Tracing With a Signal Generator—268. Gain Measurements in Short-Wave Receivers—271. Signal Tracing in Tuned R-F Receivers—272. Receiver Alignment With Signal-Tracing Instruments—273. Checking Tracking On Short-Wave Bands—275. Aligning Tuned R-F Receivers—275. Localizing Defects in Intermittent Receivers—276. Average Gain-Per-Stage Values—278. Average D-C Voltage Across Oscillator Grid Leak—281.

CHAPTER X. SIGNAL TRACING IN TELEVISION RECEIVERS.

The Complete Receiver—283. R-F Circuits—286. Oscillator Circuits—287. Mixer—288. Typical R-F, Oscillator, and Mixer Circuits—288. I-F Circuits—290. Video I-F Circuits—293. Video Second Detector Circuits—297. Video AVC Circuits—298. Video Amplifiers—302. Average Brightness and D-C Restorer Circuits—304. D-C Restorer Circuits—306. Basic D-C Restorer Circuit—309. Brightness Control—311. Grid Leak-Condenser Restorer—312. The Contrast Control—314. Synchronizing Circuits—314. Sync Separator Circuit—316. Horizontal Sync Selector—318. Vertical Sync Selector—319. Deflection Circuits—321. Circuits for Electromagnetic Deflection—322. Electrostatic Deflection—325. Power Supplies—326. High Voltage Power Supply in RCA TRK-5, Westinghouse WRT-701—327. Signal Tracing in Facsimile Receivers—330. Finch Facsimile Receiver—331. Circuit Analysis—333. Servicing the Receiver—334. Frequency Modulation—335. Advantages of Frequency Modulation—336. How Noise is Reduced—336. Special Receivers Necessary—337. What the Limiter Does—338. Special Detector Used—338. How the Discriminator Detects—340. The G-E Model GM125 Receiver—341. Alignment Procedure—343.

CHAPTER XI. SIGNAL TRACING IN RECEIVER DESIGN—345.

CHAPTER XII. SIGNAL-TRACING INSTRUMENTS—348. Checking RF-IF Signals—349. A-F Signal Tracing—353. Checking the Oscillator—354. Dynamic Voltage Measurements—355.