
Contents

Preface	xix
1 Introduction	1
1.1 Introduction to Power Processing	1
1.2 Several Applications of Power Electronics	7
1.3 Elements of Power Electronics	9
References	
I Converters in Equilibrium	11
2 Principles of Steady State Converter Analysis	13
2.1 Introduction	13
2.2 Inductor Volt-Second Balance, Capacitor Charge Balance, and the Small-Ripple Approximation	15
2.3 Boost Converter Example	22
2.4 Ćuk Converter Example	27
2.5 Estimating the Output Voltage Ripple in Converters Containing Two-Pole Low-Pass Filters	31
2.6 Summary of Key Points	34
References	34
Problems	35
3 Steady-State Equivalent Circuit Modeling, Losses, and Efficiency	39
3.1 The DC Transformer Model	39
3.2 Inclusion of Inductor Copper Loss	42
3.3 Construction of Equivalent Circuit Model	45

3.3.1	Inductor Voltage Equation	46	6.1.4	Differential Connection of the Load	138
3.3.2	Capacitor Current Equation	46	6.2	A Short List of Converters	143
3.3.3	Complete Circuit Model	47	6.3	Transformer Isolation	146
3.3.4	Efficiency	48	6.3.1	Full-Bridge and Half-Bridge Isolated Buck Converters	149
How to Obtain the Input Port of the Model		50	6.3.2	Forward Converter	154
Example: Inclusion of Semiconductor Conduction Losses in the Boost			6.3.3	Push-Pull Isolated Buck Converter	159
Converter Model		52	6.3.4	Flyback Converter	161
Summary of Key Points		56	6.3.5	Boost-Derived Isolated Converters	165
ferences		56	6.3.6	Isolated Versions of the SEPIC and the Ćuk Converter	168
ems		57	6.4	Converter Evaluation and Design	171
ch Realization		63	6.4.1	Switch Stress and Utilization	171
Switch Applications		65	6.4.2	Design Using Computer Spreadsheet	174
4.1.1	Single-Quadrant Switches	65	6.5	Summary of Key Points	177
4.1.2	Current-Bidirectional Two-Quadrant Switches	65	References		177
4.1.3	Voltage-Bidirectional Two-Quadrant Switches	67	Problems		179
4.1.4	Four-Quadrant Switches	71	II	Converter Dynamics and Control	185
4.1.5	Synchronous Rectifiers	72	7	AC Equivalent Circuit Modeling	187
A Brief Survey of Power Semiconductor Devices		73	7.1	Introduction	187
4.2.1	Power Diodes	74	7.2	The Basic AC Modeling Approach	192
4.2.2	Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET)	75	7.2.1	Averaging the Inductor Waveforms	193
4.2.3	Bipolar Junction Transistor (BJT)	78	7.2.2	Discussion of the Averaging Approximation	194
4.2.4	Insulated Gate Bipolar Transistor (IGBT)	81	7.2.3	Averaging the Capacitor Waveforms	196
4.2.5	Thyristors (SCR, GTO, MCT)	86	7.2.4	The Average Input Current	197
Switching Loss		88	7.2.5	Perturbation and Linearization	197
4.3.1	Transistor Switching with Clamped Inductive Load	92	7.2.6	Construction of the Small-Signal Equivalent Circuit Model	201
4.3.2	Diode Recovered Charge	93	7.2.7	Discussion of the Perturbation and Linearization Step	202
4.3.3	Device Capacitances, and Leakage, Package, and Stray Inductances	96	7.2.8	Results for Several Basic Converters	204
4.3.4	Efficiency vs. Switching Frequency	98	7.2.9	Example: A Nonideal Flyback Converter	204
Summary of Key Points		100	7.3	State-Space Averaging	213
ences		101	7.3.1	The State Equations of a Network	213
ems		102	7.3.2	The Basic State-Space Averaged Model	216
Discontinuous Conduction Mode		103	7.3.3	Discussion of the State-Space Averaging Result	217
Origin of the Discontinuous Conduction Mode, and Mode Boundary		107	7.3.4	Example: State-Space Averaging of a Nonideal Buck-Boost Converter	221
Analysis of the Conversion Ratio $M(D,K)$		108	7.4	Circuit Averaging and Averaged Switch Modeling	226
Boost Converter Example		112	7.4.1	Obtaining a Time-Invariant Circuit	228
Summary of Results and Key Points		117	7.4.2	Circuit Averaging	229
ms		124	7.4.3	Perturbation and Linearization	232
Other Circuits		126	7.4.4	Switch Networks	235
Circuit Manipulations		131	7.4.5	Example: Averaged Switch Modeling of Conduction Losses	242
6.1.1	Inversion of Source and Load	132	7.4.6	Example: Averaged Switch Modeling of Switching Losses	244
6.1.2	Cascade Connection of Converters	132	7.5	The Canonical Circuit Model	247
6.1.3	Rotation of Three-Terminal Cell	134	7.5.1	Development of the Canonical Circuit Model	248
		137			

7.5.2 Example: Manipulation of the Buck-Boost Converter Model into Canonical Form	250	9.4.1 The Phase Margin Test	341
7.5.3 Canonical Circuit Parameter Values for Some Common Converters	252	9.4.2 The Relationship Between Phase Margin and Closed-Loop Damping Factor	342
7.6 Modeling the Pulse-Width Modulator	253	9.4.3 Transient Response vs. Damping Factor	346
7.7 Summary of Key Points	256	9.5 Regulator Design	347
References	257	9.5.1 Lead (PD) Compensator	348
Problems	258	9.5.2 Lag (PI) Compensator	351
8 Converter Transfer Functions	265	9.5.3 Combined (PID) Compensator	353
8.1 Review of Bode Plots	267	9.5.4 Design Example	354
8.1.1 Single Pole Response	269	9.6 Measurement of Loop Gains	362
8.1.2 Single Zero Response	275	9.6.1 Voltage Injection	364
8.1.3 Right Half-Plane Zero	276	9.6.2 Current Injection	367
8.1.4 Frequency Inversion	277	9.6.3 Measurement of Unstable Systems	368
8.1.5 Combinations	278	9.7 Summary of Key Points	369
8.1.6 Quadratic Pole Response: Resonance	282	References	369
8.1.7 The Low-Q Approximation	287	Problems	369
8.1.8 Approximate Roots of an Arbitrary-Degree Polynomial	289	10 Input Filter Design	377
8.2 Analysis of Converter Transfer Functions	293	10.1 Introduction	377
8.2.1 Example: Transfer Functions of the Buck-Boost Converter	294	10.1.1 Conducted EMI	377
8.2.2 Transfer Functions of Some Basic CCM Converters	300	10.1.2 The Input Filter Design Problem	379
8.2.3 Physical Origins of the RHP Zero in Converters	300	10.2 Effect of an Input Filter on Converter Transfer Functions	381
8.3 Graphical Construction of Impedances and Transfer Functions	302	10.2.1 Discussion	382
8.3.1 Series Impedances: Addition of Asymptotes	303	10.2.2 Impedance Inequalities	384
8.3.2 Series Resonant Circuit Example	305	10.3 Buck Converter Example	385
8.3.3 Parallel Impedances: Inverse Addition of Asymptotes	308	10.3.1 Effect of Undamped Input Filter	385
8.3.4 Parallel Resonant Circuit Example	309	10.3.2 Damping the Input Filter	391
8.3.5 Voltage Divider Transfer Functions: Division of Asymptotes	311	10.4 Design of a Damped Input Filter	392
8.4 Graphical Construction of Converter Transfer Functions	313	10.4.1 R_f-C_b Parallel Damping	395
8.5 Measurement of AC Transfer Functions and Impedances	317	10.4.2 R_f-L_b Parallel Damping	396
8.6 Summary of Key Points	321	10.4.3 R_f-L_b Series Damping	398
References	322	10.4.4 Cascading Filter Sections	398
Problems	322	10.4.5 Example: Two Stage Input Filter	400
9 Controller Design	331	10.5 Summary of Key Points	403
9.1 Introduction	331	References	405
9.2 Effect of Negative Feedback on the Network Transfer Functions	331	Problems	406
9.2.1 Feedback Reduces the Transfer Functions from Disturbances to the Output	334	11 AC and DC Equivalent Circuit Modeling of the Discontinuous Conduction Mode	409
9.2.2 Feedback Causes the Transfer Function from the Reference Input to the Output to be Insensitive to Variations in the Gains in the Forward Path of the Loop	335	11.1 DCM Averaged Switch Model	410
9.3 Construction of the Important Quantities $1/(1 + T)$ and $T/(1 + T)$ and the Closed-Loop Transfer Functions	337	11.2 Small-Signal AC Modeling of the DCM Switch Network	420
9.4 Stability	337	11.2.1 Example: Control-to-Output Frequency Response of a DCM Boost Converter	428
	340	11.2.2 Example: Control-to-Output Frequency Responses of a CCM/DCM SEPIC	429

11.3 High-Frequency Dynamics of Converters in DCM	431
11.4 Summary of Key Points	434
References	434
Problems	435
12 Current Programmed Control	439
12.1 Oscillation for $D > 0.5$	441
12.2 A Simple First-Order Model	449
12.2.1 Simple Model via Algebraic Approach: Buck-Boost Example	450
12.2.2 Averaged Switch Modeling	454
12.3 A More Accurate Model	459
12.3.1 Current-Programmed Controller Model	459
12.3.2 Solution of the CPM Transfer Functions	462
12.3.3 Discussion	465
12.3.4 Current-Programmed Transfer Functions of the CCM Buck Converter	466
12.3.5 Results for Basic Converters	469
12.3.6 Quantitative Effects of Current-Programmed Control on the Converter Transfer Functions	471
12.4 Discontinuous Conduction Mode	473
12.5 Summary of Key Points	480
References	481
Problems	482
III Magnetics	489
13 Basic Magnetics Theory	491
13.1 Review of Basic Magnetics	491
13.1.1 Basic Relationships	491
13.1.2 Magnetic Circuits	491
13.2 Transformer Modeling	498
13.2.1 The Ideal Transformer	501
13.2.2 The Magnetizing Inductance	502
13.2.3 Leakage Inductances	502
13.3 Loss Mechanisms in Magnetic Devices	504
13.3.1 Core Loss	506
13.3.2 Low-Frequency Copper Loss	506
13.4 Eddy Currents in Winding Conductors	508
13.4.1 Introduction to the Skin and Proximity Effects	508
13.4.2 Leakage Flux in Windings	512
13.4.3 Foil Windings and Layers	514
13.4.4 Power Loss in a Layer	515
13.4.5 Example: Power Loss in a Transformer Winding	518
13.4.6 Interleaving the Windings	520
13.4.7 PWM Waveform Harmonics	522

13.5 Several Types of Magnetic Devices, Their $B-H$ Loops, and Core vs. Copper Loss	525
13.5.1 Filter Inductor	525
13.5.2 AC Inductor	527
13.5.3 Transformer	528
13.5.4 Coupled Inductor	529
13.5.5 Flyback Transformer	530
13.6 Summary of Key Points	531
References	532
Problems	533
14 Inductor Design	539
14.1 Filter Inductor Design Constraints	541
14.1.1 Maximum Flux Density	541
14.1.2 Inductance	542
14.1.3 Winding Area	542
14.1.4 Winding Resistance	543
14.1.5 The Core Geometrical Constant K_g	543
14.2 A Step-by-Step Procedure	544
14.3 Multiple-Winding Magnetics Design via the K_g Method	545
14.3.1 Window Area Allocation	545
14.3.2 Coupled Inductor Design Constraints	550
14.3.3 Design Procedure	552
14.4 Examples	554
14.4.1 Coupled Inductor for a Two-Output Forward Converter	554
14.4.2 CCM Flyback Transformer	557
14.5 Summary of Key Points	562
References	562
Problems	563
15 Transformer Design	565
15.1 Transformer Design: Basic Constraints	565
15.1.1 Core Loss	566
15.1.2 Flux Density	566
15.1.3 Copper Loss	567
15.1.4 Total Power Loss vs. ΔB	568
15.1.5 Optimum Flux Density	569
15.2 A Step-by-Step Transformer Design Procedure	570
15.3 Examples	573
15.3.1 Example 1: Single-Output Isolated Ćuk Converter	573
15.3.2 Example 2: Multiple-Output Full-Bridge Buck Converter	576
15.4 AC Inductor Design	580
15.4.1 Outline of Derivation	580
15.4.2 Step-by-Step AC Inductor Design Procedure	582

15.5	Summary	583
References		583
Problems		584
IV Modern Rectifiers and Power System Harmonics		
16 Power and Harmonics in Nonsinusoidal Systems		587
16.1	Average Power	589
16.2	Root-Mean-Square (RMS) Value of a Waveform	590
16.3	Power Factor	593
16.3.1	Linear Resistive Load, Nonsinusoidal Voltage	594
16.3.2	Nonlinear Dynamic Load, Sinusoidal Voltage	594
16.4	Power Phasors in Sinusoidal Systems	595
16.5	Harmonic Currents in Three-Phase Systems	598
16.5.1	Harmonic Currents in Three-Phase Four-Wire Networks	599
16.5.2	Harmonic Currents in Three-Phase Three-Wire Networks	599
16.5.3	Harmonic Current Flow in Power Factor Correction Capacitors	601
16.6	AC Line Current Harmonic Standards	602
16.6.1	International Electrotechnical Commission Standard 1000	603
16.6.2	IEEE/ANSI Standard 519	603
Bibliography		604
Problems		605
17 Line-Commutated Rectifiers		
17.1	The Single-Phase Full-Wave Rectifier	609
17.1.1	Continuous Conduction Mode	609
17.1.2	Discontinuous Conduction Mode	610
17.1.3	Behavior when C is Large	611
17.1.4	Minimizing THD when C is Small	612
17.2	The Three-Phase Bridge Rectifier	613
17.2.1	Continuous Conduction Mode	615
17.2.2	Discontinuous Conduction Mode	615
17.3	Phase Control	616
17.3.1	Inverter Mode	617
17.3.2	Harmonics and Power Factor	619
17.3.3	Commutation	619
17.4	Harmonic Trap Filters	620
17.5	Transformer Connections	622
17.6	Summary	628
References		630
Problems		631
18 Pulse-Width Modulated Rectifiers		
18.1	Properties of the Ideal Rectifier	637
	AC Harmonic Distortion	638
18.2	Realization of a Near-Ideal Rectifier	641
18.2.1	CCM Boost Converter	641
18.2.2	DCM Flyback Converter	641
18.3	Control of the Current Waveform	641
18.3.1	Average Current Control	641
18.3.2	Current Programmed Control	651
18.3.3	Critical Conduction Mode and Hysteretic Control	651
18.3.4	Nonlinear Carrier Control	651
18.4	Single-Phase Converter Systems Incorporating Ideal Rectifiers	661
18.4.1	Energy Storage	661
18.4.2	Modeling the Outer Low-Bandwidth Control System	661
18.5	RMS Values of Rectifier Waveforms	671
18.5.1	Boost Rectifier Example	671
18.5.2	Comparison of Single-Phase Rectifier Topologies	671
18.6	Modeling Losses and Efficiency in CCM High-Quality Rectifiers	671
18.6.1	Expression for Controller Duty Cycle $d(t)$	671
18.6.2	Expression for the DC Load Current	681
18.6.3	Solution for Converter Efficiency η	681
18.6.4	Design Example	681
18.7	Ideal Three-Phase Rectifiers	681
18.8	Summary of Key Points	681
References		691
Problems		691
V Resonant Converters		
19 Resonant Conversion		
19.1	Sinusoidal Analysis of Resonant Converters	701
19.1.1	Controlled Switch Network Model	711
19.1.2	Modeling the Rectifier and Capacitive Filter Networks	711
19.1.3	Resonant Tank Network	711
19.1.4	Solution of Converter Voltage Conversion Ratio $M = V/V_g$	711
19.2	Examples	711
19.2.1	Series Resonant DC-DC Converter Example	711
19.2.2	Subharmonic Modes of the Series Resonant Converter	711
19.2.3	Parallel Resonant DC-DC Converter Example	711
19.3	Soft Switching	711
19.3.1	Operation of the Full Bridge Below Resonance: Zero-Current Switching	711
19.3.2	Operation of the Full Bridge Above Resonance: Zero-Voltage Switching	721
19.4	Load-Dependent Properties of Resonant Converters	721
19.4.1	Inverter Output Characteristics	721
19.4.2	Dependence of Transistor Current on Load	729
19.4.3	Dependence of the ZVS/ZCS Boundary on Load Resistance	731

19.4.4 Another Example	737	B.2.3 Example: DCM Boost Rectifier	832
19.5 Exact Characteristics of the Series and Parallel Resonant Converters	740	B.3 Current Programmed Control	834
19.5.1 Series Resonant Converter	740	B.3.1 Current Programmed Mode Model for Simulation	834
19.5.2 Parallel Resonant Converter	748	B.3.2 Example: Frequency Responses of a Buck Converter with	837
19.6 Summary of Key Points	752	Current Programmed Control	840
References	752	References	840
Problems	755	Appendix C Middlebrook's Extra Element Theorem	843
20 Soft Switching	761	C.1 Basic Result	843
20.1 Soft-Switching Mechanisms of Semiconductor Devices	761	C.2 Derivation	846
20.1.1 Diode Switching	762	C.3 Discussion	849
20.1.2 MOSFET Switching	763	C.4 Examples	850
20.1.3 IGBT Switching	765	C.4.1 A Simple Transfer Function	850
20.2 The Zero-Current-Switching Quasi-Resonant Switch Cell	768	C.4.2 An Unmodeled Element	855
20.2.1 Waveforms of the Half-Wave ZCS Quasi-Resonant Switch Cell	768	C.4.3 Addition of an Input Filter to a Converter	857
20.2.2 The Average Terminal Waveforms	770	C.4.4 Dependence of Transistor Current on Load in a Resonant Inverter	859
20.2.3 The Full-Wave ZCS Quasi-Resonant Switch Cell	774	References	861
20.3 Resonant Switch Topologies	779	Appendix D Magnetics Design Tables	863
20.3.1 The Zero-Voltage-Switching Quasi-Resonant Switch	781	D.1 Pot Core Data	864
20.3.2 The Zero-Voltage-Switching Multi-Resonant Switch	783	D.2 EE Core Data	865
20.3.3 Quasi-Square-Wave Resonant Switches	784	D.3 EC Core Data	866
20.4 Soft Switching in PWM Converters	787	D.4 ETD Core Data	866
20.4.1 The Zero-Voltage Transition Full-Bridge Converter	790	D.5 PQ Core Data	867
20.4.2 The Auxiliary Switch Approach	791	D.6 American Wire Gauge Data	868
20.4.3 Auxiliary Resonant Commutated Pole	794	References	869
20.5 Summary of Key Points	796	Index	871
References	797		
Problems	798		
Appendices	800		
Appendix A RMS Values of Commonly-Observed Converter Waveforms	803		
A.1 Some Common Waveforms	805		
A.2 General Piecewise Waveform	805		
Appendix B Simulation of Converters	809		
B.1 Averaged Switch Models for Continuous Conduction Mode	813		
B.1.1 Basic CCM Averaged Switch Model	815		
B.1.2 CCM Subcircuit Model that Includes Switch Conduction Losses	815		
B.1.3 Example: SEPIC DC Conversion Ratio and Efficiency	816		
B.1.4 Example: Transient Response of a Buck-Boost Converter	818		
B.2 Combined CCM/DCM Averaged Switch Model	819		
B.2.1 Example: SEPIC Frequency Responses	822		
B.2.2 Example: Loop Gain and Closed-Loop Responses of a Buck Voltage Regulator	825		
	827		