

CONTENTS

Preface

page xiii

1 A MICROHISTORY OF MICROWAVE TECHNOLOGY

1. Introduction	1
2. Birth of the Vacuum Tube	11
3. Armstrong and the Regenerative Amplifier/Detector/Oscillator	14
4. The Wizard War	18
5. Some Closing Comments	27
6. Appendix A: Characteristics of Other Wireless Systems	27
7. Appendix B: Who Really Invented Radio?	29

2 INTRODUCTION TO RF AND MICROWAVE CIRCUITS

1. Definitions	37
2. Conventional Frequency Bands	38
3. Lumped versus Distributed Circuits	41
4. Link between Lumped and Distributed Regimes	44
5. Driving-Point Impedance of Iterated Structures	44
6. Transmission Lines in More Detail	46
7. Behavior of Finite-Length Transmission Lines	51
8. Summary of Transmission Line Equations	53
9. Artificial Lines	54
10. Summary	58

3 THE SMITH CHART AND S-PARAMETERS

1. Introduction	60
2. The Smith Chart	60
3. S-Parameters	66
4. Appendix A: A Short Note on Units	69
5. Appendix B: Why 50 (or 75) Ω ?	71

4	IMPEDANCE MATCHING	74
1.	Introduction	74
2.	The Maximum Power Transfer Theorem	75
3.	Matching Methods	77
5	CONNECTORS, CABLES, AND WAVEGUIDES	108
1.	Introduction	108
2.	Connectors	108
3.	Coaxial Cables	115
4.	Waveguides	118
5.	Summary	120
6.	Appendix: Properties of Coaxial Cable	121
6	PASSIVE COMPONENTS	123
1.	Introduction	123
2.	Interconnect at Radio Frequencies: Skin Effect	123
3.	Resistors	129
4.	Capacitors	133
5.	Inductors	138
6.	Magnetically Coupled Conductors	147
7.	Summary	157
7	MICROSTRIP, STRIPLINE, AND PLANAR PASSIVE ELEMENTS	158
1.	Introduction	158
2.	General Characteristics of PC Boards	158
3.	Transmission Lines on PC Board	162
4.	Passives Made from Transmission Line Segments	178
5.	Resonators	181
6.	Combiners, Splitters, and Couplers	183
7.	Summary	230
8.	Appendix A: Random Useful Inductance Formulas	230
9.	Appendix B: Derivation of Fringing Correction	233
10.	Appendix C: Dielectric Constants of Other Materials	237
8	IMPEDANCE MEASUREMENT	238
1.	Introduction	238
2.	The Time-Domain Reflectometer	238
3.	The Slotted Line	246
4.	The Vector Network Analyzer	254
5.	Summary of Calibration Methods	264
6.	Other VNA Measurement Capabilities	265
7.	References	265
8.	Appendix A: Other Impedance Measurement Devices	265
9.	Appendix B: Projects	268

9 MICROWAVE DIODES	275
1. Introduction	275
2. Junction Diodes	276
3. Schottky Diodes	279
4. Varactors	281
5. Tunnel Diodes	284
6. PIN Diodes	287
7. Noise Diodes	289
8. Snap Diodes	290
9. Gunn Diodes	293
10. MIM Diodes	295
11. IMPATT Diodes	295
12. Summary	297
13. Appendix: Homegrown “Penny” Diodes and Crystal Radios	297
10 MIXERS	305
1. Introduction	305
2. Mixer Fundamentals	306
3. Nonlinearity, Time Variation, and Mixing	312
4. Multiplier-Based Mixers	317
11 TRANSISTORS	341
1. History and Overview	341
2. Modeling	351
3. Small-Signal Models for Bipolar Transistors	352
4. FET Models	361
5. Summary	368
12 AMPLIFIERS	369
1. Introduction	369
2. Microwave Biasing 101	370
3. Bandwidth Extension Techniques	381
4. The Shunt-Series Amplifier	395
5. Tuned Amplifiers	413
6. Neutralization and Unilateralization	417
7. Strange Impedance Behaviors and Stability	420
8. Appendix: Derivation of Bridged T-Coil Transfer Function	427
13 LNA DESIGN	440
1. Introduction	440
2. Classical Two-Port Noise Theory	440
3. Derivation of a Bipolar Noise Model	445
4. The Narrowband LNA	451
5. A Few Practical Details	455

6. Appendix A: Network Synthesis	766
7. Appendix B: Elliptic Integrals, Functions, and Filters	774
8. Appendix C: Design Tables for Common Low-pass Filters	781
23 MICROSTRIP FILTERS	784
1. Background	784
2. Distributed Filters from Lumped Prototypes	784
3. Coupled Resonator Bandpass Filters	803
4. Practical Considerations	841
5. Summary	843
6. Appendix: Lumped Equivalents of Distributed Resonators	844
<i>Index</i>	847