

Contents

1	Introduction	1
1.1	Introduction	1
1.2	What Is Power Electronics?	2
1.2.1	Recent Growth in Power Electronics	3
1.3	The History of Power Electronics	4
1.3.1	The History of <i>dc</i> and <i>ac</i> Electricity in the Late Nineteenth Century	4
1.3.2	The History of <i>dc</i> and <i>ac</i> Electricity in the Late Twentieth Century	6
1.3.3	History of Modern Power Electronics	6
1.4	The Need for Power Conversion	7
1.5	Power Electronic Systems	8
1.5.1	Classification of Power Converter Circuits	10
1.5.2	Power Semiconductor Devices	17
1.5.3	Converter Modeling and Control	18
1.6	Applications of Power Electronics	19
1.7	Future Trends	19
1.8	About the Text and Its Nomenclatures	20
1.8.1	About the Text	20
1.8.2	Nomenclature	21
2	Review of Switching Concepts and Power Semiconductor Devices	25
2.1	Introduction	25
2.2	The Need for Switching in Power Electronic Circuits	26
2.3	Switching Characteristics	31
2.3.1	The Ideal Switch	31
2.3.2	The Practical Switch	31
2.4	Switching Functions and Matrix Representation	38
2.5	Types of Switches	47

2.6	Available Semiconductor Switching Devices	49
2.6.1	Bipolar and Unipolar Devices	49
2.6.2	Thyristor-Based Devices	69
2.7	Comparison of Power Devices	76
2.8	Future Trends in Power Devices	77
2.9	Snubber Circuits	78
2.10	Interest in High-Temperature Power Devices: The Wide Band Gap	79
	Problems	81
3	Switching Circuits, Power Computations, and Component Concepts	93
3.1	Introduction	93
3.2	Switching Diode Circuits	93
3.2.1	Switching Diode Circuits Under <i>dc</i> Excitation	93
3.2.2	Switching Diode Circuits with an <i>ac</i> Source	102
3.3	Controlled Switching Circuits	108
3.4	Basic Power and Harmonic Concepts	111
3.4.1	Average, Reactive, and Apparent Powers	111
3.4.2	Sinusoidal Waveforms	115
3.4.3	Non-sinusoidal Waveforms	120
3.5	Capacitor and Inductor Responses	135
3.5.1	Capacitor Transient Response	135
3.5.2	Capacitor Steady-State Response	139
3.5.3	Inductor Transient Response	139
3.5.4	Inductor Steady-State Response	142
	Problems	144
4	Non-isolated Switch Mode DC-DC Converters	173
4.1	Introduction	173
4.2	Power Supply Application	174
4.2.1	Linear Regulators	174
4.2.2	Switch-Mode Power Supplies	175
4.3	Continuous Conduction Mode	177
4.3.1	The Buck Converter	182
4.3.2	The Boost Converter	196
4.3.3	The Buck-Boost Converter	205
4.3.4	The Fourth-Order Converters	211
4.3.5	Bipolar Output Voltage Converter	225
4.4	Discontinuous Conduction Mode	227
4.4.1	The Buck Converter	228
4.4.2	The Boost Converter	234
4.4.3	The Buck-Boost Converter	238

4.5	The Effects of Converter Non-idealities	243
4.5.1	Inductor Resistance	243
4.5.2	The Boost Converter	246
4.5.3	Transistor and Diode Voltage Drops	248
4.5.4	The Effect of Switch Resistance	250
4.6	Switch Utilization Factor	257
	Problems	260
5	Isolated Switch-Mode DC-DC Converters	273
5.1	Introduction	273
5.2	Transformer Circuit Configurations	274
5.2.1	Transformer Model	274
5.2.2	Circuit Configurations	275
5.3	Buck-Derived Isolated Converters	277
5.3.1	Single-Ended Forward Converter	281
5.3.2	Half-Bridge Converters	290
5.3.3	Full-Bridge Converter	291
5.3.4	Push-Pull Converter	297
5.4	Boost-Derived Isolated Converters	303
5.4.1	Single-Ended Flyback Converter	303
5.4.2	Half-Bridge Converter	312
5.4.3	Full-Bridge Converter	312
5.5	Other Isolated Converters	319
5.5.1	Isolated Cuk Converter	319
5.5.2	The Weinberg Converter	321
5.6	Multi-output Converter	329
	Problems	330
6	Soft-Switching dc-dc Converters	347
6.1	Types of dc-dc Converters	347
6.1.1	The Resonant Concept	348
6.1.2	Resonant Versus Conventional PWM	349
6.2	Classification of Soft-Switching Resonant Converters	350
6.3	Advantages and Disadvantages of ZCS and ZVS	351
6.3.1	Switching Loci	351
6.3.2	Switching Losses	351
6.4	Zero-Current Switching Topologies	352
6.4.1	The Resonant Switch	352
6.4.2	Steady-State Analysis	354
6.5	Zero-Voltage Switching Topologies	383
6.5.1	Resonant Switch Arrangements	384
6.5.2	Steady-State Analyses	384
6.6	Zero-Voltage and Zero-Current Transition Converters	398
6.6.1	Switching Transition	398
6.6.2	The ZVT Buck Converter	400

6.6.3	The ZVT Boost Converter	408
6.6.4	The Practical ZVT Boost Converter	416
6.7	Generalized Analysis for ZCS	429
6.7.1	The Generalized Switching Cell	430
6.7.2	The Generalized Transformation Table	431
6.7.3	The Basic Operation of the ZCS-QRC Cell	433
6.7.4	The Basic Operation of the ZVS-QRC Cell	437
	Problems	447
7	Uncontrolled Diode Rectifier Circuits	461
7.1	Introduction	461
7.2	Single-Phase Rectifier Circuits	463
7.2.1	Resistive Load	463
7.2.2	Inductive Load	467
7.2.3	Capacitive Load Rectifiers	475
7.2.4	Voltage Source in the dc Side	478
7.3	The Effect of the ac-Side Inductance	479
7.3.1	Half-Wave Rectifier with Inductive Load	479
7.3.2	Half-Wave Rectifier with Capacitive Load	484
7.3.3	Full-Wave Rectifiers with an Inductive Load	489
7.4	Three-Phase Rectifier Circuits	492
7.4.1	Three-Phase Half-Wave Rectifier	493
7.4.2	Three-Phase Full-Wave Rectifiers	499
7.5	Ac-Side Inductance in Three-Phase Rectifier Circuits	501
7.5.1	Half-Wave Rectifiers	501
7.5.2	Full-Wave Bridge Rectifiers	506
	Problems	510
8	Phase-Controlled Converters	525
8.1	Introduction	525
8.2	Basic Phase-Controlled Concepts	526
8.3	Half-Wave Phase-Controlled Rectifiers	528
8.3.1	Resistive Load	528
8.3.2	Inductive Load	530
8.4	Full-Wave Phase-Controlled Rectifiers	535
8.4.1	Resistive Load	535
8.4.2	Inductive Load	537
8.5	Effect of AC-Side Inductance	550
8.5.1	Half-Wave Circuits	550
8.5.2	Full-Wave Rectifier Circuits	552
8.6	Three-Phase Phase-Controlled Converters	557
8.6.1	Half-Wave Converters	557
8.6.2	Full-Wave Converters	557
	Problems	566

9	dc-ac Inverters	575
9.1	Basic Block Diagram of dc-ac Inverters	576
9.1.1	Voltage- and Current-Source Inverters	577
9.1.2	Inverter Configurations	578
9.1.3	Output Voltage Control	578
9.2	Basic Half-Bridge Inverter Circuit	578
9.2.1	Resistive Load	578
9.2.2	Inductive-Resistive Load	583
9.3	Full-Bridge Inverters	593
9.3.1	Approximate Analysis	599
9.3.2	Generalized Analysis	600
9.4	Harmonic Reduction	609
9.4.1	Harmonic Analysis	610
9.5	Pulse Width Modulation	616
9.5.1	Equal-Pulse (Uniform) PWM	618
9.5.2	Sinusoidal PWM	626
9.6	Three-Phase Inverters	640
9.7	Current-Source Inverters	648
	Problems	651

Bibliography	663
--------------	-----

Index	667
-------	-----