

Contents

<i>Preface</i>	page xv
<i>Notation and Symbols</i>	xix
1 A System Introduction to Microwave Electronics	1
1.1 Radio Frequencies, Microwaves, Millimeter Waves	1
1.2 Transmitting Information Through RF and Microwaves	4
1.2.1 A Review of Signal Modulation	5
1.2.2 The RF Interface: Architecture	7
1.2.3 Linear and Nonlinear Building Blocks of the RF Interface	14
1.3 Enabling Technologies for RF, Microwaves and mm Waves	18
1.3.1 Examples of (M)MICs	22
1.4 Questions and Problems	25
1.4.1 Questions	25
1.4.2 Problems	26
<i>References</i>	26
2 Passive Elements and Circuit Layout	28
2.1 Transmission Lines	28
2.1.1 Transmission Line Theory	28
2.1.2 Parameters of Quasi-TEM Lines	38
2.1.3 The Reflection Coefficient and the Smith Chart	43
2.2 Planar Transmission Lines in Microwave Integrated Circuits	51
2.2.1 The Coaxial Cable	53
2.2.2 The Microstrip	54
2.2.3 The Coplanar Waveguide	59
2.2.4 Coupling and Radiation Losses in Planar Lines	62
2.3 Lumped Parameter Components	65
2.3.1 Inductors	66
2.3.2 Capacitors	71
2.3.3 Resistors	72
2.3.4 Chip Inductors, Resistors and Capacitors	73
2.4 Layout of Planar Hybrid and Integrated Circuits	74
2.4.1 Some Layout-Related Issues	75

	2.4.2 Hybrid Layout	78
	2.4.3 Integrated Layout	79
2.5	Microwave Circuit Packaging	81
2.6	Questions and Problems	84
	2.6.1 Questions	84
	2.6.2 Problems	84
	<i>References</i>	85
3	CAD Techniques	87
	3.1 Modeling of Linear and Nonlinear Blocks	87
	3.2 Power Waves and the Scattering Parameters	89
	3.2.1 Representations of Linear Two-Ports	89
	3.2.2 Power Waves	92
	3.2.3 Power Wave n -Port Model: The Scattering Matrix	93
	3.2.4 Properties of the S-Matrix	97
	3.2.5 Power Wave Equivalent Circuit	100
	3.2.6 Direct Evaluation of the Scattering Parameters	102
	3.2.7 Reference Plane Shift	103
	3.2.8 Cascade Connection of Two-Ports: The T-Matrix	105
	3.2.9 Solving a Network in Terms of Power Waves	106
	3.3 Analysis Techniques for Linear and Nonlinear Circuits	108
	3.3.1 Time-Domain vs. Frequency-Domain Methods	108
	3.3.2 The Harmonic Balance Technique	108
	3.3.3 The HB Technique: Multi-Tone Excitation	112
	3.3.4 The Envelope HB Time-Frequency Technique	119
	3.4 Circuit Optimization and Layout Generation	123
	3.5 Questions and Problems	124
	3.5.1 Questions	124
	3.5.2 Problems	125
	<i>References</i>	126
4	Directional Couplers and Power Dividers	129
	4.1 Coupled Quasi-TEM Lines	129
	4.1.1 Analysis of Symmetrical Coupled Lines	129
	4.1.2 Coupled Planar Lines	134
	4.1.3 Coupled Microstrips	135
	4.2 The Directional Coupler	139
	4.2.1 General Properties of Directional Couplers and Power Dividers	141
	4.3 The Two-Conductor Coupled Line Coupler	144
	4.3.1 Frequency Behavior of the Synchronous Coupler	149
	4.3.2 Effect of Velocity Mismatch and Compensation Techniques	152
	4.4 Multiconductor Line Couplers	155
	4.4.1 The Lange Coupler	160

4.5	Interference Couplers	162
4.5.1	Branch-Line Coupler	162
4.5.2	Lumped-Parameter Branch-Line Couplers	168
4.5.3	The Hybrid Ring	172
4.6	Power Combiners and Dividers	173
4.6.1	The Wilkinson Distributed Divider	174
4.6.2	Wilkinson Lumped Dividers	179
4.7	Directional Couplers Summary	181
4.8	Questions and Problems	182
4.8.1	Questions	182
4.8.2	Problems	183
	<i>References</i>	184

5	Active RF and Microwave Semiconductor Devices	185
5.1	Active Microwave Components	185
5.1.1	Semiconductor Microwave Components	185
5.1.2	Device Modeling Approaches	190
5.2	Semiconductors and Semiconductor Alloys for Microwave Transistors	192
5.2.1	Semiconductor Properties: A Reminder	193
5.2.2	Transport Properties	197
5.2.3	Heterostructures and Semiconductor Alloys	199
5.2.4	The Substrate Issue	202
5.3	Heterojunctions and Reduced Dimensionality Structures	203
5.4	Microwave Schottky-Gate Field-Effect Transistors	205
5.4.1	FET DC Model	209
5.4.2	Choice of the DC Working Point	211
5.4.3	FET Small-Signal Model and Equivalent Circuit	211
5.4.4	Scaling the Small-Frequency Parameters vs. the Gate Periphery	218
5.4.5	Frequency Behavior of the Scattering Parameters	219
5.4.6	High-Speed Compound Semiconductor FETs: The HEMT Family	222
5.5	The RF MOSFET	230
5.6	Microwave FETs: A Comparison	232
5.7	Heterojunction Bipolar Transistors	234
5.7.1	HBT Equivalent Circuit	237
5.7.2	HBT Choices and Material Systems	240
5.8	Measurement-Based Microwave FET Small- and Large-Signal Models	242
5.8.1	Small- and Large-Signal Circuit Models	242
5.8.2	Extracting the Small-Signal Equivalent Circuit from Measurements	242
5.8.3	Large-Signal FET Circuit Model Principles	246

5.8.4	MESFET LS Models	249
5.8.5	HEMT LS Models	252
5.9	Measurement-Based Bipolar Small- and Large-Signal Models	254
5.10	Questions and Problems	255
5.10.1	Questions	255
5.10.2	Problems	256
	<i>References</i>	257
6	Microwave Linear Amplifiers	261
6.1	Introduction	261
6.2	Generator-Load Power Transfer	262
6.2.1	Generator Directly Connected to Load	262
6.2.2	Power Transfer in Loaded Two-Ports	265
6.3	Power Gains of a Loaded Two-Port	268
6.3.1	Maximum Gain and Maximum Power Transfer	268
6.3.2	Operational Gain	270
6.3.3	Available Power Gain	274
6.3.4	Transducer Gain	275
6.3.5	Power Matching and Unconditional Stability	275
6.4	Two-Port Stability	276
6.4.1	Analysis of Stability Conditions	279
6.5	Two-Port Stability Criteria	283
6.5.1	Two-Parameter Criteria	283
6.5.2	Proof of Two-Parameter Stability Criteria	284
6.5.3	One-Parameter Stability Criterion	289
6.5.4	Proof of the One-Parameter Criterion	289
6.6	Two-Port Stability and Power Matching	290
6.6.1	Unconditional Stability and Simultaneous Power Matching	290
6.6.2	Managing Conditional Stability	292
6.6.3	Stability Circles and Constant Gain Contours	292
6.6.4	Unilateral Two-Port	293
6.7	Examples of FET Stability Behavior	295
6.7.1	Stability and Gains at Constant Frequency	295
6.7.2	Stability and Gains as a Function of Frequency	297
6.8	Linear Microwave Amplifier Classes	300
6.8.1	The Linear Amplifier – Design Steps	303
6.9	The Open-Loop Narrowband Amplifier	304
6.9.1	Design of Matching Sections	306
6.10	Active Device Stabilization and Bias	314
6.10.1	Stabilization	314
6.10.2	DC Bias	318
6.11	The Open-Loop Wideband Amplifier	320

6.11.1	The Balanced Amplifier	321
6.12	The Wideband Feedback Amplifier	326
6.13	The Distributed Amplifier	334
6.13.1	The Continuous Distributed Amplifier	336
6.13.2	The Discrete Cell Distributed Amplifier	342
6.14	Questions and Problems	349
6.14.1	Questions	349
6.14.2	Problems	349
	<i>References</i>	350

7	Low-Noise Amplifier Design	352
7.1	Introduction	352
7.2	A Review of Random Processes	353
7.2.1	First- and Second-Order Statistics	353
7.2.2	Random Process Through Linear Systems	357
7.2.3	Symbolic Frequency-Domain (Phasor) Notation	358
7.3	Analyzing Circuits with Random Generators: The Symbolic Technique	359
7.4	Equivalent Circuit of Noisy Linear N -Ports	362
7.4.1	Noisy One-Ports	362
7.4.2	Noisy N -Ports	363
7.5	The Physical Origin of Noise	366
7.5.1	Thermal and Diffusion Noise	367
7.5.2	RG Noise	367
7.5.3	$1/f$ or Flicker Noise	368
7.6	Noise Models of Passive Devices	368
7.6.1	Noise in Passive Devices: The Nyquist Law	369
7.6.2	Noise in Junction Diodes	371
7.7	System-Oriented Device Noise Parameters: The Noise Figure	372
7.7.1	Evaluating the Noise Figure	374
7.7.2	The Minimum Noise Figure	381
7.8	Noise Models of Microwave Transistors	385
7.8.1	Noise Models of Field-Effect Transistors	385
7.8.2	Noise Models for Bipolar Transistors	389
7.9	Noise Figure of Cascaded Two-Ports	390
7.9.1	Noise Measure	392
7.10	Low-Noise Amplifiers	392
7.10.1	Common-Gate (Base) LNA Stage	394
7.10.2	LNA with Inductive Source/Emitter Series Feedback	398
7.11	Questions and Problems	407
7.11.1	Questions	407
7.11.2	Problems	408
	<i>References</i>	409

8	Power Amplifiers	411
8.1	Introduction	411
8.2	Characteristics of Power Amplifiers	412
8.2.1	Power, Gain, Distortion	412
8.2.2	AM–AM and AM–PM Characteristics	420
8.2.3	Dynamic Range	422
8.2.4	Efficiency and Power Added Efficiency	423
8.2.5	Input Matching	424
8.3	Power Amplifier Classes	424
8.4	The Quasi-Linear Power Amplifier (Class A)	426
8.4.1	Class A Design and the Load-Pull Approach	432
8.5	Analysis of Distortion and Power Saturation in a Class A Amplifier	437
8.5.1	Power-Series Analysis of Compression and Intermodulation	437
8.5.2	Power Saturation in Class A	443
8.6	Nonlinear Amplifier Classes: AB, B, C	444
8.6.1	Single-Ended Class B Amplifier	445
8.6.2	From Class A to Class C Amplifier	448
8.7	High-Efficiency Amplifiers	456
8.7.1	Harmonic Loading: The Class F Amplifier	456
8.7.2	The Switching Class E Power Amplifier	460
8.7.3	The Doherty Amplifier	468
8.8	Layout and Power Combining Techniques	481
8.9	Linearization Techniques	481
8.10	Questions and Problems	484
8.10.1	Questions	484
8.10.2	Problems	486
	<i>References</i>	487
9	Microwave Measurements	489
9.1	Introduction	489
9.2	Basic Microwave Instrumentation Tools	489
9.3	The Reflectometer	491
9.4	The Vector Network Analyzer	497
9.4.1	Downconversion Module Solutions	497
9.4.2	VNA Calibration	499
9.4.3	Defining the Error Model	500
9.4.4	Calibration Algorithms	501
9.5	Load and Source Pull Characterization	507
9.5.1	Scalar Systems	508
9.5.2	Vectorial Systems	509
9.5.3	Load Tuning Techniques	510
9.6	System-Level Characterization	513
9.7	Noise Measurements	514
9.8	Questions and Problems	517

	9.8.1 Questions	517
	9.8.2 Problems	518
	<i>References</i>	519
10	CAD Projects	522
	10.1 Introduction	522
	10.2 Microstrip Line and Stub Matching of a Complex Load	522
	10.3 Design of a 3 dB Directional Coupler at 20 GHz	524
	10.4 Fitting and Optimization of a Field-Effect Small-Signal Equivalent Circuit	528
	10.5 Small-Signal FET Stabilization	531
	10.6 Design of a Maximum Gain Amplifier at 15 GHz	532
	10.7 Design of a Two-Stage Balanced Amplifier	538
	10.8 Design of Parallel Resistive Feedback Wideband Amplifiers	543
	10.9 Design of a Uniform DAMP with 40 GHz Bandwidth	546
	10.10 FET Noise, Single-Ended and Balanced LNA Design	550
	10.11 Design of 5 GHz LNA with Source Inductive Series Feedback	554
	10.12 Design of a 3.5 GHz Narrowband Hybrid Class A Power Amplifier	556
	10.13 Design of a 3.5 GHz Narrowband Hybrid Class B and AB Power Amplifier	561
	<i>References</i>	564
	<i>Index</i>	566