

Contents:

PREFACE	3
PART A: ANALOG CIRCUITS AND DEVICES	5
1. SEMICONDUCTOR DIODES	5
1.1 A Topic Overview	5
1.1.1 Semiconductor materials	5
1.1.2 A PN junction	6
1.1.3 A semiconductor diode	8
1.1.4 Zener diode	8
1.1.5 Light emitting diodes (LED)	9
1.2 Application Examples	10
1.2.1 Rectifier circuits	10
1.2.2 A simple Zener regulator	11
1.2.3 A LED driver	12
1.3. Laboratory Projects	12
1.4. Questions and Problems	14
2. TRANSISTORS AND TRANSISTOR CIRCUITS	15
2.1 A Topic Overview	15
2.1.1 Bipolar junction transistor	15
2.1.2 Field effect transistors	19
2.2 Application Examples	21
2.2.1 A transistor amplifier	21
2.2.2 Special types of transistor amplifiers	24
2.2.3 Feedback	25
2.2.4 A transistor switching circuit	26
2.3. Laboratory Projects	27
2.4. Questions and Problems	31
3. OPERATIONAL AMPLIFIERS	33
3.1 A Topic Overview	33
3.1.1 Integrated circuits	33
3.1.2 Operational amplifier	35
3.2 Application Examples	36
3.2.1 The inverting amplifier	36
3.2.2 The summing amplifier	37
3.2.3 The noninverting amplifier	37
3.2.4 The differential amplifier	38
3.2.5 The comparator	39
3.2.6 The integrator	40
3.2.7 Multivibrators with Op-Amps	40
3.3. Laboratory Projects	42

MICROELECTRONICS (Contents)

3.4. Questions and Problems	44
PART B: DIGITAL CIRCUITS	46
4. BASIC LOGIC CIRCUITS	46
4.1 A Topic Overview	46
4.1.1 Logic statements and Boolean algebra	46
4.1.2 Logic gates	48
4.1.3 The TTL logic family	49
4.1.4 The CMOS family	52
4.2 Application Examples	52
4.2.1 Conversion of logic functions	52
4.2.2 Task solving by means of logic gates	53
4.2.3 Simplification with Karnaugh maps	55
4.2.4 A coded lock	57
4.3. Laboratory Projects	58
4.4. Questions and Problems.	61
5. COMBINATORIAL CIRCUITS	64
5.1 A Topic Overview	64
5.1.1 A multiplexer	64
5.1.2 A binary decoder	65
5.1.3 A 7-segment display decoder/driver	66
5.1.4 A digital adder	67
5.2 Application Examples	68
5.2.1 Logic function implementation in a multiplexer	68
5.2.2 Logic function implementation in a binary decoder	70
5.2.3 Subtraction with the full adder	72
5.3 Laboratory Projects	73
5.4 Questions and Problems	75
6. SEQUENTIAL CIRCUITS	75
6.1 A Topic Overview	75
6.1.1 An SR latch	75
6.1.2 A D-type latch	76
6.1.3 JK-, D-, T-type flip-flops.	77
6.1.4 Registers	79
6.1.5 A shift register	80
6.1.6 Counters	80
6.1.7 Memory circuits and systems	82
6.2 Application Examples	84
6.2.1 A chatterless switch.	84
6.2.2 An example of asynchronous sequential control	84
6.2.3 Designing registers with flip-flops	86
6.2.4 Designing an asynchronous counter.	87

MICROELECTRONICS (Contents)

6.2.5 Changing the counting cycle of a counter	87
6.2.6 A sequential automaton.	88
6.2.7 Programming a memory	89
6.3 Laboratory Projects	90
6.4 Questions and Problems	93
PART C: MICROPROCESSOR SYSTEMS	97
7. BASIC CONCEPTS OF MICROPROCESSOR SYSTEMS	97
7.1 A Topic Overview	97
7.1.1 Systems based on microprocessors	97
7.1.2 Microprocessors	99
7.1.3 Memory in microprocessor systems	99
7.1.4 External devices	102
7.1.5 Special types of microprocessors and	102
7.1.6 Programs	104
7.2 Application Examples	106
7.2.1 An overview of the main application fields	104
7.2.2 Personal computers	105
7.2.3 An example of a control system	107
7.2.3 Designing control systems	109
7.3. Laboratory Projects	110
7.4. Questions and Problems	112
8. MICROPROCESSOR 8086	114
8.1 A Topic Overview	114
8.1.1 Basic characteristic of the 8086 CPU	114
8.1.2 Data and addresses	115
8.1.3 Registers	116
8.1.4 Addressing modes	119
8.1.5 The 8086 instruction set	120
8.2 Application Examples	124
8.2.1 Creating programs for the 8086 processor	124
8.2.2 A starting example	125
8.2.3 Another example	126
8.2.4 Program debugging	129
8.2.5 Some other examples	130
8.3. Laboratory Projects	133
8.4. Questions and Problems	134
9. COMPUTER CONTROLLED SYSTEMS	136
9.1 A Topic Overview	136
9.1.1 A computer controlled system	136
9.1.2 Examples of sensing units	138
9.1.3 Examples of effecting units	143
9.1.4 A/D and D/A conversion	147
9.2 Application Examples	150

MICROELECTRONICS (Contents)

9.2.1	A control system based on the 8086 processor	150
9.2.2	An example of the control of output devices	151
9.2.3	An example of the communication with input devices	153
9.3.	Laboratory Projects	155
9.4.	Questions and Problems	156

APPENDICES

A.	Decimal, binary and hexadecimal numbers	159
B.	Hints for the tasks employing the E&L Instr.set	163

