

Chapter 1

Introduction 1

- 1.1 Power Electronics 1**
- 1.2 Converter Classification 1**
- 1.3 Power Electronics Concepts 3**
- 1.4 Electronic Switches 5**
 - The Diode 6*
 - Thyristors 7*
 - Transistors 8*
- 1.5 Switch Selection 11**
- 1.6 Spice, PSpice, and Capture 13**
- 1.7 Switches in Pspice 14**
 - The Voltage-Controlled Switch 14*
 - Transistors 16*
 - Diodes 17*
 - Thyristors (SCRs) 18*
 - Convergence Problems in PSpice 18*
- 1.8 Bibliography 19**
 - Problems 20**

Chapter 2

Power Computations 21

- 2.1 Introduction 21**
- 2.2 Power and Energy 21**
 - Instantaneous Power 21*
 - Energy 22*
 - Average Power 22*
- 2.3 Inductors and Capacitors 25**
- 2.4 Energy Recovery 27**

- 2.5 Effective Values: RMS 34
- 2.6 Apparent Power and Power Factor 42
 - Apparent Power S* 42
 - Power Factor* 43
- 2.7 Power Computations for Sinusoidal AC Circuits 43
- 2.8 Power Computations for Nonsinusoidal Periodic Waveforms 44
 - Fourier Series* 45
 - Average Power* 46
 - Nonsinusoidal Source and Linear Load* 46
 - Sinusoidal Source and Nonlinear Load* 48
- 2.9 Power Computations Using PSpice 51
- 2.10 Summary 58
- 2.11 Bibliography 59
- Problems 59

Chapter 3

Half-Wave Rectifiers 65

- 3.1 Introduction 65
- 3.2 Resistive Load 65
 - Creating a DC Component Using an Electronic Switch* 65
- 3.3 Resistive-Inductive Load 67
- 3.4 PSpice Simulation 72
 - Using Simulation Software for Numerical Computations* 72

- 3.5** *RL-Source Load* 75
Supplying Power to a DC Source from an AC Source 75
- 3.6** *Inductor-Source Load* 79
Using Inductance to Limit Current 79
- 3.7** *The Freewheeling Diode* 81
Creating a DC Current 81
Reducing Load Current Harmonics 86
- 3.8** *Half-Wave Rectifier With a Capacitor Filter* 88
Creating a DC Voltage from an AC Source 88
- 3.9** *The Controlled Half-Wave Rectifier* 94
Resistive Load 94
RL Load 96
RL-Source Load 98
- 3.10** *PSpice Solutions For Controlled Rectifiers* 100
Modeling the SCR in PSpice 100
- 3.11** *Commutation* 103
The Effect of Source Inductance 103
- 3.12** *Summary* 105
- 3.13** *Bibliography* 106
Problems 106

Chapter 4

Full-Wave Rectifiers 111

- 4.1** *Introduction* 111
- 4.2** *Single-Phase Full-Wave Rectifiers* 111
The Bridge Rectifier 111
The Center-Tapped Transformer Rectifier 114
Resistive Load 115
RL Load 115
Source Harmonics 118
PSpice Simulation 119
RL-Source Load 120

	<i>Capacitance Output Filter</i>	122
	<i>Voltage Doublers</i>	125
	<i>LC Filtered Output</i>	126
4.3	Controlled Full-Wave Rectifiers	131
	<i>Resistive Load</i>	131
	<i>RL Load, Discontinuous Current</i>	133
	<i>RL Load, Continuous Current</i>	135
	<i>PSpice Simulation of Controlled Full-Wave Rectifiers</i>	139
	<i>Controlled Rectifier with RL-Source Load</i>	140
	<i>Controlled Single-Phase Converter Operating as an Inverter</i>	142
4.4	Three-Phase Rectifiers	144
4.5	Controlled Three-Phase Rectifiers	149
	<i>Twelve-Pulse Rectifiers</i>	151
	<i>The Three-Phase Converter Operating as an Inverter</i>	154
4.6	DC Power Transmission	156
4.7	Commutation: The Effect of Source Inductance	160
	<i>Single-Phase Bridge Rectifier</i>	160
	<i>Three-Phase Rectifier</i>	162
4.8	Summary	163
4.9	Bibliography	164
	Problems	164

Chapter 5

AC Voltage Controllers 171

5.1	Introduction	171
5.2	The Single-Phase AC Voltage Controller	171
	<i>Basic Operation</i>	171
	<i>Single-Phase Controller with a Resistive Load</i>	173
	<i>Single-Phase Controller with an RL Load</i>	177
	<i>PSpice Simulation of Single-Phase AC Voltage Controllers</i>	180

- 5.3 Three-Phase Voltage Controllers 183
 - Y-Connected Resistive Load* 183
 - Y-Connected RL Load* 187
 - Delta-Connected Resistive Load* 189
- 5.4 Induction Motor Speed Control 191
- 5.5 Static VAR Control 191
- 5.6 Summary 192
- 5.7 Bibliography 193
 - Problems 193

Chapter 6

DC-DC Converters 196

- 6.1 Linear Voltage Regulators 196
- 6.2 A Basic Switching Converter 197
- 6.3 The Buck (Step-Down) Converter 198
 - Voltage and Current Relationships* 198
 - Output Voltage Ripple* 204
 - Capacitor Resistance—The Effect on Ripple Voltage* 206
 - Synchronous Rectification for the Buck Converter* 207
- 6.4 Design Considerations 207
- 6.5 The Boost Converter 211
 - Voltage and Current Relationships* 211
 - Output Voltage Ripple* 215
 - Inductor Resistance* 218
- 6.6 The Buck-Boost Converter 221
 - Voltage and Current Relationships* 221
 - Output Voltage Ripple* 225
- 6.7 The Ćuk Converter 226
- 6.8 The Single-Ended Primary Inductance Converter (SEPIC) 231
- 6.9 Interleaved Converters 237
- 6.10 Nonideal Switches and Converter Performance 239
 - Switch Voltage Drops* 239
 - Switching Losses* 240

- 6.11 Discontinuous-Current Operation** 241
 - Buck Converter with Discontinuous Current* 241
 - Boost Converter with Discontinuous Current* 244
- 6.12 Switched-Capacitor Converters** 247
 - The Step-Up Switched-Capacitor Converter* 247
 - The Inverting Switched-Capacitor Converter* 249
 - The Step-Down Switched-Capacitor Converter* 250
- 6.13 PSpice Simulation of DC-DC Converters** 251
 - A Switched PSpice Model* 252
 - An Averaged Circuit Model* 254
- 6.14 Summary** 259
- 6.15 Bibliography** 259
 - Problems** 260

Chapter 7

DC Power Supplies 265

- 7.1 Introduction** 265
- 7.2 Transformer Models** 265
- 7.3 The Flyback Converter** 267
 - Continuous-Current Mode* 267
 - Discontinuous-Current Mode in the Flyback Converter* 275
 - Summary of Flyback Converter Operation* 277
- 7.4 The Forward Converter** 277
 - Summary of Forward Converter Operation* 283
- 7.5 The Double-Ended (Two-Switch) Forward Converter** 285
- 7.6 The Push-Pull Converter** 287
 - Summary of Push-Pull Operation* 290
- 7.7 Full-Bridge and Half-Bridge DC-DC Converters** 291

7.8	Current-Fed Converters	294
7.9	Multiple Outputs	297
7.10	Converter Selection	298
7.11	Power Factor Correction	299
7.12	PSpice Simulation of DC Power Supplies	301
7.13	Power Supply Control	302
	<i>Control Loop Stability</i>	303
	<i>Small-Signal Analysis</i>	304
	<i>Switch Transfer Function</i>	305
	<i>Filter Transfer Function</i>	306
	<i>Pulse-Width Modulation Transfer Function</i>	307
	<i>Type 2 Error Amplifier with Compensation</i>	308
	<i>Design of a Type 2 Compensated Error Amplifier</i>	311
	<i>PSpice Simulation of Feedback Control</i>	315
	<i>Type 3 Error Amplifier with Compensation</i>	317
	<i>Design of a Type 3 Compensated Error Amplifier</i>	318
	<i>Manual Placement of Poles and Zeros in the Type 3 Amplifier</i>	323
7.14	PWM Control Circuits	323
7.15	The AC Line Filter	323
7.16	The Complete DC Power Supply	325
7.17	Bibliography	326
	Problems	327

Chapter 8

Inverters 331

8.1	Introduction	331
8.2	The Full-Bridge Converter	331
8.3	The Square-Wave Inverter	333
8.4	Fourier Series Analysis	337
8.5	Total Harmonic Distortion	339
8.6	PSpice Simulation of Square Wave Inverters	340

- 8.7 Amplitude and Harmonic Control 342
- 8.8 The Half-Bridge Inverter 346
- 8.9 Multilevel Inverters 348
 - Multilevel Converters with Independent DC Sources* 349
 - Equalizing Average Source Power with Pattern Swapping* 353
 - Diode-Clamped Multilevel Inverters* 354
- 8.10 Pulse-Width-Modulated Output 357
 - Bipolar Switching* 357
 - Unipolar Switching* 358
- 8.11 PWM Definitions and Considerations 359
- 8.12 PWM Harmonics 361
 - Bipolar Switching* 361
 - Unipolar Switching* 365
- 8.13 Class D Audio Amplifiers 366
- 8.14 Simulation of Pulse-Width-Modulated Inverters 367
 - Bipolar PWM* 367
 - Unipolar PWM* 370
- 8.15 Three-Phase Inverters 373
 - The Six-Step Inverter* 373
 - PWM Three-Phase Inverters* 376
 - Multilevel Three-Phase Inverters* 378
- 8.16 PSpice Simulation of Three-Phase Inverters 378
 - Six-Step Three-Phase Inverters* 378
 - PWM Three-Phase Inverters* 378
- 8.17 Induction Motor Speed Control 379
- 8.18 Summary 382
- 8.19 Bibliography 383
 - Problems 383

Chapter 9

Resonant Converters 387

- 9.1** Introduction 387
- 9.2** A Resonant Switch Converter:
Zero-Current Switching 387
 - Basic Operation* 387
 - Output Voltage* 392
- 9.3** A Resonant Switch Converter:
Zero-Voltage Switching 394
 - Basic Operation* 394
 - Output Voltage* 399
- 9.4** The Series Resonant Inverter 401
 - Switching Losses* 403
 - Amplitude Control* 404
- 9.5** The Series Resonant
DC-DC Converter 407
 - Basic Operation* 407
 - Operation for $\omega_s > \omega_o$* 407
 - Operation for $\omega_o/2 < \omega_s < \omega_o$* 413
 - Operation for $\omega_s < \omega_o/2$* 413
 - Variations on the Series Resonant DC-DC Converter* 414
- 9.6** The Parallel Resonant
DC-DC Converter 415
- 9.7** The Series-Parallel DC-DC
Converter 418
- 9.8** Resonant Converter Comparison 421
- 9.9** The Resonant DC Link Converter 422
- 9.10** Summary 426
- 9.11** Bibliography 426
 - Problems 427

Chapter 10

Drive Circuits, Snubber Circuits, and Heat Sinks 431

- 10.1** Introduction 431
- 10.2** MOSFET and IGBT Drive Circuits 431
 - Low-Side Drivers 431*
 - High-Side Drivers 433*
- 10.3** Bipolar Transistor Drive Circuits 437
- 10.4** Thyristor Drive Circuits 440
- 10.5** Transistor Snubber Circuits 441
- 10.6** Energy Recovery Snubber Circuits 450
- 10.7** Thyristor Snubber Circuits 450
- 10.8** Heat Sinks and Thermal Management 451
 - Steady-State Temperatures 451*
 - Time-Varying Temperatures 454*
- 10.9** Summary 457
- 10.10** Bibliography 457
 - Problems 458

Appendix A Fourier Series for Some Common Waveforms 461

Appendix B State-Space Averaging 467

Index 473