

Table of Contents

About the Author	xix
About the Technical Reviewer	xxi
Acknowledgments	xxiii
Chapter 1: Introduction.....	1
1.1 Working the Examples	2
1.2 Initial Tools and Supplies	3
1.3 Safety Guidelines	5
1.4 Electrostatic Discharge	7
1.5 Using Your Multimeter Correctly	7
Chapter 2: Dealing with Units	9
2.1 SI Units.....	9
2.2 Scaling Units	12
2.3 Using Abbreviations	14
2.4 Significant Figures	15
Apply What You Have Learned.....	18
Part I: Basic Concepts	21
Chapter 3: What Is Electricity?	23
3.1 Charge.....	23
3.2 Measuring Charge and Current.....	26
3.3 AC vs. DC.....	28

TABLE OF CONTENTS

3.4 Which Way Does Current Flow?	30
Review	31
Apply What You Have Learned.....	32
Chapter 4: Voltage and Resistance	35
4.1 Picturing Voltage	35
4.2 Volts Are Relative	36
4.3 Relative Voltages and Ground Potential	37
4.4 Resistance	38
Review	41
Apply What You Have Learned.....	42
Chapter 5: Your First Circuit	45
5.1 Circuit Requirements	45
5.2 Basic Components	47
5.3 Creating Your First Circuit	49
5.4 Adding Wires	52
5.5 Drawing Circuits.....	53
5.6 Drawing the Ground	56
Review	57
Apply What You Have Learned.....	58
Chapter 6: Constructing and Testing Circuits	61
6.1 The Solderless Breadboard	61
6.2 Putting a Circuit onto a Breadboard.....	64
6.3 Using Fewer Wires	69
6.4 Testing Circuits with a Multimeter	72
6.5 Using a Multimeter with a Breadboard	75
6.6 Measuring Current with a Multimeter	77

6.7 Using a Power Regulator.....	78
Review	80
Apply What You Have Learned.....	83
Chapter 7: Analyzing Series and Parallel Circuits	85
7.1 Series Circuits.....	85
7.2 Parallel Circuits.....	87
7.2.1 Kirchhoff's Current Law	88
7.2.2 Kirchhoff's Voltage Law	90
7.3 Equivalent Parallel Resistance	93
7.4 Wires in a Circuit.....	97
7.5 Wiring Parallel Circuits onto a Breadboard	99
Review	100
Apply What You Have Learned.....	102
Chapter 8: Diodes and How to Use Them.....	105
8.1 Basic Diode Behavior	105
8.2 Circuit Calculations with Diodes in Series	107
8.3 Circuit Calculations with Diodes in Parallel	109
8.4 Diode Short Circuits	113
8.5 Nonconducting Diodes	115
8.6 Usage of Diodes	115
8.7 Other Types of Diode Protection.....	120
8.8 Zener Diodes	122
8.9 Schottky Diode	123
8.10 Diode-Like Behavior in Other Components	123
Review	123
Apply What You Have Learned.....	126

Chapter 9: Basic Resistor Circuit Patterns	129
9.1 Switches and Buttons	129
9.2 Current-Limiting Resistor Pattern	131
9.3 Voltage Divider Pattern	132
9.3.1 Calculating the Voltages	134
9.3.2 Finding Resistor Ratios.....	135
9.3.3 Finding Resistor Values	136
9.3.4 General Considerations	138
9.4 The Pull-Up Resistor.....	138
9.5 Pull-Down Resistors.....	141
Review	141
Apply What You Have Learned.....	143
Chapter 10: Understanding Power	145
10.1 Important Terms Related to Power.....	145
10.2 Power in Electronics	147
10.3 Component Power Limitations	149
10.4 Handling Power Dissipation with Heatsinks	150
10.5 Transforming Power	151
10.6 Amplifying Low-Power Signals	153
Review	154
Apply What You Have Learned.....	156
Chapter 11: Integrated Circuits and Resistive Sensors	159
11.1 The Parts of an Integrated Circuit	159
11.2 The LM393 Voltage Comparator	163
11.3 The Importance and Problems of Datasheets	164
11.4 A Simple Circuit with the LM393.....	167

11.5 Resistive Sensors and Voltages	169
11.6 Sensing and Reacting to Darkness	170
Sources and Sinks	172
Review	173
Apply What You Have Learned.....	175
Part II: Digital Electronics and Microcontrollers	177
Chapter 12: Using Logic ICs.....	179
12.1 Logic ICs.....	179
12.2 Getting a 5 V Source.....	185
12.3 Pull-Down Resistors.....	187
12.4 Combining Logic Circuits	190
12.5 Understanding Chip Names	193
Review	196
Apply What You Have Learned.....	197
Chapter 13: Introduction to Microcontrollers	201
13.1 The ATmega328/P Chip	203
13.2 The Arduino Environment	204
13.3 The Arduino Uno	206
13.4 Programming the Arduino	207
Review	210
Apply What You Have Learned.....	211
Chapter 14: Building Projects with Arduino	213
14.1 Powering Your Breadboard from an Arduino Uno.....	213
14.2 Wiring Inputs and Outputs to an Arduino Uno	214
14.3 A Simple Arduino Project with LEDs.....	216

TABLE OF CONTENTS

14.4 Changing Functionality Without Rewiring	219
Review	220
Apply What You Have Learned.....	221
Chapter 15: Analog Input and Output on an Arduino	223
15.1 Reading Analog Inputs	223
15.2 Analog Output with PWM	226
Review	229
Apply What You Have Learned.....	231
Part III: Capacitors and Inductors.....	233
Chapter 16: Capacitors	235
16.1 What Is a Capacitor?	235
16.2 How Capacitors Work.....	237
16.3 Types of Capacitors	241
16.4 Charging and Discharging a Capacitor.....	243
16.5 Series and Parallel Capacitances.....	245
16.6 Capacitors and AC and DC	248
16.7 Using Capacitors in a Circuit.....	249
Review	251
Exercises.....	253
Chapter 17: Capacitors as Timers	255
17.1 Time Constants	255
17.2 Constructing a Simple Timer Circuit	258
17.3 Resetting Our Timer	263
Review	265
Apply What You Have Learned.....	267

Chapter 18: Introduction to Oscillator Circuits.....	269
18.1 Oscillation Basics.....	269
18.2 The Importance of Oscillating Circuits	271
18.3 Building an Oscillator.....	273
18.4 Calculating On and Off Times with the 555.....	279
18.5 Choosing the Capacitor	283
Review	284
Apply What You Have Learned.....	287
Chapter 19: Producing Sound with Oscillations	289
19.1 How Sound Is Produced by Speakers	289
19.2 Graphing Electricity.....	290
19.3 Outputting a Tone to Headphones	292
19.4 AC vs. DC.....	294
19.5 Using Capacitors to Separate AC and DC Components	295
19.6 Speaker Wattage.....	297
19.7 Sound Control	298
Review	300
Apply What You Have Learned.....	302
Chapter 20: Inductors.....	303
20.1 Inductors, Coils, and Magnetic Flux	303
20.1.1 What Is an Inductor?.....	303
20.1.2 What Is Magnetic Flux?	304
20.1.3 What Is the Difference Between Electric and Magnetic Fields.....	304
20.2 Induced Voltages.....	306
20.3 Resisting Changes in Current.....	307
20.4 Analogy from Mechanics.....	308

TABLE OF CONTENTS

20.5 Uses of Inductors	308
20.6 Inductive Kick.....	309
Review	311
Apply What You Have Learned.....	312
Chapter 21: Inductors and Capacitors in Circuits.....	315
21.1 RL Circuits and Time Constants	315
21.2 Inductors and Capacitors as Filters	317
21.3 Parallel and Series Capacitors and Inductors	318
Review	319
Apply What You Have Learned.....	320
Chapter 22: Reactance and Impedance	323
22.1 Reactance	323
22.2 Impedance	326
22.3 RLC Circuits.....	329
22.4 Ohm's Law for AC Circuits.....	331
22.5 Resonant Frequencies of RLC Circuits	334
22.6 Low-Pass Filters	335
22.7 Converting a PWM Signal into a Voltage	336
Review	337
Exercises.....	339
Chapter 23: DC Motors.....	343
23.1 Theory of Operation.....	343
23.2 Important Facts About Motors.....	344
23.3 Using a Motor in a Circuit.....	345
23.4 Attaching Things to Motors	347

23.5 Bidirectional Motors	348
23.6 Servo Motors.....	349
23.7 Stepper Motors	350
Review	350
Apply What You Have Learned.....	352
Part IV: Amplification Circuits	353
Chapter 24: Amplifying Power with Transistors	355
24.1 An Amplification Parable	356
24.2 Amplifying with Transistors.....	357
24.3 Parts of the BJT	358
24.4 NPN Transistor Operation Basics.....	361
Rule 1: The Transistor Is Off by Default.....	361
Rule 2: V_{BE} Needs to Be 0.6 V to Turn the Transistor On	361
Rule 3: V_{BE} Will Always Be Exactly 0.6 V When the Transistor Is On	361
Rule 4: The Collector Should Always Be More Positive Than the Emitter	362
Rule 5: When the Transistor Is On, I_{CE} Is a Linear Amplification of I_{BE}	362
Rule 6: The Transistor Cannot Amplify More Than the Collector Can Supply	362
Rule 7: If the Base Voltage Is Greater Than the Collector Voltage, the Transistor Is Saturated.....	363
24.5 The Transistor as a Switch	364
24.6 Connecting a Transistor to an Arduino Output.....	367
24.7 Stabilizing Transistor Beta With a Feedback Resistor	368
24.8 A Word of Caution.....	370
Review	370
Apply What You Have Learned.....	372

Chapter 25: Transistor Voltage Amplifiers.....	375
25.1 Converting Current into Voltage with Ohm's Law.....	375
25.2 Reading the Amplified Signal.....	378
25.3 Amplifying an Audio Signal	380
25.4 Adding a Second Stage.....	385
25.5 Using an Oscilloscope.....	387
Review	388
Apply What You Have Learned.....	390
Chapter 26: Examining Partial Circuits.....	391
26.1 The Need for a Model.....	391
26.2 Calculating Thévenin Equivalent Values.....	393
26.3 Another Way of Calculating Thévenin Resistance	396
26.4 Finding the Thévenin Equivalent of an AC Circuit with Reactive Elements	397
26.5 Using Thévenin Equivalent Descriptions	398
26.6 Finding Thévenin Equivalent Circuits Experimentally	399
Review	403
Apply What You Have Learned.....	404
Chapter 27: Using Field Effect Transistors for Switching and Logic Applications	407
27.1 Operation of a FET.....	408
27.2 The N-Channel Enhancement Mode MOSFET	410
27.3 Using a MOSFET.....	410
27.4 MOSFETs in Logic Circuits	414
Review	415
Apply What You Have Learned.....	416

Chapter 28: Going Further	417
Appendix A: Glossary	419
Appendix B: Electronics Symbols	435
Appendix C: Integrated Circuit Naming Conventions	439
C.1 Logic Chip Basic Conventions	439
Appendix D: More Math Than You Wanted to Know	443
D.1 Basic Formulas	443
D.1.1 Charge and Current Quantities	443
D.1.2 Volt Quantities	444
D.1.3 Resistance and Conductance Quantities	444
D.1.4 Ohm's Law	445
D.1.5 Power	445
D.1.6 Capacitance	445
D.1.7 Inductance	446
D.2 Semiconductors	447
D.2.1 Diodes	447
D.2.2 NPN BJT	448
D.3 DC Motor Calculations	448
D.4 555 Timer Oscillator Frequency Equation	450
D.5 Output Gain Calculations in BJT Common Emitter Applications	452
D.6 The Thévenin Formula	461
D.7 Electronics and Calculus	463
D.7.1 Current and Voltage	463
D.7.2 Capacitors and Inductors	464
D.7.3 Time Constants	465

Appendix E: Simplified Datasheets for Common Devices	467
E.1 Batteries.....	468
E.1.1 Overview.....	468
E.1.2 Variations.....	468
E.1.3 Notes	469
E.2 Resistors	469
E.2.1 Overview.....	469
E.2.2 Finding a Resistor Value	470
E.3 Diodes	471
E.3.1 Overview.....	471
E.3.1 Variations.....	472
E.3.3 Forward Voltage Drop	472
E.3.4 Usages.....	473
E.4 Capacitors	473
E.4.1 Overview.....	473
E.4.2 Variations.....	474
E.4.3 Finding Capacitance Values.....	475
E.5 Inductors	475
E.5.1 Overview.....	475
E.5.2 Uses.....	476
E.5.3 Inductive Kick	476
E.5.4 Inductor Color Codes	477
E.6 NPN BJTs	477
E.6.1 Overview.....	477
E.6.2 Variations.....	478
E.6.3 Pin Configuration	478
E.6.4 Design Considerations.....	479

E.7 YwRobot Power Module	479
E.7.1 Overview.....	479
E.7.2 Variations.....	480
E.7.3 Pin Configuration	480
E.7.4 Limitations.....	480
E.8 555 Timer	481
E.8.1 Overview.....	481
E.8.2 Variations.....	482
E.8.3 Pin Configuration	482
E.8.4 Specifications	483
E.8.5 Implementation Example.....	483
E.9 LM393 and LM339 Voltage Comparator	483
E.9.1 Overview.....	483
E.9.2 Variations.....	484
E.9.3 Specifications	484
E.10 CD4081 and 7408 Quad-AND Gate.....	485
E.10.1 Overview.....	485
E.10.2 Variations.....	485
E.10.3 Specifications (CD4081)	486
E.10.4 Specifications (7408).....	486
E.11 CD4071 and 7432 Quad-OR Gate	487
E.11.1 Overview.....	487
E.11.2 Variations.....	487
E.11.3 Specifications (CD4071)	488
E.11.4 Specifications (7432).....	488

TABLE OF CONTENTS

E.12 CD4001 and 7402 Quad-NOR Gate.....	489
E.12.1 Overview.....	489
E.12.2 Variations.....	489
E.12.3 Specifications (CD4001)	490
E.12.4 Specifications (7402).....	490
E.13 CD4011 and 7400 Quad-NAND Gate	491
E.13.1 Overview.....	491
E.13.2 Variations.....	491
E.13.3 Specifications (CD4011)	492
E.13.4 Specifications (7400).....	492
E.14 CD4070 and 7486 Quad-XOR Gate.....	493
E.14.1 Overview.....	493
E.14.2 Variations.....	493
E.14.3 Specifications (CD4070)	494
E.14.4 Specifications (7486).....	494
E.15 LM78xx Voltage Regulator	495
E.15.1 Overview.....	495
E.15.2 Variations.....	495
E.15.3 Specifications	496
E.15.4 Usage Notes	497
Index.....	499