

Contents

0.1	Preface	7
0.2	References	8
1	Electrostatics	9
1.1	Electric Charge	9
1.2	Electric field	12
1.3	Electric Field of an Electric Charge	17
1.4	Electric field in a material	18
1.4.1	Conductors	18
1.4.2	Insulators	20
1.5	Capacitance	22
1.5.1	Parallel Connection	23
1.5.2	Series Connection	24
1.5.3	Capacitance of a Plane Capacitor	26
1.6	Energy Density	28
1.7	Force Density on Charged Plates	30
1.8	Dielectric Strength	31
2	Direct Electric Current	33
2.1	Electric Current	33
2.2	Electromotive Force (E.M.F.)	35
2.3	Resistance	37

2.4	Ohm's Law	41
2.5	Electric Power and Energy	42
2.6	Series and parallel Circuits	44
2.6.1	Series Circuit	44
2.6.2	Parallel Circuit	47
2.6.3	Open-circuit and Short-circuit	50
2.6.4	Series-Parallel Circuit	51
2.7	Kirchhoff's Laws	52
2.7.1	Current Law	53
2.7.2	Voltage Law	54
2.7.3	The Branch Current Method	56
2.7.4	Real Source of Electric Energy	58
3	Magnetostatics	61
3.1	Magnetic Field	61
3.2	Magnetic Field of an Electric Current	64
3.3	Force Acting on a Current	69
3.4	Magnetic Field in Material	73
3.5	Magnetomotive Force, m.m.f.	77
3.6	Magnetic Circuit	79
3.6.1	Reluctance	80
3.6.2	Kirchoff's Laws in a Magnetic Circuit	82
3.6.3	Magnetic Leakage and Fringing	84
3.6.4	Examples	85
3.6.5	Some Remarks to the Magnetic Circuit	95
3.7	Forces in a Magnetic Field	97
3.8	Comparison of electric and magnetic effects	99
4	Electrodynamics	101
4.1	Electromagnetic Induction	101

4.1.1	Conductor Moving in Magnetic Field	102
4.1.2	Coil in Magnetic Field	104
4.1.3	Coupled Coils	106
4.2	Inductive Elements	107
4.3	Inductance	109
4.3.1	Definition	109
4.3.2	Inductance as a Circuit Element	111
4.4	Inductance of a Coil	113
4.4.1	Ferromagnetic Core	114
4.4.2	Magnetic Energy of a Coil	118
4.5	Mutual Inductance	119
4.5.1	Definition	121
4.5.2	Magnetic Energy in Coupled Coils	124
4.5.3	Coupling Coefficient	126
4.5.4	Mutual Inductance as a Circuit Element	127
4.5.5	Coupled Coils Connected in Series	128
4.6	Current in Capacitor	130
5	Transition Effects	134
5.1	Inductance and Resistance	136
5.1.1	Switching Current on	136
5.1.2	Switching Current off	138
5.2	Capacitance and Resistance	140
5.2.1	Charging the Capacitor	140
5.2.2	Discharging the Capacitor	142
5.3	Time Constants	143
5.4	Series Connected Inductance and Capacitance	144
6	Alternating Current	148
6.1	Basic Properties of an Alternating Current	148

6.1.1	Generation of Harmonic A.C.	149
6.1.2	Mean and Effective Value	151
6.2	Phasors	155
6.2.1	Definition	155
6.2.2	Addition and Subtraction of Phasors	157
6.3	Basic Elements in A.C. Circuit	160
6.3.1	Resistance	160
6.3.2	Inductance	160
6.3.3	Capacitance	165
6.3.4	Real Inductance	168
6.3.5	Comparison	171
6.4	Power in A.C. Circuit	171
6.4.1	Basic Circuit Elements	172
6.4.2	General Load	175
6.4.3	Power Factor	180
6.5	Use of Complex Calculus	182
6.5.1	Operation over Complex Numbers	183
6.5.2	Complex Phasor	186
6.5.3	Complex Ohm's Law	187
6.5.4	Impedance and Admittance	190
6.5.5	Solution of A.C. Circuit	193
6.5.6	Complex power	195
6.6	Resonant Circuit	196
6.6.1	Series Resonant Circuit	196
6.6.2	Parallel Resonant Circuit	200
6.6.3	Comparison of Resonant Circuits	202
7	Important A.C. Circuits	204
7.1	Three-Phase Circuits	204

7.1.1	Generation of Three-Phase E.M.F.	205
7.1.2	Delta and Star Connection	206
7.1.3	Relation Between Line and Phase Quantities . . .	209
7.1.4	Power in Three-Phase System	216
7.2	Two-ports	217
7.2.1	Circuit Properties of Two-Ports	217
7.2.2	Two-Port Transmission Properties	224
7.2.3	Connection of Two-ports	224
7.3	Electrical-Mechanical Analogy	226
8	Transformers	229
8.1	Principle of Action	230
8.2	Ideal Transformer	232
8.3	Transformer of no Load	235
8.4	Transformer with Load	240
8.5	Equivalent Circuit	242
8.6	Efficiency of Transformer	247
8.7	Measurement of Transformer	250
8.8	Use of Transformer	253
9	Alternating Current Machines	255
9.1	Construction	256
9.2	Induced E.M.F.	262
9.2.1	Distributed Winding	263
9.2.2	Short-Pitch Winding	265
9.2.3	General Formula for Induced E.M.F.	266
9.3	Rotating Magnetic Field	267
9.4	Synchronous Generator	268
9.4.1	Influence of the Load	269
9.4.2	Voltage Regulation	271

9.5	Synchronous Generator in the Net	277
9.5.1	Synchronization	277
9.5.2	Interaction with Net	278
9.6	Synchronous Motor	281
9.7	Induction Motor	285
9.7.1	Principle	285
9.7.2	Rotor Induced E.M.F.	289
9.7.3	Torque	293
9.7.4	Starting the Induction Motors	299
9.7.5	Equivalent Circuit of Induction Motor	301
10	Direct Current Machines	303
10.1	Construction	303
10.2	Induced Voltage	308
10.3	Armature Reaction	309
10.4	Commutation	314
10.4.1	Linear Commutation	314
10.4.2	Nonlinear Commutation	316
10.4.3	Methods of Improving Commutation	317
10.5	D.C. Machine as a Motor or Generator	320
10.6	Motors	325
10.6.1	Starting	326
10.6.2	Speed Characteristics and Control	328
10.6.3	Torque Characteristics	333
10.7	Generators	336
10.8	Efficiency of D.C. Machines	339
11	Semiconductors	342
11.1	Intrinsic Semiconductor	342
11.2	Doped Semiconductors	344

CONTENTS

6-1

11.2.1 N-type semiconductor	344
11.2.2 P-type semiconductor	346
11.2.3 Comparison	349
11.3 P-N Junction	349
11.4 Junction Diode	353
11.5 Rectifiers	354
11.5.1 Half-Wave Rectifier	355
11.5.2 Full-Wave Rectifier	357
11.5.3 Three-Phase Rectifier	359
11.6 Smoothing	360
11.7 Zener Diode	363
11.8 Thyristor	364
11.8.1 Principle of Thyristor	364
11.8.2 Use of Thyristor	367