

Table of Contents

CHAPTER 1: INTRODUCTION	10
1.1 Author's Background	11
1.2 Expected Level of the Reader	12
1.3 Reader Hardware	13
1.4 Microcontroller vs Microprocessor (or Why Arduino?)	14
1.5 Standard Data Logger	15
1.6 Extra Details	16
CHAPTER 2: THE ADC	17
2.1 Flash Converter	17
2.2 Successive Approximation Converter, SAC	19
2.3 Sigma Delta Converter	20
CHAPTER 3: CALIBRATING THE ARDUINO UNO	23
3.1 Basic Operation of the Arduino ADC	23
3.2 Summing ADC Readings	25
3.3 Calibration of the Uno	27

3.4 Other Vref Options	31
3.5 More Thoughts on System Calibration	33
3.5.1 To Marry or Not to Marry?	33
3.5.2 Closed Loop Calibration	34
3.5.1 Accuracy vs Resolution	35
CHAPTER 4: INTERFACING SIGNALS TO THE ARDUINO	37
4.1 Simple Voltage Divider for Input Voltages > the Arduino Supply Voltage	37
4.1.1 Adding a Capacitor to the Voltage Divider	39
4.1.2 Adding Diodes to the Voltage Divider	43
4.2 Coupling ac Voltage Signals to the Arduino	44
4.3 Current Loop (Constant Current) Sensor Interface	47
4.4 The Operational Amplifier (Op-Amp)	50
4.4.1 Non-Inverting Op-Amp Circuit	51
4.4.2 The Inverting Op-Amp Circuit	52
4.4.3 Input Offset Voltage	53
4.4.4 Input Bias Current	54
4.4.5 Rail-to-Rail	55
4.5 Instrumentation Amplifiers	55
4.5.1 Reference Voltage, Vref	59
4.6 Measurement Circuit Temperature Drift	61
4.7 DC Amplifier Circuit Examples	64
4.7.1. Example: Op-Amp Thermistor Measurement	64
4.7.2 Example: In-Amp Thermistor Measurement	68
4.7.3 Wheatstone Bridge and In-Amp	70
4.8. Choosing Passive Components	73
4.9 Running On Batteries	75
CHAPTER 5: RECORDING DYNAMIC SIGNALS	77
5.1 Digital Sampling with the Arduino	77
5.1.1 Recording Sensor Data	78
5.1.2 Sampling Data at a Constant Rate	80

5.2 Saving to an External Memory	87
5.2.1 Saving Data to the SD Card	87
5.2.2 Saving to SRAM (Building an Arduino Scope)	89
5.2.3 Saving Your Data to the PC	92
5.3 Nyquist Frequency and Aliasing	93
5.3.1 Oversampling and Nyquist	97
5.4 Understanding Analog Signals	100
5.4.1 Signal Peak to Peak Amplitude?	101
5.4.2 Bandwidth?	101
5.4.3 What portion of the incoming signal contains the information?	104
5.4.4 What is the driving impedance?	105
CHAPTER 6 ANALOG ANTI-ALIASING FILTERS	107
6.1 Active Analog Filters	107
6.1.1 Working in dB	111
6.2 A CAD Designed AA Filter	114
6.2.1 CAD Active Analog Filters and Arduino	115
6.3 Simple Anti-Aliasing Filters Using only a Calculator	116
6.3.1 The Mighty RC Filter	116
6.3.2 Building Anti-Aliasing Filters into Signal Conditioning Amplifiers	120
6.3.3 Simulated Real World AA Filter Example with an In-Amp	123
6.4 The Bessel Filter and IC Filters	126
6.5 ADC Quantization Levels and Nyquist Frequency	128
6.6 Converting Arduino 10Bit ADC to 13Bit ADC	130
6.7 The Arduino AD22B High Resolution Shield	134
6.8 The Arduino DAC12B Shield	135
CHAPTER 7 DIGITAL FILTERS	139
7.1 Digital Filters	139
7.1.1 Is it real?	139
7.3 The Dreaded Moving Average	143

7.4 The IIR Filter	149
7.4.1 Low Pass IIR Butterworth Filter	150
7.4.2 One Pole, Low Pass IIR Filter	151
7.4.3 Two Pole, Low Pass IIR Filter	153
7.4.4 Three Pole, Low Pass IIR Filter	157
7.5 Time Shifting the IIR LP Filter	161
7.6 High Pass IIR Filters	163
7.6.1 One Pole High Pass IIR Filter	164
7.6.2 Two Pole High Pass IIR Filter	164
7.7 Band Pass Butterworth IIR Filter	166
7.8 The Median Digital Filter	169
CHAPTER 8 PLOTTING YOUR MEASUREMENTS	173
8.1 Some Good and Bad Examples	173
8.2 Correlation Between Two Measurements	175
CHAPTER 9 REDUCING ELECTRONIC NOISE	177
9.1 Arduino Power Supply	177
9.2 Conductively Coupled Noise	178
9.2.1 Noisy Supply Voltage (V_{sup})	179
9.2.2 Impedance: Keeping it Low to Reduce Noise	184
9.3 Wireless Coupled Noise	190
9.3.1 Capacitive Coupled Noise	191
9.3.2 Magnetic Coupled Noise	194
9.3.3 RF Coupled Noise	196
9.4 Found Noise on the Signal?	197
9.5 Concluding Notes on Reducing Noise	199
CHAPTER 10 PROGRAMMING EXAMPLES	201
10.1 Auto-Ranging the Mega	201
10.1.1 Test Circuit	205

10.1.2 MegaAutoRange Sketch -----	205
10.2 SD_Logger -----	210
10.2.1 Test Circuit -----	211
10.2.3 SD_Logger Sketch -----	212
10.3 SRAM Scope2 Sketch -----	215
10.3.1 Test circuit -----	218
10.3.2 SRAM_Scope2 Sketch -----	219
10.4 Saving to a PC w RTC -----	223
10.4.1 Test Setup -----	225
10.4.2 RTC_Rev5 -----	225
10.5 AD22B and DAC12B Sketch -----	232
10.5.1 Test Circuit -----	233
10.5.2 AD22B_DAC12B_Test Sketch -----	235
10.6 SRAM Low Pass Butterworth -----	241
10.6.1 Test Circuit -----	242
10.6.2 SRAM_LP Sketch -----	242
INDEX -----	247
OH YEA, I WAS RIGHT SHEET -----	251