

Contents

Preface ix

Chapter 1 Introduction 2

1-1	Approximations	1-5	Norton's Theorem
1-2	Voltage Sources	1-6	DC Circuit Troubleshooting
1-3	Current Sources	1-7	AC Circuit Troubleshooting
1-4	Thevenin's Theorem		

Chapter 2 Semiconductors 30

2-1	Conductors	2-8	The Unbiased Diode
2-2	Semiconductors	2-9	Forward Bias
2-3	Silicon Crystals	2-10	Reverse Bias
2-4	Intrinsic Semiconductors	2-11	Breakdown
2-5	Two Types of Flow	2-12	Energy Levels
2-6	Doping a Semiconductor	2-13	Barrier Potential and Temperature
2-7	Two Types of Extrinsic Semiconductors	2-14	Reverse-Biased Diode

Chapter 3 Diode Theory 58

3-1	Basic Ideas	3-7	How to Calculate Bulk Resistance
3-2	The Ideal Diode	3-8	DC Resistance of a Diode
3-3	The Second Approximation	3-9	Load Lines
3-4	The Third Approximation	3-10	Surface-Mount Diodes
3-5	Troubleshooting	3-11	Introduction to Electronic Systems
3-6	Reading a Data Sheet		

Chapter 4 Diode Circuits 88

4-1	The Half-Wave Rectifier	4-7	Peak Inverse Voltage and Surge Current
4-2	The Transformer	4-8	Other Power-Supply Topics
4-3	The Full-Wave Rectifier	4-9	Troubleshooting
4-4	The Bridge Rectifier	4-10	Clippers and Limiters
4-5	The Choke-Input Filter	4-11	Clampers
4-6	The Capacitor-Input Filter	4-12	Voltage Multipliers

Chapter 5 Special-Purpose Diodes 142

5-1	The Zener Diode	5-7	Load Lines
5-2	The Loaded Zener Regulator	5-8	Light-Emitting Diodes (LEDs)
5-3	Second Approximation of a Zener Diode	5-9	Other Optoelectronic Devices
5-4	Zener Drop-Out Point	5-10	The Schottky Diode
5-5	Reading a Data Sheet	5-11	The Varactor
5-6	Troubleshooting	5-12	Other Diodes

Chapter 6 BJT Fundamentals 190

6-1	The Unbiased Transistor	6-9	Surface-Mount Transistors
6-2	The Biased Transistor	6-10	Variations in Current Gain
6-3	Transistor Currents	6-11	The Load Line
6-4	The CE Connection	6-12	The Operating Point
6-5	The Base Curve	6-13	Recognizing Saturation
6-6	Collector Curves	6-14	The Transistor Switch
6-7	Transistor Approximations	6-15	Troubleshooting
6-8	Reading Data Sheets		

Chapter 7 BJT Biasing 242

7-1	Emitter Bias	7-6	Accurate VDB Analysis
7-2	LED Drivers	7-7	VDB Load Line and Q Point
7-3	Troubleshooting Emitter Bias Circuits	7-8	Two-Supply Emitter Bias
7-4	More Optoelectronic Devices	7-9	Other Types of Bias
7-5	Voltage-Divider Bias	7-10	Troubleshooting VDB Circuits
		7-11	PNP Transistors

Chapter 8 Basic BJT Amplifiers 282

8-1	Base-Biased Amplifier	8-7	Analyzing an Amplifier
8-2	Emitter-Biased Amplifier	8-8	AC Quantities on the Data Sheet
8-3	Small-Signal Operation	8-9	Voltage Gain
8-4	AC Beta	8-10	The Loading Effect of Input Impedance
8-5	AC Resistance of the Emitter Diode	8-11	Swamped Amplifier
8-6	Two Transistor Models	8-12	Troubleshooting

Chapter 9 Multistage, CC, and CB Amplifiers 328

9-1	Multistage Amplifiers	9-6	Darlington Connections
9-2	Two-Stage Feedback	9-7	Voltage Regulation
9-3	CC Amplifier	9-8	The Common-Base Amplifier
9-4	Output Impedance	9-9	Troubleshooting Multistage Amplifiers
9-5	Cascading CE and CC		

Chapter 10 Power Amplifiers 368

- | | | | |
|-------------|------------------------------------|--------------|-----------------------------|
| 10-1 | Amplifier Terms | 10-6 | Biasing Class-AB Amplifiers |
| 10-2 | Two Load Lines | 10-7 | Class-AB Driver |
| 10-3 | Class-A Operation | 10-8 | Class-C Operation |
| 10-4 | Class-B Operation | 10-9 | Class-C Formulas |
| 10-5 | Class-B Push-Pull Emitter Follower | 10-10 | Transistor Power Rating |

Chapter 11 JFETs 416

- | | | | |
|-------------|------------------------------|--------------|-------------------------|
| 11-1 | Basic Ideas | 11-6 | Transconductance |
| 11-2 | Drain Curves | 11-7 | JFET Amplifiers |
| 11-3 | The Transconductance Curve | 11-8 | The JFET Analog Switch |
| 11-4 | Biasing in the Ohmic Region | 11-9 | Other JFET Applications |
| 11-5 | Biasing in the Active Region | 11-10 | Reading Data Sheets |
| | | 11-11 | JFET Testing |

Chapter 12 MOSFETs 472

- | | | | |
|-------------|----------------------------------|--------------|--------------------------------|
| 12-1 | The Depletion-Mode MOSFET | 12-7 | CMOS |
| 12-2 | D-MOSFET Curves | 12-8 | Power FETs |
| 12-3 | Depletion-Mode MOSFET Amplifiers | 12-9 | High-Side MOSFET Load Switches |
| 12-4 | The Enhancement-Mode MOSFET | 12-10 | MOSFET H-Bridge |
| 12-5 | The Ohmic Region | 12-11 | E-MOSFET Amplifiers |
| 12-6 | Digital Switching | 12-12 | Wide Bandgap (WBG) MOSFETs |
| | | 12-13 | MOSFET Testing |

Chapter 13 Thyristors 530

- | | | | |
|-------------|----------------------------------|-------------|--------------------------|
| 13-1 | The Four-Layer Diode | 13-5 | Bidirectional Thyristors |
| 13-2 | The Silicon Controlled Rectifier | 13-6 | IGBTs |
| 13-3 | The SCR Crowbar | 13-7 | Other Thyristors |
| 13-4 | SCR Phase Control | 13-8 | Troubleshooting |

Chapter 14 Frequency Effects 574

- | | | | |
|-------------|------------------------------------|--------------|----------------------------------|
| 14-1 | Frequency Response of an Amplifier | 14-7 | More Bode Plots |
| 14-2 | Decibel Power Gain | 14-8 | The Miller Effect |
| 14-3 | Decibel Voltage Gain | 14-9 | Risetime-Bandwidth Relationship |
| 14-4 | Impedance Matching | 14-10 | Frequency Analysis of BJT Stages |
| 14-5 | Decibels above a Reference | 14-11 | Frequency Analysis of FET Stages |
| 14-6 | Bode Plots | | |

Chapter 15 Differential Amplifiers 630

- | | | | |
|-------------|------------------------------------|-------------|---------------------|
| 15-1 | The Differential Amplifier | 15-5 | Common-Mode Gain |
| 15-2 | DC Analysis of a Diff Amp | 15-6 | Integrated Circuits |
| 15-3 | AC Analysis of a Diff Amp | 15-7 | The Current Mirror |
| 15-4 | Input Characteristics of an Op Amp | 15-8 | The Loaded Diff Amp |

Chapter 16 Operational Amplifiers 672

- | | | | |
|-------------|----------------------------|-------------|----------------------------------|
| 16-1 | Introduction to Op Amps | 16-5 | Two Op-Amp Applications |
| 16-2 | The 741 Op Amp | 16-6 | Linear ICs |
| 16-3 | The Inverting Amplifier | 16-7 | Op Amps as Surface-Mount Devices |
| 16-4 | The Noninverting Amplifier | | |

Chapter 17 Negative Feedback 716

- | | | | |
|-------------|---------------------------------|-------------|--------------------|
| 17-1 | Four Types of Negative Feedback | 17-4 | The ICVS Amplifier |
| 17-2 | VCVS Voltage Gain | 17-5 | The VCIS Amplifier |
| 17-3 | Other VCVS Equations | 17-6 | The ICIS Amplifier |
| | | 17-7 | Bandwidth |

Chapter 18 Linear Op-Amp Circuit Applications 746

- | | | | |
|-------------|---------------------------------|--------------|------------------------------------|
| 18-1 | Inverting-Amplifier Circuits | 18-6 | Summing Amplifier Circuits |
| 18-2 | Noninverting-Amplifier Circuits | 18-7 | Current Boosters |
| 18-3 | Inverter/Noninverter Circuits | 18-8 | Voltage-Controlled Current Sources |
| 18-4 | Differential Amplifiers | 18-9 | Automatic Gain Control |
| 18-5 | Instrumentation Amplifiers | 18-10 | Single-Supply Operation |

Chapter 19 Active Filters 794

- | | | | |
|-------------|---|--------------|--|
| 19-1 | Ideal Responses | 19-7 | VCVS Equal-Component Low-Pass Filters |
| 19-2 | Approximate Responses | 19-8 | VCVS High-Pass Filters |
| 19-3 | Passive Filters | 19-9 | MFB Bandpass Filters |
| 19-4 | First-Order Stages | 19-10 | Bandstop Filters |
| 19-5 | VCVS Unity-Gain Second-Order Low-Pass Filters | 19-11 | The All-Pass Filter |
| 19-6 | Higher-Order Filters | 19-12 | Biquadratic and State-Variable Filters |

Chapter 20 Nonlinear Op-Amp Circuit Applications 856

20-1	Comparators with Zero Reference	20-6	Waveform Conversion
20-2	Comparators with Nonzero References	20-7	Waveform Generation
20-3	Comparators with Hysteresis	20-8	Another Triangular Generator
20-4	Window Comparator	20-9	Active-Diode Circuits
20-5	The Integrator	20-10	The Differentiator
		20-11	Class-D Amplifier

Chapter 21 Oscillators 908

21-1	Theory of Sinusoidal Oscillation	21-7	The 555 Timer
21-2	The Wien-Bridge Oscillator	21-8	Astable Operation of the 555 Timer
21-3	Other RC Oscillators	21-9	555 Circuit Applications
21-4	The Colpitts Oscillator	21-10	The Phase-Locked Loop
21-5	Other LC Oscillators	21-11	Function Generator ICs
21-6	Quartz Crystals		

Chapter 22 Regulated Power Supplies 964

22-1	Supply Characteristics	22-5	Current Boosters
22-2	Shunt Regulators	22-6	DC-to-DC Converters
22-3	Series Regulators	22-7	Switching Regulators
22-4	Monolithic Linear Regulators		

Chapter 23 Industry 4.0 1016

23-1	Industry 4.0: An Overview	23-5	Active Sensors
23-2	Smart Sensors	23-6	Data Conversion
23-3	Different Types of Sensors	23-7	Data Exchange
23-4	Passive Sensors		

Appendix A	Data Sheet List 1050
-------------------	----------------------

Appendix B	Mathematical Derivations 1051
-------------------	-------------------------------

Appendix C	Digital/Analog Trainer System 1057
-------------------	------------------------------------

Appendix D	Thevenizing the R/2R D/A Converter 1060
-------------------	---

Appendix E	Summary Table Listing 1062
-------------------	----------------------------

Glossary	1064
-----------------	------

Answers	Odd-Numbered Problems 1077
----------------	----------------------------

Index	1083
--------------	------