

Contents

Preface	xiii
Symbols used in this book	xvi
SI units and abbreviations	xix
1 D.C. circuits and methods of circuit analysis	1
Aims and objectives	1
1.1 Introduction	3
1.2 Electric current, electromotive force, potential difference, energy and power, resistance and conductance	3
1.2.1 Summary of Section 1.2	3
1.2.2 Resistance and conductance	4
1.2.3 Internal resistance and output voltage of an e.m.f. source	8
1.3 Resistors in series and in parallel	9
1.3.1 Resistors in series	9
1.3.2 Resistors in parallel	10
1.3.3 The voltage divider	12
1.3.4 The current divider	13
1.3.5 The variable potential divider (or 'pot')	13
1.3.6 Summary of Section 1.3	15
1.4 The measurement of current, voltage and resistance	15
1.4.1 Using ammeters and voltmeters	15
1.4.2 The multimeter	16
1.4.3 The moving-coil multimeter	17
1.4.4 The digital multimeter	19
1.4.5 Summary of Section 1.4	21
1.5 Kirchhoff's laws	22
1.5.1 Introduction	22
1.5.2 Kirchhoff's current law	22
1.5.3 Kirchhoff's voltage law	22
1.6 Thévenin and Norton equivalent circuits	24
1.6.1 Voltage and current sources	24
1.6.2 Thévenin's theorem	26

1.6.3	Norton's theorem	28
1.6.4	Calculating the effects of voltmeters and ammeters	29
1.6.5	Circuits with multiple sources—the superposition principle	31
1.6.6	Summary of Section 1.6	32
1.7	Nodal analysis	33
1.7.1	Introduction	33
1.7.2	An outline of the method	34
1.7.3	Choosing a reference node	35
1.7.4	Obtaining the node voltage equations	35
1.7.5	Completing the analysis	35
1.7.6	A circuit with multiple e.m.f. sources	36
1.7.7	Summary of Section 1.7	37
1.8	Analysing circuits using a computer-aided design (CAD) package	37
	Answers to self-assessment questions	38
2	Signals, waveforms and a.c. components	45
	Aims and objectives	45
2.1	Electrical waveforms	47
2.2	Sinusoidal waveforms and frequency	48
2.3	Voltage, r.m.s. and power	56
2.3.1	Periodic waveforms	56
2.3.2	Non-periodic waveforms: signals and noise	62
2.3.3	Symbols for voltages and currents	67
2.4	Frequency spectra	69
2.4.1	Periodic waveforms	69
2.4.2	Spectra of signals and noise	74
2.5	A.C. components	77
2.5.1	Capacitors	77
2.5.2	Inductors	84
2.5.3	Transformers	91
2.6	Conclusion and summary	95
	Answers to self-assessment questions	97
3	Phasor analysis of a.c. circuits	100
	Aims and objectives	100
3.1	Phasors	101
3.1.1	Phasor diagrams	102
3.1.2	Phasor notation	104

3.1.3	Phasor addition	105
3.1.4	Phasor analysis of the low-pass CR circuit	106
3.2	Phasor multiplication and division	109
3.2.1	Multiplication: voltage gain	109
3.2.2	Division: impedance	111
3.3	Phasor manipulations using the operator j	112
3.3.1	The operator j	112
3.3.2	Using the operator j	114
3.3.3	Complex number terminology	117
3.3.4	Addition and subtraction of phasors in component form	117
3.3.5	Multiplication and division of complex numbers	118
3.4	Equivalent impedance and admittance	122
3.4.1	Impedance	122
3.4.2	Admittance	122
3.5	Circuit analysis using the operator j	124
3.5.1	A.C. analysis of the low-pass CR circuit	124
3.6	The decibel	128
3.7	Bode plots	130
3.7.1	Bode plots for simple low-pass networks	131
3.7.2	Simple high-pass networks	134
3.7.3	Networks with two break points	136
3.8	The frequency response of RLC circuits	140
3.8.1	The series RLC circuit	140
3.8.2	The series RLC bandpass circuit	142
3.8.3	Bandwidth of the series bandpass circuit	144
3.8.4	Bode plots for the bandpass RLC circuit	145
3.8.5	Parallel resonance	148
3.9	The principle of duality	149
3.10	Summary	150
	Answers to self-assessment questions	154
4	Amplifiers and feedback	167
	Aims and objectives	167
4.1	What are amplifiers?	168
4.1.1	Equivalent circuits	169
4.1.2	Inverting and non-inverting amplifiers	171
4.2	The operational amplifier	173

4.3	Feedback and operational amplifiers	175
4.3.1	A basic non-inverting feedback amplifier (series feedback connection)	177
4.3.2	Stability in feedback amplifiers	181
4.3.3	Frequency response and gain–bandwidth product	183
4.3.4	Input and output impedance	186
4.3.5	Frequency limitations of negative feedback	188
4.3.6	The inverting feedback amplifier (parallel or shunt feedback)	188
4.3.7	Current-derived feedback	191
4.4	Summary of feedback principles	192
4.5	Further examples of feedback circuits	192
4.5.1	Summing amplifiers	193
4.5.2	<i>CR</i> -active filters	195
4.6	Output offset and equivalent input offset sources	198
4.6.1	Bias current and input offset voltage and current	198
4.6.2	Calculating the output offset voltage	200
4.7	Noise and equivalent noise sources	204
4.7.1	Sources of internal noise	204
4.7.2	Amplifier equivalent noise generators	206
4.7.3	Calculating amplifier output noise	206
4.8	Voltage, current and speed limitations	208
4.8.1	Voltage swing	208
4.8.2	Current limit: short-circuit protection	208
4.8.3	Slew rate	209
4.8.4	Full-power bandwidth	209
4.9	A summary of some op amp feedback circuits	210
	Answers to self-assessment questions	211

5	Combinational logic circuits	215
	Aims and objectives	215
5.1	A simple interlock example	217
5.1.1	Truth table	218
5.1.2	Implementation	219
5.1.3	Summary of Section 5.1	221
5.2	Binary inputs and outputs	221
5.2.1	Coding	221
5.2.2	Number representation	222

5.2.3	Other symbols and distinct items	225
5.2.4	Summary of Section 5.2	226
5.3	Truth tables and Boolean notation	226
5.3.1	Problems with only one input	227
5.3.2	Problems with two inputs	227
5.3.3	Problems with more than two inputs	232
5.3.4	Implementation using gates	235
5.3.5	Summary of Section 5.3	236
5.4	Basic rules of Boolean algebra	237
5.4.1	Simplifying Boolean expressions	238
5.4.2	Summary of Section 5.4	239
5.5	Karnaugh maps	240
5.5.1	Obtaining product terms	240
5.5.2	Designing a seven-segment decoder using Karnaugh maps	245
5.5.3	The inverted Karnaugh map	247
5.5.4	NAND gate representation	251
5.5.5	Summary of Section 5.5	253
5.6	Electronic combinational logic	253
5.6.1	Some SSI devices	254
5.6.2	MSI devices	256
5.6.3	Programmable logic devices	258
5.6.4	Custom and semi-custom integrated circuits	265
5.7	Electrical characteristics of logic families	265
5.7.1	LS TTL	265
5.7.2	Other TTL families	270
5.7.3	Emitter-coupled logic	271
5.7.4	CMOS	271
5.7.5	Summary of Sections 5.6 and 5.7	274
	Answers to self-assessment questions	274

6 Sequential logic circuits 281

	Aims and objectives	281
6.1	Introduction	282
6.2	Latches	283
6.2.1	The clocked <i>SR</i> latch	285
6.2.2	The clocked <i>D</i> latch	286
6.2.3	Summary of Section 6.2	287
6.3	Flip-flops	287
6.3.1	The master–slave flip-flop	287

6.3.2	The edge-triggered flip-flop	288
6.3.3	The <i>JK</i> flip-flop	292
6.3.4	Practical flip-flops	293
6.3.5	Summary of Section 6.3	293
6.4	Registers	294
6.4.1	Timing characteristics of a transparent register	294
6.4.2	A commercial 8-bit register	295
6.4.3	Timing characteristics for edge-triggered registers	298
6.5	Shift registers	298
6.6	Counters	301
6.6.1	Synchronous counters	303
6.6.2	An integrated circuit counter	305
6.6.3	Cascading counters	306
6.6.4	Modulo- <i>n</i> counters	307
6.6.5	Frequency division	308
6.6.6	Summary of Sections 6.4 to 6.6	310
6.7	The state-transition diagram	310
6.8	A general sequential machine	312
6.8.1	The state table	313
6.8.2	The state-assignment table	313
6.8.3	Sequential PLDs	315
6.8.4	Summary of Sections 6.7 and 6.8	316
	Answers to self-assessment questions	317
7	Analogue–digital conversion	320
	Aims and objectives	320
7.1	Introduction	321
7.2	Digital-to-analogue conversion	321
7.2.1	Introduction	321
7.2.2	The binary-weighted resistor network	323
7.2.3	Buffering the resistor network	325
7.2.4	D-A converter with a stabilized voltage source	327
7.2.5	The <i>R-2R</i> ladder resistor network	329
7.2.6	Bipolar conversion	331
7.2.7	Quantization	333
7.2.8	Summary of Section 7.2	335
7.3	Analogue-to-digital conversion	336
7.3.1	The comparator and flash converter	336
7.3.2	The counter-ramp converter	338
7.3.3	The successive approximation A-D converter	340
7.3.4	Integrating converters	342

7.3.5	Quantization	346
7.3.6	Multiplexers	346
7.3.7	Summary of Section 7.3	347
7.4	The conversion of a.c. signals	348
7.4.1	Sample-and-hold devices	350
7.4.2	Specifying the sample-and-hold	351
7.4.3	Summary of Section 7.4	353
	Answers to self-assessment questions	353
8	Diodes and power supplies	356
	Aims and objectives	356
8.1	Introduction	356
8.2	Diodes	357
8.2.1	Electrons and holes	357
8.2.2	The structure of pn junctions	358
8.2.3	The properties of pn junction diodes	359
8.3	Power supplies	362
8.3.1	The transformer	364
8.3.2	Half-wave rectification	365
8.3.3	Full-wave rectification	366
8.3.4	Filtering circuits	367
8.4	Voltage regulation	371
8.4.1	Linear voltage regulators	373
8.4.2	Switched-mode power supplies	376
8.5	Summary	381
	Answers to self-assessment questions	382
9	Basic transistor circuits	385
	Aims and objectives	385
9.1	Introduction	386
9.2	Bipolar transistors	387
9.2.1	Operation of bipolar transistors	388
9.2.2	A simple amplifier and the hybrid- π equivalent circuit	391
9.2.3	A practical, discrete common-emitter amplifier	396
9.2.4	The long-tailed pair (differential pair)	398
9.2.5	The emitter-follower	401
9.3	Field-effect transistors (FETS)	403
9.3.1	The operation of JFETs	404
9.3.2	The operation of MOSFETs	405

9.3.3	MOSFETs compared with bipolars	408
9.3.4	FET circuits	408
9.4	Bipolar and FET push-pull output stages	408
9.4.1	A double emitter-follower	409
9.4.2	A double source follower	410
9.5	Basic switching and digital circuits	412
9.5.1	The transistor as a switch	412
9.5.2	Switching circuits using bipolar transistors	413
9.5.3	Switching circuits using FETs	415
9.6	Summary	418
	Answers to self-assessment questions	422
	Index	424