

CONTENTS

Instruction to study	12
1. HISTORY OF ELECTRONICS, LINEARIZATION	15
1.1 History	15
1.2 Linearization	19
1.3 Three-terminal linearization	20
1.4 The indefinite admittance matrix	22
1.5 The quiescent point in general	24
Summary	24
Question 1	25
Problems 1	25
2. QUIESCENT POINT OF ACTIVE TRIPOLES, ADMITTANCE MODELS	27
2.1 The quiescent point of a bipolar junction transistor	27
2.1.1 Basic description of a BJT principle	27
2.1.2 The BJT simplest AC model – common emitter	31
2.1.3 The BJT more complex AC model common emitter	32
2.1.4 The BJT simplest AC model – collector capacitance	34
2.2 The quiescent point of a field effect transistor	35
2.2.1 Basic description of a FET principle	35
2.2.1.1 Consider an n -channel „depletion mode“ device	36
2.2.1.2 Consider an n -channel „enhancement-mode“ device	38
2.3 The FET AC model – common source (in active – saturation region)	46
2.3.1 Note to the FET model	48
2.4 Triode – vacuum tubes	49

2.4.1 Basic description of a triode principle	49
2.4.2 Quiescent point	51
2.4.3 Small – signal model (parameters) and small – signal triode model	52
2.5 Admittance model of general active three- terminal device	53
Summary	60
Question 2	61
Problems 2	61
Problems key 2	62
3. MODERN AMPLIFIER STRUCTURES.....	65
3.1 Basic principle of structure	65
3.1.1 Conventional circuit techniques – VFA (Voltage Feedback Amplifier)	65
3.1.2 Current conveyer CCII (diamond transistor)	66
3.1.3 Current feedback amplifier (CFA – AD848, transimpedance amplifier)	67
3.1.4 VFA based on CFA structure	70
3.2 Basic signal (AC) and matrix model	71
3.2.1 VFA and matrix model	71
3.2.2 One input voltage amplifier model	72
3.2.3 Current conveyer signal and matrix model	72
3.2.4 CFA and matrix model	73
3.2.5 VFA based on CFA signal and matrix model	75
3.2.6 Transadmittance amplifier (TAA, OTA) signal and matrix model	75
3.3 Conclusion	75
Summary	76
Question 3	77
Problems 3	77
Problems key 3	78

4. BASIC FEEDBACK THEORY, STABILITY	79
4.1 Feedback – principle	79
4.2 Transfer function sensitivity	81
4.3 Frequency characteristic	81
4.4 Input impedance	82
4.5 Output impedance	84
4.6 Feedback system stability	85
4.6.1 Nyquist stability criterion	86
4.6.2 Nyquist stability criterion – Bode plots	88
Summary	91
Question 4	91
Problems 4	91
Problems key 4	93
5. GENERALIZED NODAL VOLTAGE ANALYSIS	96
5.1 An admittance model of $n+1$ terminal	96
5.2 The parallel connection of n - terminals	98
5.3 Determination of nodal voltages, transfer functions and circuit currents	104
5.4 Determination of input impedance	106
5.5 Voltage signal source (ideal)	106
5.6 Determination of output impedance (generally node impedance)	109
5.7 Interconnection of two nodes	110
Summary	110
Question 5	110
Problems 5	111
Problems key 5	112

6. ANALYSIS OF AMPLIFYING STRUCTURES (IDEALLY NO FREQUENCY DEPENDENT) AND OSCILLATORS	116
6.1 An linear circuits – transistors and triode	116
6.1.1 Common emitter connection (CE)	116
6.1.2 Common collector conection (CC)	118
6.1.2.1 Notice – buffer large signal properties	120
6.1.3 Common base configuration (CB)	120
6.1.4 Effect of the C_{CB}	121
6.1.5 Cascode amplifier with two BJTs	123
6.1.6 Common source configuration (CS; NMOSFET enhancement mode)	125
6.1.7 Cascode amplifier with FET and BJT	127
6.1.8 Triode amplifier	130
6.1.9 FE amplifier with rezistors R_s	132
6.2 An linear circuits with operational amplifiers (OPA)	135
6.2.1 Current – to – voltage converter	136
6.2.2 Inverting amplifier with OPA	138
6.2.3 Noninverting amplifier with OPA	141
6.2.4 Differential amplifier with OPA	143
6.2.5 3 – dB frequency – f_3	144
6.2.6 Wien oscilator	146
6.2.7 Phase shift oscilator	149
Summary	152
Question 6	153
Problems 6	153
Problems key 6	154
7. ANALYSIS OF FREQUENCY STRUCTURES 2 ND ORDER FILTERS	155

7.1 Approximation LP normalized functions –general – for a cascade realization	157
7.2 Butterworth LP	158
7.2.1 Determining needed n for the Butterwothr lowpass	159
7.3 Butterworth HP	160
7.4 Chebyshev LP	161
7.5 Bessel	163
7.6 Summary	165
7.7 Network functions	166
7.7.1 Basic low-pass network funkcions	166
7.7.2 Basic high-pass network funkcions	167
7.7.3 Band-pass network funkcions	169
7.7.4 Band-stop network funkcions	170
7.8 Examples of second order filter realization	172
7.8.1 Sallen-Key LP (2 nd order) filter	173
7.8.2 Inverting LP (2 nd order) filter	175
7.8.3 Inverting BP (2 nd order) filter	177
7.8.4 Inverting HP (2 nd order) filter	179
7.8.5 Sallen-Key HP (2 nd order) filter	179
7.8.6 Notch filter (2 nd order; bandstop)	181
7.9 Examples of first order filter realization	182
7.10 Basic cascade - connection	184
7.10.1 Two LP2 cascade	185
7.10.2 Two HP2 cascade	188
7.10.3 Cascade connection of LP2 and HP2	190
7.10.4 Cascade connection of LP2 and BP2	192
7.10.5 Cascade connection of HP2 and BP2	192

7.11 Non ideal operational amplifiers	193
Summary	194
Question 7	195
Problems 7	196
Problems key 7	197
8. RECTIFIERS, CURRENT AND VOLTAGE SOURCES LOGARITHMIC AMPLIFIER, ANALOG MULTIPLIER	200
8.1 Rectifier	200
8.2 Voltage sources	205
8.3 Current sources	210
8.4 Logarithmic amplifier	212
8.5 Antilogarithmic amplifier	218
8.6 Multiplier – divider	218
8.7 Square root circuit; square circuit	221
Summary	221
Question 8	222
Problems 8	222
Problems key 8	223
9. MODULATION, DEMODULATION, SIGNAL SAMPLING	227
9.1 Amplitude modulation circuits (AM), demodulation	227
9.2 Angular modulation – frequency (FM) and phase (PM)	235
9.2.1 Frequency modulation	236
9.2.2 Basic demodulation FM principle	238
9.2.3 Circuit operation of a Foster-Seeley discriminator	240
9.2.4 Ratio detector	243
9.2.5 Phase – locked loop (PLL)	251

9.2.6 Phase modulation	254
9.2.7 PM demodulator	256
9.3 Pulse modulations	261
9.4 Sampling theorem	267
Summary	268
Question 9	269
Problems 9	270
Problems key 9	270
10. A/D AND D/A CONVERTER PRINCIPLES.....	272
10.1 Basic consideration – ADC	272
10.2 Basic consideration – DAC	277
10.2.1 Summation of binary weighted currents	278
10.2.2 R-2R ladder	278
10.2.3 DAC with current output	279
10.2.4 Multiplying DACs (MDAC)	280
10.3 Basic principles of ADCs	280
10.3.1 Flash conversion (parallel encoder)	281
10.3.2 Dual slope ADCs	281
10.3.3 SAR ADCs	283
10.3.4 Voltage – to frequency ADC	285
10.3.5 Delta sigma converter	285
10.3.6 Pipelined analog – to digital converters	285
10.3.7 Comparison of ADCs	286
Summary	287
Question 10	288

Problems 10	288
Problems key 10	288
11. AMPLITUDE STABILIZATION OF THE HARMONIC OSCILATOR.....	290
11.1 Wien bridge oscillator	290
11.2 Phase shift oscillator	295
11.3 Band pass filter – comparator oscillator (spot sinus)	297
Summary	299
Question 11	299
Problems 11	300
Problems key 11	300
12. FREQUENCY AND TIME DOMAIN CONSIDERATION.....	301
12.1 Step response od second order systems and damping ratio	304
Summary	307
Question 12	308
Problems 12	308
Problems key 12	309
13. RELAXATION OSCILLATORS.....	310
Summary	317
Question 13	318
Problems 13	318
Problems key 13	318
14. THERMAL CONSIDERATION, THERMAL RESISTANCE.....	320
14.1 Thermal circuit	322
14.2 Required Heat – Sink thermal resistance	324
14.3 Heat – Sink types	325

14.4 Junction temperature under pulsed conditions	326
Summary	329
Question 14	330
Problems 14	330
Problems key 14	331
15. REREFERENCE	332
16. INDEX	334