

Contents

<i>Preface</i>	<i>ix</i>
1 Fundamentals	1
1.1 Units	1
1.2 Standard Form Notation	1
1.3 'Scientific' Notation	2
1.4 Electric versus Electronic	4
1.5 Basic Electrical Concepts	5
1.5.1 Bohr Model	5
1.5.2 Electric Current	7
1.5.3 Electromotive Force (emf)	8
1.5.4 Resistance (R)	9
1.5.5 Potential Difference (p.d.)	14
1.5.6 Conventional Current and Electron Flow	16
1.5.7 Ohm's Law	16
1.5.8 Internal Resistance (r)	17
1.5.9 Energy (W) and Power (P)	20
1.5.10 Alternating and Direct Quantities	23
1.5.11 Use of Meters	24
1.6 Simulation Packages	25
Assignment Questions	26
2 D.C. Circuits	28
2.1 Resistors in Series	28
2.2 Resistors in Parallel	33
2.3 Series/Parallel Combinations	39
2.4 Kirchhoff's Current Law	44
2.5 Kirchhoff's Voltage Law	46
2.6 Potentiometer	51
Assignment Questions	54
Suggested Practical Assignments	59
Assignment 1	59
Assignment 2	59
Assignment 3	60
Assignment 4	60

- 3.1 Coulomb's Law 61
- 3.2 Electric Fields 62
- 3.3 Electric Field Strength (E), Electric Flux (ψ) and Flux Density (D) 64
- 3.4 The Charging Process and Potential Gradient 65
- 3.5 Capacitance (C) 68
- 3.6 Permittivity 69
- 3.7 Calculating Capacitor Values 70
- 3.8 Capacitors in Parallel 72
- 3.9 Capacitors in Series 75
- 3.10 Series/Parallel Combinations 78
- 3.11 Energy Stored 80
- 3.12 Dielectric Strength and Working Voltage 84
- 3.13 Capacitor Types 85
 - 3.13.1 Paper 86
 - 3.13.2 Air 86
 - 3.13.3 'Plastic' 87
 - 3.13.4 Silvered Mica 87
 - 3.13.5 Mixed Dielectric 87
 - 3.13.6 Electrolytic 88
- Assignment Questions 89
- Suggested Practical Assignment 93

4 Magnetic Fields and Circuits

94

- 4.1 Magnetic Materials 94
- 4.2 Magnetic Fields 94
- 4.3 The Magnetic Circuit 97
- 4.4 Magnetic Flux and Flux Density 98
- 4.5 Magnetomotive Force (mmf) 99
- 4.6 Magnetic Field Strength 100
- 4.7 Permeability 101
- 4.8 Magnetisation (B/H) Curve 105
- 4.9 Composite Series Magnetic Circuits 109
- 4.10 Reluctance (S) 111
- 4.11 Magnetic Hysteresis 114
- 4.12 Parallel Magnetic Circuits 116
- Assignment Questions 117
- Suggested Practical Assignments 119
 - Assignment 1 119
 - Assignment 2 120

5 Electromagnetism

122

- 5.1 Faraday's Law of Electromagnetic Induction 122
- 5.2 Fleming's Right-Hand Rule 124
- 5.3 Emf Induced in a Single Straight Conductor 127
- 5.4 Force on a Current-Carrying Conductor 132
- 5.5 The Motor Principle 134
- 5.6 Force between Parallel Conductors 136

5.7	Eddy Currents	139
5.8	Self- and Mutual Inductance	140
5.8.1	Self-Inductance	141
5.8.2	Flux Linkages	142
5.8.3	Factors Affecting Inductance	144
5.8.4	Mutual Inductance	146
5.8.5	Relationship between Self- and Mutual Inductance	147
5.9	Energy Stored—	149
5.10	The Transformer Principle—	152
	Assignment Questions—	157
	Suggested Practical Assignments	159
	Assignment 1	160
	Assignment 2	160
	Assignment 3	160

6 Semiconductor Theory and Diodes 162

6.1	Atomic Structure	162
6.2	Intrinsic (Pure) Semiconductors	163
6.3	Electron–Hole Pair Generation and Recombination	165
6.4	Conduction in Intrinsic and Extrinsic (Impure) Semiconductors	166
6.5	n-type Semiconductor	167
6.6	p-type Semiconductor	168
6.7	The p-n Junction	169
6.8	Forward-Biased and Reverse-Biased Diode	171
6.9	Diode Characteristics	173
6.10	The Zener Diode	175
6.11	The LED	179
6.12	The Solar Cell	181
	Assignment Questions	182
	Suggested Practical Assignments	182
	Assignment 1	182
	Assignment 2	182

7 Transistors 184

7.1	Bipolar Transistor	184
7.2	Transistor Effect	186
7.3	Transistor as Switch	188
7.4	Transistor as Amplifier	189
7.5	Field Effect Transistor	191
7.6	Integrated Circuits and Moore's Law	192
7.7	Opamps	194
7.8	Inverting and Non-Inverting Amplifiers with Opamps	196
	Assignment Questions	199

8 Alternating Quantities 200

8.1	Production of an Alternating Waveform	200
8.2	Angular Velocity and Frequency	203
8.3	Standard Expression for an Alternating Quantity	204

8.4	<i>Average and r.m.s. Value and Peak and Form Factor</i>	205
8.5	<i>Rectifiers</i>	210
8.6	<i>Phase and Phase Angle</i>	213
8.7	<i>Phasor Representation</i>	215
8.8	<i>Addition of Alternating Quantities</i>	218
8.9	<i>Oscilloscope</i>	224
	<i>Assignment Questions</i>	226
9	D.C. Machines	229
9.1	<i>Motor/Generator Duality</i>	229
9.2	<i>The Generation of d.c. Voltage</i>	231
9.3	<i>Separately Excited Generator</i>	234
9.4	<i>Shunt Generator</i>	235
9.5	<i>Series Generator</i>	237
9.6	<i>Shunt Motor</i>	239
9.7	<i>Series Motor</i>	240
	<i>Assignment Questions</i>	242
10	D.C. Transients	243
10.1	<i>Capacitor-Resistor Series Circuit: Charging</i>	243
10.2	<i>Capacitor-Resistor Series Circuit: Discharging</i>	247
10.3	<i>Inductor-Resistor Series Circuit: Charging</i>	249
10.4	<i>Inductor-Resistor Series Circuit: Discharging</i>	253
	<i>Assignment Questions</i>	254
	<i>Suggested Practical Assignments</i>	254
	<i>Assignment 1</i>	254
	<i>Appendix A: Physical Quantities with SI and other preferred units</i>	257
	<i>Appendix B: Answers to Assignment Questions</i>	259
	<i>Index</i>	264