

Contents

Author's word	7
Introduction	9
Unit conversions and basic electrical quantities	10
Electric charge, current, voltage, current density and current field intensity	12
Diagram, schematic symbols	14
Basic schematic symbols	14
Electrical schematic symbols (IEC and ANSI symbols)	15
Example of using schematic symbols in diagrams	17
Diagrams in electrical engineering	18
Calculation of conductor resistance	20
Resistance dependence on temperature	22
Ohm's law and a simple electrical circuit	24
Work, power and thermal effects of electric current	26
Efficiency of electrical devices	27
Voltage drop on a line	30
DC current and voltage sources	32
Kirchhoff's laws I. and II.	34
Connecting resistors	36
Connecting sources	38
Transfiguration	40
Changing the range of measuring instruments	42
Solving circuits using various methods	44
Electrostatic field	50
Capacitors and their capacitance	52
Fundamentals of semiconductors	54
N-type conductivity (negative)	54
P-type conductivity (positive)	55
Diode	55
Graetz connection	57
Transistor	58
Bipolar transistor	58
Unipolar transistor	61
MOSFET with a conductive channel	62
MOSFET with an induced channel	63
Digital circuits using transistors	64
LKO TTL construction	65
LKO CMOS construction	66
Magnetism	68
Electromagnetic induction	70
Single-phase alternating current and circuits	72

Three-phase alternating current 74

Transient phenomena 76

Conclusion 78

Terminology 80

Electricity distribution diagram from power plant to consumer/household 83

Sources used 83

