

Contents

1	Introduction	1
1.1	Electrical Measurement Systems	1
1.2	Common and Normal Mode	2
1.3	Signal-To-Noise Ratio	3
1.4	Decibel Units	3
1.5	Differential-Ended Versus Single-Ended	4
1.6	Signals	4
1.6.1	Risetime and Falltime	4
1.6.2	Bandwidth	5
1.7	Systems	5
1.8	Solved Problems	6
2	Noise: Sources and Remedies	9
2.1	Introduction	9
2.2	Internal Noise	10
2.2.1	Johnson Noise	10
2.2.2	Shot Noise	11
2.2.3	1/f-Noise	11
2.2.4	Quantization Noise	12
2.3	Coupling By Radiation	12
2.3.1	Electric Dipole Antennas	12
2.3.2	Magnetic Dipole Antennas	16
2.4	Capacitive Crosstalk	20
2.5	Inductive Crosstalk	23
2.6	Common Impedances	25
2.7	Summary and Recommendations	29
2.8	Solved Problems	30
	Reference	31

3	Sensors	33
3.1	Introduction	33
3.2	Temperature Sensors	34
3.2.1	Thermocouples	34
3.2.2	Metal Temperature Sensors	39
3.2.3	Measuring Resistance	40
3.2.4	Bandgap Sensors	42
3.2.5	Cryogenic Temperatures	43
3.2.6	Extremely High Temperatures	43
3.3	The Strain Gauge Principle	45
3.3.1	Strain Gauges	45
3.3.2	The Wheatstone Bridge	47
3.3.3	Accelerometers	49
3.3.4	Pressure Sensors	50
3.3.5	Flow Sensors	51
3.3.6	Fluid Level Sensors	53
3.3.7	Torque Sensors	53
3.3.8	Viscosity Sensors	55
3.3.9	Load Cell	55
3.4	Piezoelectric Crystals	56
3.5	Hall Sensors	58
3.6	Position Sensors	59
3.7	Photo Sensors	61
3.7.1	Light Units	61
3.7.2	Photodiodes	61
3.7.3	Avalanche Photodiodes	63
3.7.4	Position-Sensitive Detectors	64
3.7.5	Photomultipliers	65
3.8	Particle Detectors	67
3.8.1	Channel Electron Multipliers	67
3.8.2	Microchannel Plates	68
3.9	Vacuum Gauges	69
3.9.1	Introduction	69
3.9.2	The Pirani Gauge	69
3.9.3	Gas Ionization Gauges	71
3.10	Solved Problems	72
	References	76
4	The Instrumentation Amplifier	77
4.1	Introduction	77
4.2	Implementations	79
4.2.1	Classic IA Circuit	79
4.3	CMRR Versus SNR	83
4.4	Solved Problems	84

5	Transmission Lines	85
5.1	Introduction	85
5.2	The Characteristic Impedance	85
5.3	Termination	95
5.4	Splitting and Splicing	97
5.5	Attenuation	98
5.6	Time Domain Reflectometry	99
5.7	Solved Problems	101
	References	109
6	Probes	111
6.1	Introduction	111
6.2	Passive Probes	113
6.3	Active Probes	116
6.4	Current Probes	117
6.5	Solved Problems	119
7	Transform Theory	123
7.1	Introduction	123
7.2	The Fourier Transform	125
7.2.1	Case 1: Signal is Periodic	125
7.2.2	Case 2: Signal is Non-Periodic, But 'Time-Limited'	129
7.2.3	Case 3: Signal is Non-Periodic and Infinite	131
7.2.4	FFT Outputs	134
7.2.5	Aliasing	136
7.3	Describing Systems	138
7.3.1	Distortion-Free Systems	141
7.4	Complex Frequencies	143
7.4.1	Laplace Representation of Systems	145
7.4.2	The z Transform	149
7.5	Solved Problems	153
	Reference	159
8	Spectrum Analyzers	161
8.1	Introduction	161
8.2	Windows	164
8.3	Resolution Bandwidth	166
8.3.1	Quantifying the Leakage	166
8.3.2	Resolution Bandwidth	169
8.4	Heterodyne Analyzers	170
8.5	Solved Problems	172

9	Analog Filters	175
9.1	Introduction	175
9.2	First-Order Filters	175
9.2.1	Passive Filters	175
9.3	Second-Order Filters	177
9.3.1	'Biquad'	177
9.3.2	Lowpass: $b_2 = b_1 = 0$	178
9.3.3	Bandpass: $b_2 = b_0 = 0$	179
9.3.4	Highpass: $b_1 = b_0 = 0$	180
9.4	Implementations	180
9.4.1	The Double Integral Method	180
9.4.2	The Sallen–Key Link	182
9.4.3	Switched Capacitors	184
9.4.4	More About Passive Filters	185
9.4.5	Special Cases	186
9.5	Filter Models	186
9.5.1	Butterworth	187
9.5.2	Chebyshev	188
9.5.3	Cauer	190
9.6	Filter Transformations	191
9.6.1	Lowpass to Lowpass	192
9.6.2	Lowpass to Highpass	193
9.6.3	Lowpass to Bandpass	193
9.6.4	Lowpass to Bandstop	194
9.7	Time Domain	195
9.7.1	Convolution	195
9.8	Solved Problems	202
10	Digital Filters	209
10.1	Introduction	209
10.2	FIR Filters	211
10.3	IIR Filters	213
10.4	Designing Digital Filters	218
10.4.1	FIR Filters: The Inverse Fourier Transform Method	218
10.4.2	IIR Filters: The Bilinear Transformation Method	220
10.5	Solved Problems	223
11	ADCs and Sampling	229
11.1	Introduction	229
11.2	Sampling	230
11.3	Quantization and Quantization Noise	230
11.4	Digital-to-Analog Converters	233
11.5	SAR ADCs	234
11.6	Flash ADCs	236
11.7	Pipeline ADCs	236

11.8	Dual Slope ADCs	240
11.8.1	The Integrator	240
11.8.2	The Dual Slope Circuit	241
11.9	Level-Crossing ADCs	244
11.10	Equivalent Number of Bits	247
11.11	Oversampling	247
11.11.1	As a Means to Reduce Noise	247
11.11.2	As a Means to Improve Resolution	250
11.12	Dithering	250
11.13	Sigma-Delta ADCs	253
11.13.1	Background	253
11.13.2	Theory	255
11.14	Extreme Sampling Rates	257
11.14.1	Interleaved SARs	258
11.14.2	Equivalent-Time Sampling	258
11.15	Solved Problems	260
	References	265
12	Time-to-Digital Converters	267
12.1	Introduction	267
12.2	The Vernier Principle	270
12.2.1	Vernier TDC with no Reference Clock	270
12.2.2	Vernier TDC with a Reference Clock	271
12.3	Delaylines	272
12.4	Time Stretching	274
12.5	Solved Problems	276
	References	278
13	Statistics	279
13.1	Introduction	279
13.2	Expectation and Variance	281
13.3	Unbiased Estimators	282
13.4	Interval Estimations	284
13.5	The Uniform Distribution	287
13.6	Solved Problems	288
14	Uncertainty Budgets	291
14.1	Introduction	291
14.2	Signal Models	291
14.3	Uncertainty Budgets	294
14.3.1	Examples	295
14.4	'Guesstimating'	299
14.5	Summary	301
14.6	Solved problems	302
	References	305

15	The Lock-In Amplifier	307
15.1	Introduction	307
15.2	Phase Sensitive Detector	308
15.2.1	PSDs	308
15.2.2	Analog PSDs	311
15.2.3	Multiplying PSDs	312
15.3	Phase-Locked Loops	313
15.4	LIAs	313
15.5	Solved Problems	315
	References	318
16	Correlation	319
16.1	Introduction	319
16.2	Cross-Correlation	320
16.2.1	Implementation: Matched Filters	326
16.3	Auto-Correlation	327
16.3.1	Auto-Correlation Applications	331
16.4	Discrete-Time Correlation	333
16.4.1	Cross-Correlation	333
16.4.2	Auto-Correlation	335
16.4.3	Circular Correlation	336
16.5	Solved Problems	338
	References	345
17	Curve Fitting	347
17.1	Introduction	347
17.2	The Orthogonality Principle	349
17.3	Curve Fitting to Exponential Functions	355
17.4	MATLAB Tips	356
17.5	Matrix Uncertainties and Pitfalls	357
17.5.1	Error Propagation in Matrices	357
17.5.2	Ill-Conditioned Matrices	358
17.6	The Sampling Theorem Revisited	360
17.7	Solved Problems	364
18	Introduction to Control Theory	369
18.1	Control Systems	369
18.2	Feedback Systems	371
18.3	Control Systems	373
18.4	The PI Controller	374
18.5	The PD Controller	376
18.6	The PID Controller	377
18.7	Identifying the System	378
18.7.1	First-Order Systems	378
18.7.2	Second-Order Systems	382
18.8	Finding the Control Parameters	384

Acronym

18.8.1	Ziegler–Nichol’s Rule of Thumb	384
18.8.2	Using Phase and Gain Margin Criteria	385
18.9	Discretizing	387
18.9.1	Euler Transformation	387
18.9.2	Bilinear Transformation	389
Appendix: Operational Amplifiers		391
Index		401

AC	Alternating Current
ACF	Auto-Correlation Function
ADC	Analog-to-Digital Converter
BAG	Bayard–Alpert Gauge
BIPM	Bureau International de Poids et Mesures
BNC	Bayonet Neill–Concelman
CAN	Controller Area Network
CEM	Channel Electron Multiplier
CC	Cold Junction Compensation
CMRR	Common Mode Rejection Ratio
CMOS	Complementary Metal Oxide Semiconductor
CLT	Central Limit Theorem
CW	Continuous Wave
DAC	Digital-to-Analog Converter
DAQ	Data Acquisition
DC	Direct Current
dB	decibel
DCV	Direct Current Voltage meter
DFT	Discrete Fourier Transform
DLS	Dynamic Light Scattering
DMM	Digital Multimeter
ECG	Electro Cardio Gram
EM	Electro Magnetic
EMC	Electromagnetic Compatibility
emf	electromotive force
ENOB	Equivalent Number of Bits
FIR	Finite Impulse Response
FFT	Fast Fourier Transform
GUM	Guide to the expression of Uncertainty in Measurement
HV	High Vacuum
IA	Instrumentation Amplifier