

Contents

	Preface	<i>xvii</i>
	Acknowledgments	<i>xix</i>
1	Introduction	1
1.1	History of Lumped Elements	1
1.2	Why Use Lumped Elements for RF and Microwave Circuits?	2
1.3	L , C , R Circuit Elements	4
1.4	Basic Design of Lumped Elements	6
1.4.1	Capacitor	7
1.4.2	Inductor	8
1.4.3	Resistor	8
1.5	Lumped-Element Modeling	9
1.6	Fabrication	11
1.7	Applications	12
	References	13
2	Inductors	17
2.1	Introduction	17

2.2	Basic Definitions	18
2.2.1	Inductance	18
2.2.2	Magnetic Energy	18
2.2.3	Mutual Inductance	20
2.2.4	Effective Inductance	20
2.2.5	Impedance	21
2.2.6	Time Constant	21
2.2.7	Quality Factor	22
2.2.8	Self-Resonant Frequency	23
2.2.9	Maximum Current Rating	23
2.2.10	Maximum Power Rating	23
2.2.11	Other Parameters	23
2.3	Inductor Configurations	24
2.4	Inductor Models	25
2.4.1	Analytical Models	25
2.4.2	Coupled-Line Approach	28
2.4.3	Mutual Inductance Approach	34
2.4.4	Numerical Approach	36
2.4.5	Measurement-Based Model	38
2.5	Coupling Between Inductors	45
2.5.1	Low-Resistivity Substrates	45
2.5.2	High-Resistivity Substrates	46
2.6	Electrical Representations	50
2.6.1	Series and Parallel Representations	50
2.6.2	Network Representations	51
	References	52
3	Printed Inductors	57
3.1	Inductors on Si Substrate	58
3.1.1	Conductor Loss	60
3.1.2	Substrate Loss	63
3.1.3	Layout Considerations	64
3.1.4	Inductor Model	65
3.1.5	Q-Enhancement Techniques	69
3.1.6	Stacked-Coil Inductor	80
3.1.7	Temperature Dependence	84

3.2	Inductors on GaAs Substrate	86
3.2.1	Inductor Models	87
3.2.2	Figure of Merit	88
3.2.3	Comprehensive Inductor Data	88
3.2.4	Q-Enhancement Techniques	104
3.2.5	Compact Inductors	112
3.2.6	High Current Handling Capability Inductors	116
3.3	Printed Circuit Board Inductors	118
3.4	Hybrid Integrated Circuit Inductors	121
3.4.1	Thin-Film Inductors	121
3.4.2	Thick-Film Inductors	124
3.4.3	LTCC Inductors	126
3.5	Ferromagnetic Inductors	127
	References	129
4	Wire Inductors	137
4.1	Wire-Wound Inductors	137
4.1.1	Analytical Expressions	137
4.1.2	Compact High-Frequency Inductors	144
4.2	Bond Wire Inductor	146
4.2.1	Single and Multiple Wires	147
4.2.2	Wire Near a Corner	150
4.2.3	Wire on a Substrate Backed by a Ground Plane	151
4.2.4	Wire Above a Substrate Backed by a Ground Plane	153
4.2.5	Curved Wire Connecting Substrates	154
4.2.6	Twisted Wire	155
4.2.7	Maximum Current Handling of Wires	155
4.3	Wire Models	156
4.3.1	Numerical Methods for Bond Wires	156
4.3.2	Measurement-Based Model for Air Core Inductors	156
4.3.3	Measurement-Based Model for Bond Wires	158
4.4	Magnetic Materials	160
	References	161

5	Capacitors	163
5.1	Introduction	163
5.2	Capacitor Parameters	165
5.2.1	Capacitor Value	165
5.2.2	Effective Capacitance	166
5.2.3	Tolerances	166
5.2.4	Temperature Coefficient	166
5.2.5	Quality Factor	167
5.2.6	Equivalent Series Resistance	167
5.2.7	Series and Parallel Resonances	167
5.2.8	Dissipation Factor or Loss Tangent	170
5.2.9	Time Constant	170
5.2.10	Rated Voltage	170
5.2.11	Rated Current	170
5.3	Chip Capacitor Types	171
5.3.1	Multilayer Dielectric Capacitor	171
5.3.2	Multiplate Capacitor	172
5.4	Discrete Parallel Plate Capacitor Analysis	173
5.4.1	Vertically Mounted Series Capacitor	173
5.4.2	Flat-Mounted Series Capacitor	176
5.4.3	Flat-Mounted Shunt Capacitor	177
5.4.4	Measurement-Based Model	178
5.5	Voltage and Current Ratings	181
5.5.1	Maximum Voltage Rating	181
5.5.2	Maximum RF Current Rating	181
5.5.3	Maximum Power Dissipation	182
5.6	Capacitor Electrical Representation	185
5.6.1	Series and Shunt Connections	185
5.6.2	Network Representations	187
	References	188
6	Monolithic Capacitors	191
6.1	MIM Capacitor Models	192
6.1.1	Simple Lumped Equivalent Circuit	193

6.1.2	Coupled Microstrip-Based Distributed Model	194
6.1.3	Single Microstrip-Based Distributed Model	198
6.1.4	EC Model for MIM Capacitor on Si	202
6.1.5	EM Simulations	204
6.2	High-Density Capacitors	206
6.2.1	Multilayer Capacitors	208
6.2.2	Ultra-Thin-Film Capacitors	211
6.2.3	High-K Capacitors	212
6.2.4	Fractal Capacitors	212
6.2.5	Ferroelectric Capacitors	214
6.3	Capacitor Shapes	216
6.3.1	Rectangular Capacitors	217
6.3.2	Circular Capacitors	218
6.3.3	Octagonal Capacitors	218
6.4	Design Considerations	220
6.4.1	Q-Enhancement Techniques	220
6.4.2	Tunable Capacitor	223
6.4.3	Maximum Power Handling	223
	References	227
7	Interdigital Capacitors	229
7.1	Interdigital Capacitor Models	230
7.1.1	Approximate Analysis	230
7.1.2	J-Inverter Network Equivalent Representation	235
7.1.3	Full-Wave Analysis	236
7.1.4	Measurement-Based Model	238
7.2	Design Considerations	239
7.2.1	Compact Size	239
7.2.2	Multilayer Capacitor	241
7.2.3	Q-Enhancement Techniques	244
7.2.4	Voltage Tunable Capacitor	247
7.2.5	High-Voltage Operation	249
7.3	Interdigital Structure as a Photodetector	249
	References	251

8	Resistors	253
8.1	Introduction	253
8.2	Basic Definitions	255
8.2.1	Power Rating	255
8.2.2	Temperature Coefficient	256
8.2.3	Resistor Tolerances	256
8.2.4	Maximum Working Voltage	256
8.2.5	Maximum Frequency of Operation	257
8.2.6	Stability	257
8.2.7	Noise	257
8.2.8	Maximum Current Rating	257
8.3	Resistor Types	257
8.3.1	Chip Resistors	258
8.3.2	MCM Resistors	258
8.3.3	Monolithic Resistors	258
8.4	High-Power Resistors	265
8.5	Resistor Models	267
8.5.1	EC Model	268
8.5.2	Distributed Model	269
8.5.3	Meander Line Resistor	270
8.6	Resistor Representations	272
8.6.1	Network Representations	272
8.6.2	Electrical Representations	272
8.7	Effective Conductivity	274
8.8	Thermistors	276
	References	276
9	Via Holes	279
9.1	Types of Via Holes	279
9.1.1	Via Hole Connection	279
9.1.2	Via Hole Ground	281
9.2	Via Hole Models	282
9.2.1	Analytical Expression	283

9.2.2	Quasistatic Method	284
9.2.3	Parallel Plate Waveguide Model	286
9.2.4	Method of Moments	287
9.2.5	Measurement-Based Model	289
9.3	Via Fence	290
9.3.1	Coupling Between Via Holes	293
9.3.2	Radiation from Via Ground Plug	293
9.4	Plated Heat Sink Via	294
9.5	Via Hole Layout	294
	References	296
10	Airbridges and Dielectric Crossovers	299
10.1	Airbridge and Crossover	299
10.2	Analysis Techniques	301
10.2.1	Quasistatic Method	301
10.2.2	Full-Wave Analysis	306
10.3	Models	308
10.3.1	Analytical Model	308
10.3.2	Measurement-Based Model	310
	References	315
11	Transformers and Baluns	317
11.1	Basic Theory	318
11.1.1	Parameters Definition	318
11.1.2	Analysis of Transformers	319
11.1.3	Ideal Transformers	322
11.1.4	Equivalent Circuit Representation	323
11.1.5	Equivalent Circuit of a Practical Transformer	325
11.1.6	Wideband Impedance Matching Transformers	326
11.1.7	Types of Transformers	329
11.2	Wire-Wrapped Transformers	329
11.2.1	Tapped Coil Transformers	329
11.2.2	Bond Wire Transformer	332
11.3	Transmission-Line Transformers	332

11.4	Ferrite Transformers	336
11.5	Parallel Conductor Winding Transformers on Si Substrate	339
11.6	Spiral Transformers on GaAs Substrate	341
11.6.1	Triformer Balun	344
11.6.2	Planar-Transformer Balun	345
	References	349
12	Lumped-Element Circuits	353
12.1	Passive Circuits	353
12.1.1	Filters	353
12.1.2	Hybrids and Couplers	356
12.1.3	Power Dividers/Combiners	370
12.1.4	Matching Networks	372
12.1.5	Lumped-Element Biasing Circuit	377
12.2	Control Circuits	380
12.2.1	Switches	381
12.2.2	Phase Shifters	387
12.2.3	Digital Attenuator	390
	References	392
13	Fabrication Technologies	395
13.1	Introduction	395
13.1.1	Materials	396
13.1.2	Mask Layouts	401
13.1.3	Mask Fabrication	401
13.2	Printed Circuit Boards	402
13.2.1	PCB Fabrication	404
13.2.2	PCB Inductors	405
13.3	Microwave Printed Circuits	405
13.3.1	MPC Fabrication	407
13.3.2	MPC Applications	408
13.4	Hybrid Integrated Circuits	410
13.4.1	Thin-Film MICs	410

13.4.2	Thick-Film Technology	412
13.4.3	Cofired Ceramic and Glass-Ceramic Technology	414
13.5	GaAs MICs	416
13.5.1	MMIC Fabrication	418
13.5.2	MMIC Example	421
13.6	CMOS Fabrication	421
13.7	Micromachining Fabrication	424
	References	425
14	Microstrip Overview	429
14.1	Design Equations	429
14.1.1	Characteristic Impedance and Effective Dielectric Constant	429
14.1.2	Effect of Strip Thickness	431
14.2	Design Considerations	432
14.2.1	Effect of Dispersion	433
14.2.2	Microstrip Losses	433
14.2.3	Quality Factor Q	435
14.2.4	Enclosure Effect	438
14.2.5	Frequency Range of Operation	443
14.2.6	Power-Handling Capability	444
14.3	Coupled Microstrip Lines	456
14.3.1	Even-Mode Capacitance	457
14.3.2	Odd-Mode Capacitance	458
14.3.3	Characteristic Impedances	459
14.3.4	Effective Dielectric Constants	459
14.4	Microstrip Discontinuities	460
14.5	Compensated Microstrip Discontinuities	461
14.5.1	Step-in-Width	461
14.5.2	Chamfered Bend	462
14.5.3	T-Junction	463
	References	465

Appendix	469
About the Author	471
Index	473