

*This Wiley Student Edition is part of a continuing program of paperbound textbooks especially designed for students in developing countries at a reduced price.*


**THIS BOOK IS FOR SALE ONLY IN THE COUNTRY TO WHICH IT IS FIRST CONSIGNED BY WILEY INDIA PVT. LTD. AND SHOULD NOT BE RE-EXPORTED.**

**FOR SALE ONLY IN:**


**INDIA, BANGLADESH, NEPAL, PAKISTAN, SRI LANKA AND BHUTAN**
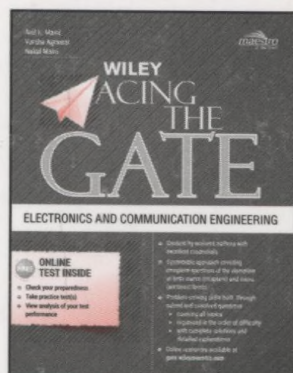
## Wiley Acing the GATE series

A complete solution for all GATE preparation needs



978-81-265-4543-8

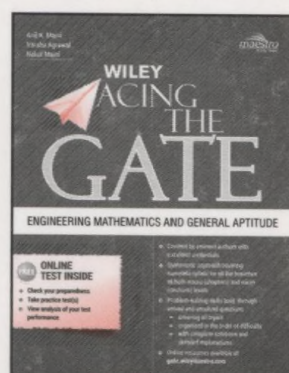

978-81-265-4741-8

- ▶ Systematic and self-explanatory theory
- ▶ Solved examples to build problem-solving skills
- ▶ Solved previous years' GATE questions
- ▶ Strategic tips and exam analysis
- ▶ Graded practice exercises with solutions
- ▶ Complete sets of latest papers solved

**FREE!**

- ✓ Online test with every book
- ✓ Online resources available at [www.gate.wileymaestro.com](http://www.gate.wileymaestro.com)

### Wiley India Pvt. Ltd.

4435-36/7, Ansari Road, Daryaganj  
New Delhi-110 002

Customer Care +91 11 43630000

Fax +91 11 23275895

[csupport@wiley.com](mailto:csupport@wiley.com)

[www.wileyindia.com](http://www.wileyindia.com)

[www.wiley.com](http://www.wiley.com)



ISBN: 978-81-265-4190-4



**WILEY**



**ELECTROMAGNETIC THEORY 1****1.1 Introduction to Microwave Engineering 1**

Applications of Microwave Engineering 2

A Short History of Microwave Engineering 4

**1.2 Maxwell's Equations 6****1.3 Fields in Media and Boundary Conditions 10**

Fields at a General Material Interface 12      Fields at a Dielectric Interface 14

Fields at the Interface with a Perfect Conductor (Electric Wall) 14

The Magnetic Wall Boundary Condition 15      The Radiation Condition 15

**1.4 The Wave Equation and Basic Plane Wave Solutions 15**

The Helmholtz Equation 15      Plane Waves in a Lossless Medium 16

Plane Waves in a General Lossy Medium 17

Plane Waves in a Good Conductor 19

**1.5 General Plane Wave Solutions 20**

Circularly Polarized Plane Waves 24

**1.6 Energy and Power 25**

Power Absorbed by a Good Conductor 27

**1.7 Plane Wave Reflection from a Media Interface 28**

General Medium 28      Lossless Medium 30

Good Conductor 31      Perfect Conductor 32

The Surface Impedance Concept 33

**1.8 Oblique Incidence at a Dielectric Interface 35**

Parallel Polarization 36      Perpendicular Polarization 37

Total Reflection and Surface Waves 38

**1.9 Some Useful Theorems 40**

The Reciprocity Theorem 40

Image Theory 42



**TRANSMISSION LINE THEORY 48**

**2.1 The Lumped-Element Circuit Model for a Transmission Line 48**

Wave Propagation on a Transmission Line 50      The Lossless Line 51

**2.2 Field Analysis of Transmission Lines 51**

Transmission Line Parameters 51  
The Telegrapher Equations Derived from Field Analysis of a Coaxial Line 54  
Propagation Constant, Impedance, and Power Flow for the Lossless Coaxial Line 56

**2.3 The Terminated Lossless Transmission Line 56**

Special Cases of Lossless Terminated Lines 59

**2.4 The Smith Chart 63**

The Combined Impedance–Admittance Smith Chart 67  
The Slotted Line 68

**2.5 The Quarter-Wave Transformer 72**

The Impedance Viewpoint 72      The Multiple-Reflection Viewpoint 74

**2.6 Generator and Load Mismatches 76**

Load Matched to Line 77      Generator Matched to Loaded Line 77  
Conjugate Matching 77

**2.7 Lossy Transmission Lines 78**

The Low-Loss Line 79      The Distortionless Line 80  
The Terminated Lossy Line 81  
The Perturbation Method for Calculating Attenuation 82  
The Wheeler Incremental Inductance Rule 83

**2.8 Transients on Transmission Lines 85**

Reflection of Pulses from a Terminated Transmission Line 86  
Bounce Diagrams for Transient Propagation 87

**TRANSMISSION LINES AND WAVEGUIDES 95**

**3.1 General Solutions for TEM, TE, and TM Waves 96**

TEM Waves 98      TE Waves 100  
TM Waves 100      Attenuation Due to Dielectric Loss 101

**3.2 Parallel Plate Waveguide 102**

TEM Modes 103      TM Modes 104      TE Modes 107

**3.3 Rectangular Waveguide 110**

TE Modes 110      TM Modes 115  
TE<sub>m0</sub> Modes of a Partially Loaded Waveguide 119

**3.4 Circular Waveguide 121**

TE Modes 122      TM Modes 125

**3.5 Coaxial Line 130**

TEM Modes 130      Higher Order Modes 131



<b>3.6 Surface Waves on a Grounded Dielectric Sheet</b>	<b>135</b>
TM Modes	135
TE Modes	137
<b>3.7 Stripline</b>	<b>141</b>
Formulas for Propagation Constant, Characteristic Impedance, and Attenuation	141
An Approximate Electrostatic Solution	144
<b>3.8 Microstrip Line</b>	<b>147</b>
Formulas for Effective Dielectric Constant, Characteristic Impedance, and Attenuation	148
Frequency-Dependent Effects and Higher Order Modes	150
<b>3.9 The Transverse Resonance Technique</b>	<b>153</b>
$TE_{0n}$ Modes of a Partially Loaded Rectangular Waveguide	153
<b>3.10 Wave Velocities and Dispersion</b>	<b>154</b>
Group Velocity	155
<b>3.11 Summary of Transmission Lines and Waveguides</b>	<b>157</b>
Other Types of Lines and Guides	158

## **4 MICROWAVE NETWORK ANALYSIS 165**

<b>4.1 Impedance and Equivalent Voltages and Currents</b>	<b>166</b>
Equivalent Voltages and Currents	166
The Concept of Impedance	170
Even and Odd Properties of $Z(\omega)$ and $\Gamma(\omega)$	173
<b>4.2 Impedance and Admittance Matrices</b>	<b>174</b>
Reciprocal Networks	175
Lossless Networks	177
<b>4.3 The Scattering Matrix</b>	<b>178</b>
Reciprocal Networks and Lossless Networks	181
A Shift in Reference Planes	184
Power Waves and Generalized Scattering Parameters	185
<b>4.4 The Transmission (<math>ABCD</math>) Matrix</b>	<b>188</b>
Relation to Impedance Matrix	191
Equivalent Circuits for Two-Port Networks	191
<b>4.5 Signal Flow Graphs</b>	<b>194</b>
Decomposition of Signal Flow Graphs	195
Application to Thru-Reflect-Line Network Analyzer Calibration	197
<b>4.6 Discontinuities and Modal Analysis</b>	<b>203</b>
Modal Analysis of an $H$ -Plane Step in Rectangular Waveguide	203
<b>4.7 Excitation of Waveguides—Electric and Magnetic Currents</b>	<b>210</b>
Current Sheets That Excite Only One Waveguide Mode	210
Mode Excitation from an Arbitrary Electric or Magnetic Current Source	212
<b>4.8 Excitation of Waveguides—Aperture Coupling</b>	<b>215</b>
Coupling Through an Aperture in a Transverse Waveguide Wall	218
Coupling Through an Aperture in the Broad Wall of a Waveguide	220



**IMPEDANCE MATCHING AND TUNING 228**

- 5.1 Matching with Lumped Elements ( $L$  Networks) 229**
  - Analytic Solutions 230      Smith Chart Solutions 231
- 5.2 Single-Stub Tuning 234**
  - Shunt Stubs 235      Series Stubs 238
- 5.3 Double-Stub Tuning 241**
  - Smith Chart Solution 242      Analytic Solution 245
- 5.4 The Quarter-Wave Transformer 246**
- 5.5 The Theory of Small Reflections 250**
  - Single-Section Transformer 250      Multisection Transformer 251
- 5.6 Binomial Multisection Matching Transformers 252**
- 5.7 Chebyshev Multisection Matching Transformers 256**
  - Chebyshev Polynomials 257      Design of Chebyshev Transformers 258
- 5.8 Tapered Lines 261**
  - Exponential Taper 262      Triangular Taper 263
  - Klopfenstein Taper 264
- 5.9 The Bode–Fano Criterion 266**

**MICROWAVE RESONATORS 272**

- 6.1 Series and Parallel Resonant Circuits 272**
  - Series Resonant Circuit 272      Parallel Resonant Circuit 275
  - Loaded and Unloaded  $Q$  277
- 6.2 Transmission Line Resonators 278**
  - Short-Circuited  $\lambda/2$  Line 278      Short-Circuited  $\lambda/4$  Line 281
  - Open-Circuited  $\lambda/2$  Line 282
- 6.3 Rectangular Waveguide Cavity Resonators 284**
  - Resonant Frequencies 284      Unloaded  $Q$  of the  $TE_{10\ell}$  Mode 286
- 6.4 Circular Waveguide Cavity Resonators 288**
  - Resonant Frequencies 289      Unloaded  $Q$  of the  $TE_{nm\ell}$  Mode 291
- 6.5 Dielectric Resonators 293**
  - Resonant Frequencies of  $TE_{01\delta}$  Mode 294
- 6.6 Excitation of Resonators 297**
  - The Coupling Coefficient and Critical Coupling 298
  - A Gap-Coupled Microstrip Resonator 299
  - An Aperture-Coupled Cavity 302
  - Determining Unloaded  $Q$  from Two-Port Measurements 305
- 6.7 Cavity Perturbations 306**
  - Material Perturbations 306      Shape Perturbations 309



**POWER DIVIDERS AND DIRECTIONAL COUPLERS 317****7.1 Basic Properties of Dividers and Couplers 317**

Three-Port Networks (T-Junctions) 318

Four-Port Networks (Directional Couplers) 320

**7.2 The T-Junction Power Divider 324**

Lossless Divider 324      Resistive Divider 326

**7.3 The Wilkinson Power Divider 328**

Even-Odd Mode Analysis 328

Unequal Power Division and  $N$ -Way Wilkinson Dividers 332**7.4 Waveguide Directional Couplers 333**

Bethe Hole Coupler 334      Design of Multihole Couplers 338

**7.5 The Quadrature ( $90^\circ$ ) Hybrid 343**

Even-Odd Mode Analysis 344

**7.6 Coupled Line Directional Couplers 347**

Coupled Line Theory 347      Design of Coupled Line Couplers 351

Design of Multisection Coupled Line Couplers 356

**7.7 The Lange Coupler 359****7.8 The  $180^\circ$  Hybrid 362**

Even-Odd Mode Analysis of the Ring Hybrid 364

Even-Odd Mode Analysis of the Tapered Coupled Line Hybrid 367

Waveguide Magic-T 371

**7.9 Other Couplers 372****MICROWAVE FILTERS 380****8.1 Periodic Structures 381**

Analysis of Infinite Periodic Structures 382

Terminated Periodic Structures 384

 $k$ - $\beta$  Diagrams and Wave Velocities 385**8.2 Filter Design by the Image Parameter Method 388**

Image Impedances and Transfer Functions for Two-Port Networks 388

Constant- $k$  Filter Sections 390       $m$ -Derived Filter Sections 393

Composite Filters 396

**8.3 Filter Design by the Insertion Loss Method 399**

Characterization by Power Loss Ratio 399

Maximally Flat Low-Pass Filter Prototype 402

Equal-Ripple Low-Pass Filter Prototype 404

Linear Phase Low-Pass Filter Prototypes 406

**8.4 Filter Transformations 408**

Impedance and Frequency Scaling 408

Bandpass and Bandstop Transformations 411



## **8.5 Filter Implementation 415**

Richards' Transformation 416      Kuroda's Identities 416  
Impedance and Admittance Inverters 421

## **8.6 Stepped-Impedance Low-Pass Filters 422**

Approximate Equivalent Circuits for Short Transmission Line Sections 422

## **8.7 Coupled Line Filters 426**

Filter Properties of a Coupled Line Section 426  
Design of Coupled Line Bandpass Filters 430

## **8.8 Filters Using Coupled Resonators 437**

Bandstop and Bandpass Filters Using Quarter-Wave Resonators 437  
Bandpass Filters Using Capacitively Coupled Series Resonators 441  
Bandpass Filters Using Capacitively Coupled Shunt Resonators 443

# **9**

## **THEORY AND DESIGN OF FERRIMAGNETIC COMPONENTS 451**

### **9.1 Basic Properties of Ferrimagnetic Materials 452**

The Permeability Tensor 452      Circularly Polarized Fields 458  
Effect of Loss 460      Demagnetization Factors 462

### **9.2 Plane Wave Propagation in a Ferrite Medium 465**

Propagation in Direction of Bias (Faraday Rotation) 465  
Propagation Transverse to Bias (Birefringence) 469

### **9.3 Propagation in a Ferrite-Loaded Rectangular Waveguide 471**

$TE_{m0}$  Modes of Waveguide with a Single Ferrite Slab 471  
 $TE_{m0}$  Modes of Waveguide with Two Symmetrical Ferrite Slabs 474

### **9.4 Ferrite Isolators 475**

Resonance Isolators 476      The Field Displacement Isolator 479

### **9.5 Ferrite Phase Shifters 482**

Nonreciprocal Latching Phase Shifter 482  
Other Types of Ferrite Phase Shifters 485      The Gyrator 486

### **9.6 Ferrite Circulators 487**

Properties of a Mismatched Circulator 488      Junction Circulator 488

# **10**

## **NOISE AND NONLINEAR DISTORTION 496**

### **10.1 Noise in Microwave Circuits 496**

Dynamic Range and Sources of Noise 497  
Noise Power and Equivalent Noise Temperature 498  
Measurement of Noise Temperature 501

### **10.2 Noise Figure 502**

Definition of Noise Figure 502      Noise Figure of a Cascaded System 504  
Noise Figure of a Passive Two-Port Network 506  
Noise Figure of a Mismatched Lossy Line 508  
Noise Figure of a Mismatched Amplifier 510



- 10.3 Nonlinear Distortion 511**  
 Gain Compression 512      Harmonic and Intermodulation Distortion 513  
 Third-Order Intercept Point 515      Intercept Point of a Cascaded System 516  
 Passive Intermodulation 519
- 10.4 Dynamic Range 519**  
 Linear and Spurious Free Dynamic Range 519

## 11

### ACTIVE RF AND MICROWAVE DEVICES 524

- 11.1 Diodes and Diode Circuits 525**  
 Schottky Diodes and Detectors 525  
 PIN Diodes and Control Circuits 530  
 Varactor Diodes 537      Other Diodes 538      Power Combining 539
- 11.2 Bipolar Junction Transistors 540**  
 Bipolar Junction Transistor 540      Heterojunction Bipolar Transistor 542
- 11.3 Field Effect Transistors 543**  
 Metal Semiconductor Field Effect Transistor 544  
 Metal Oxide Semiconductor Field Effect Transistor 546  
 High Electron Mobility Transistor 546
- 11.4 Microwave Integrated Circuits 547**  
 Hybrid Microwave Integrated Circuits 548  
 Monolithic Microwave Integrated Circuits 548
- 11.5 Microwave Tubes 552**

## 12

### MICROWAVE AMPLIFIER DESIGN 558

- 12.1 Two-Port Power Gains 558**  
 Definitions of Two-Port Power Gains 559  
 Further Discussion of Two-Port Power Gains 562
- 12.2 Stability 564**  
 Stability Circles 564      Tests for Unconditional Stability 567
- 12.3 Single-Stage Transistor Amplifier Design 571**  
 Design for Maximum Gain (Conjugate Matching) 571  
 Constant-Gain Circles and Design for Specified Gain 575  
 Low-Noise Amplifier Design 580      Low-Noise MOSFET Amplifier 582
- 12.4 Broadband Transistor Amplifier Design 585**  
 Balanced Amplifiers 586      Distributed Amplifiers 588  
 Differential Amplifiers 593
- 12.5 Power Amplifiers 596**  
 Characteristics of Power Amplifiers and Amplifier Classes 597  
 Large-Signal Characterization of Transistors 598  
 Design of Class A Power Amplifiers 599



**13.1 RF Oscillators 605**

General Analysis 606      Oscillators Using a Common Emitter BJT 607  
 Oscillators Using a Common Gate FET 609      Practical Considerations 610  
 Crystal Oscillators 612

**13.2 Microwave Oscillators 613**

Transistor Oscillators 615      Dielectric Resonator Oscillators 617

**13.3 Oscillator Phase Noise 622**

Representation of Phase Noise 623  
 Leeson's Model for Oscillator Phase Noise 624

**13.4 Frequency Multipliers 627**

Reactive Diode Multipliers (Manley-Rowe Relations) 628  
 Resistive Diode Multipliers 631      Transistor Multipliers 633

**13.5 Mixers 637**

Mixer Characteristics 637      Single-Ended Diode Mixer 642  
 Single-Ended FET Mixer 643      Balanced Mixer 646  
 Image Reject Mixer 649  
 Differential FET Mixer and Gilbert Cell Mixer 650      Other Mixers 652

**14.1 System Aspects of Antennas 658**

Fields and Power Radiated by an Antenna 660  
 Antenna Pattern Characteristics 662  
 Antenna Gain and Efficiency 664  
 Aperture Efficiency and Effective Area 665  
 Background and Brightness Temperature 666  
 Antenna Noise Temperature and  $G/T$  669

**14.2 Wireless Communications 671**

The Friis Formula 673  
 Link Budget and Link Margin 674  
 Radio Receiver Architectures 676  
 Noise Characterization of a Receiver 679  
 Digital Modulation and Bit Error Rate 681  
 Wireless Communication Systems 684

**14.3 Radar Systems 690**

The Radar Equation 691      Pulse Radar 693      Doppler Radar 694  
 Radar Cross Section 695

**14.4 Radiometer Systems 696**

Theory and Applications of Radiometry 697      Total Power Radiometer 699  
 The Dicke Radiometer 700

**14.5 Microwave Propagation 701**

Atmospheric Effects 701      Ground Effects 703      Plasma Effects 704



## **14.6 Other Applications and Topics 705**

Microwave Heating 705      Power Transfer 705

Biological Effects and Safety 706

---

## **APPENDICES 712**

**A Prefixes 713**

**B Vector Analysis 713**

**C Bessel Functions 715**

**D Other Mathematical Results 718**

**E Physical Constants 718**

**F Conductivities for Some Materials 719**

**G Dielectric Constants and Loss Tangents for Some Materials 719**

**H Properties of Some Microwave Ferrite Materials 720**

**I Standard Rectangular Waveguide Data 720**

**J Standard Coaxial Cable Data 721**

---

## **ANSWERS TO SELECTED PROBLEMS 722**

---

## **INDEX 725**