

# CONTENTS

PREFACE TO THE THIRD EDITION . . . . . v

PREFACE TO THE FIRST EDITION . . . . . vii

## CHAPTER I

MAGNETS AND MAGNETISM . . . . . 9

Discovery of the Property of Magnets—Artificial Magnets—Permanent Magnets—Properties of Magnets—The Earth a Magnet—Poles of a Magnet—Distribution of Magnetic Field—Lines of Force Conventional—Unit Magnetic Pole—How Magnets Attract Pieces of Iron—Why Iron Can Be Magnetized—Theory of Magnetism—How Magnets Are Demagnetized—Electricity and Magnetism—Direction of Magnetic Field about a Conductor—Relation between Direction of Current and Magnetic Field—Determining Direction of Magnetic Field about a Conductor—Magnetic Field around a Number of Conductors—Properties of Electromagnets.

## CHAPTER II

FUNDAMENTALS OF THE ELECTRIC CIRCUIT . . . . . 29

Production of Voltage—Electric Pressure and Temperature—Unit of Electric Current—Electrical Resistance—No Perfect Insulators of Electricity—Pump Analogy of Electric Circuit—Measurement of Pressure—Measurement of Current Flow—How to Increase Voltage—Pump Analogy of Voltage Sources in Series—How Current Is Increased—Pump Analogy of Current Sources in Parallel—Series-parallel and Parallel-series Connections.

## CHAPTER III

OHM'S LAW, SERIES AND PARALLEL CIRCUITS . . . . . 49

Three Electric Units—Unit of Electric Current—Relation between Volts, Amperes and Ohms—How to Remember Ohm's Law—Electric Generator—Factors That Influence Flow of Current—Ohm's Law Problems—What Constitutes Electrical Resistance—Series Circuits—Flow of Electric Cur-

rent Compared to Water Flowing through a Pipe—Voltage Drop along a Circuit Is Similar to Pressure Drop in a Pipe Line—The Value of the Volts across Each Section of Resistance in Any Circuit May Be Found by Ohm's Law—Parallel Circuits—Hydraulic Analogy of a Parallel Circuit—The Total Resistance of Any Circuit Is Equal to the Total Voltage Divided by the Total Current—Joint Resistance of Two or More Unequal Resistances in Parallel—Resistance and Conductance—Formula for Finding Joint Resistance—Two Methods of Working Out Joint Resistance Problems—Volts Drop across a Circuit—Determining Value of Current by Volts Drop and Resistance of Section of a Circuit.

## CHAPTER IV

## ENERGY, WORK AND POWER. . . . . 73

Energy the Ability of Doing Work—Steam under Pressure Possesses Energy—Foot-pound Unit of Work—Defining Unit of Power—Definition of Energy, Work and Power—Horsepower Defined by James Watt—When Energy Is Expended Heat Is Produced—Mechanical Equivalent of Heat—British Thermal Unit—Power of an Electric Circuit—Heat Equivalent of an Electric Current.

## CHAPTER V

## COMPLEX CIRCUITS AND EFFECTS OF INTERNAL RESISTANCE. . . . . 82

Circuits in Which Elements Are Grouped in Series and Parallel—Internal Resistance—How to Compute Value of Current When Effect of Internal Resistance Is Considered—Volts Drop in a Source of Electromotive Force—Volts Drop through Resistance of Armature—Effects of Increasing the Load on Batteries.

## CHAPTER VI

## ELECTRICAL INSTRUMENTS. . . . . 93

Principles on Which Electrical Instruments Are Constructed—Movement for Modern-type Instrument—Instrument Connected as Voltmeter—Turning Effort Proportional to the Current in the Coil—Not Voltage That Causes the Coil to Move, but Current—Instrument Connected to Measure Current—Instrument to Measure Both Volts and Amperes—Direct-reading Wattmeter—Watt-hour Meter.

## CHAPTER VII

## METHODS OF MEASURING RESISTANCE . . . . . 107

Voltmeter-and-ammeter Method—Known-resistance Method—Measuring High Resistance—Measuring Insulation Resist-

ance—The Wheatstone Bridge—Hydraulic Analogy of a Wheatstone Bridge—Condition to Give Balanced Pressure—Measuring Insulation Resistance with a Megohm Meter.

## CHAPTER VIII

## FUNDAMENTAL PRINCIPLES OF DYNAMO-ELECTRIC MACHINERY . . . 119

Electromagnetic Induction—Rule for Determining Direction of Electromotive Force—Lines of Magnetic Force—Unit Electromotive Force—Fundamental Principle of the Electric Motor—Direction Conductor Will Move in a Magnetic Field Depends upon the Direction of the Current—Counter-electromotive Force—How an Electric Generator Is Loaded—Simplest Form of Electric Machine—Factors Governing Value of the Voltage—Current Reverses in External Circuit—Electromotive Force or Current Curve—Machine with Ring-type Armature.

## CHAPTER IX

## DIRECT-CURRENT MACHINERY CONSTRUCTION . . . . . 138

Types of Armatures—Objections to Ring-type Armatures—Drum-type Armatures—Effects of Eddy Currents—Eliminating Eddy Currents—Objection to Smooth-core Armatures—Field Magnets—Early Types of Field Magnets—Consequent-pole Type Machine—Materials Used in Field Poles—Function of the Commutator—Commutator Construction.

## CHAPTER X

## INDUCTANCE AND COMMUTATION . . . . . 156

Magnetic Field about a Conductor—How Voltage Is Induced in a Conductor—Voltage Induced by Decreasing Current—Mutual Inductance—Self-inductance—Neutral Point on Commutator—How Voltage in Armature Is Maintained Constant—Effects of Self-induction on Commutation—Commutation Period Short.

## CHAPTER XI

## TYPES OF DIRECT-CURRENT GENERATORS . . . . . 168

Exciting Field Coils of Direct-current Generators—Residual Magnetism—How Voltage Is Built up in the Armature—Lines of Force in Field Poles Does Not Increase in Proportion to the Current Flowing in the Field Coils—Field-coil Connections and Armature Rotation—Reversing Rotation of Armature—Series-connected Generator—Ampere-turns on Field Poles—Load on a Series Generator—Voltage Control on Shunt Generator—Diagrams of Direct-current Generators—Effects of Loading a

Shunt Generator on Voltage Regulation—How Voltage May Be Maintained Constant—Compound-wound Generator—Crossing Field Connections of Compound-wound Generator.

#### CHAPTER XII

#### DIRECT-CURRENT GENERATOR CHARACTERISTICS . . . . . 189

Voltage Curves of Shunt Generator—Volts Drop in Armature with Fields Separately Excited—Voltage Curve of Series Generator—External Characteristic Curves—Voltage Curve of Compound Generator—Series Winding to Compensate for Volts Drop in Armature—Voltage at Terminals of Compound Generator—Proper Amount of Compounding—Compounding Shunt—Short-shunt and Long-shunt Connections.

#### CHAPTER XIII

#### LOSSES IN DIRECT-CURRENT MACHINERY . . . . . 201

Loss in Transformation of Energy—Friction Losses—Current to Excite the Field Coils—Copper Losses in the Armature—Eddy-current Losses—Hysteresis Losses—Total Losses in an Electric Machine.

#### CHAPTER XIV

#### DIRECT-CURRENT MOTORS . . . . . 208

Fundamental Principle of Electric Motor—Effects of Changing Brush Position—Another Theory of Motor Operation—Both Motor and Generator Action Present in all Dynamo-electric Machines—Counter-electromotive Force—How Motor Operates When Loaded—How Speed of Motor May Be Adjusted.

#### CHAPTER XV

#### TYPES OF DIRECT-CURRENT MOTORS . . . . . 219

Five Types of Motors—Torque of Series Motor Varies as the Square of the Current—Shunt-type Motors—Torque of Shunt Motor Varies as the Armature Current—Compound-type Motors—Effects of Armature Reaction—Commutating-pole Machines—Number of Interpoles Used—Motors with Compensating Windings.

#### CHAPTER XVI

#### LOCATING POSITION OF BRUSHES ON COMMUTATOR . . . . . 233

Brush Position—Locating the Neutral—Armature-speed Method—Induced-voltage Method—Millivoltmeter Method—Adjusting the Interpoles.

## CHAPTER XVII

## THREE-WIRE SYSTEMS AND HOW THEY MAY BE OBTAINED . . . . . 241

Voltages for Direct-current Circuits—Three-wire System—Balancer Sets for Three-wire Systems—How Balancer Set Maintains Three-wire Systems Voltage Balanced—Compound-wound Balancer Sets—Three-wire Generators.

## CHAPTER XVIII

## DIRECT-CURRENT GENERATORS IN PARALLEL . . . . . 254

Reasons for Operating Generators in Parallel—Effects of Generator Characteristics on Parallel Operation—Compound Generators in Parallel—Equalizer Connection—Putting Generators into Service—Parallel Operation of Three-wire Generators.

## CHAPTER XIX

## FUNDAMENTAL PRINCIPLES OF ALTERNATING CURRENT . . . . . 268

Dynamo-electric Machines Fundamentally Generate Alternating Current—Distance Traveled and Rate of Motion—Principles of the Dynamo-electric Machines—Alternating Electromotive Force—Electrical Degrees—A Number of Conductors Connected in Series Generating Voltage—Relation between Cycles, Poles and Speed.

## CHAPTER XX

## MEASUREMENT AND ADDITION OF ALTERNATING VOLTAGES AND CURRENT . . . . . 283

Instruments for Alternating-current Circuits—Voltmeter and Ammeter Readings—Addition of Voltages and Currents.

## CHAPTER XXI

## TWO-PHASE AND THREE-PHASE CIRCUITS . . . . . 294

Two-phase Systems—Three-wire Two-phase Systems—Three-phase Systems—Three-phase Machine with Ring Armature—Delta and Star Connections.

## CHAPTER XXII

## OPERATING ALTERNATORS IN PARALLEL. . . . . 311

Condition for Parallel Operation—Adjusting Load on Two or More Alternators—Putting an Alternator into Service—Other Methods of Synchronizing—Electrodynamometer Type of Synchronoscope—Synchronoscope Connections.

## CHAPTER XXIII

## KILOWATTS, KILOVOLT-AMPERES AND POWER FACTOR. . . . . 324

How Current Builds Up in a Direct-current Circuit—Lenz's Law—Current Lags behind Voltage—Pump Analogy of Alternating Current—Apparent Watts and Useful Watts—A Wattmeter Reads True Watts—Power in an alternating-current Circuit—Effects of Capacity—Power of Polyphase Circuits.

## CHAPTER XXIV

## TRANSFORMERS . . . . . 337

The Alternating-current System—Transformer Efficiency—Types of Transformers—Types of Cores—Iron Losses and Copper Losses—Core Construction—Primary and Secondary Windings—Ratio of Primary to Secondary Volts—Relation between Primary and Secondary Currents—Rating of Transformers—Primary- and Secondary-winding Connections.

## CHAPTER XXV

## ALTERNATING-CURRENT MOTORS. . . . . 356

Squirrel-cage Type—Magnetic Field in Induction-motor Stator—Rotating Magnetic Field—Motor Speed—Direction of Rotation—Slip of an Induction Motor—How Torque Is Produced—Induction-generator Operation—Rotor Construction—Starting Torque vs. Rotor-winding Resistance—Connecting Rotor Bars to End Rings—Rotor-bar Insulation—Brazen Rotor Bars to Rings—Types of Squirrel-cage Motors—Wound-rotor Motors—Synchronous Motors—Fynn-Weichsel Motors—Commutator-type Polyphase Motors—Single-phase Motors.

## CHAPTER XXVI

## STARTING ALTERNATING-CURRENT MOTORS . . . . . 381

Full-voltage Starting—Reduced-voltage Starting—How Auto-transformers Operate—Comparison of Auto-transformer and Resistance Starting—Wound-rotor Motors—Synchronous Motors—Speed Adjustment—Reverse Direction of Rotation.

## CHAPTER XXVII

## ELECTRONS AND ELECTRON TUBES . . . . . 392

Elements—Electrons and Protons—Electric Current—Electron Flow—Electron Velocity—Electron Emission—Thermionic Emission—Electron-tube Filaments—Anodes and Grids—Two-element Tubes—Space Charge—High-vacuum and Gas-

filled Tubes—Control Grid—Tetrodes and Pentodes—Photoelectric Tubes—Photoelectric-tube Circuits.

CHAPTER XXVIII

ELECTRONIC RECTIFIERS . . . . . 415  
 Half-wave Rectification—Full-wave Rectification—Dual-element Tubes—Charging Storage Batteries—Thyratrons—Grid-voltage Control—Mercury-arc Rectifiers—Single-anode Rectifiers.

CHAPTER XXIX

D-C-MOTOR SPEED CONTROL. . . . . 428  
 Motor Controller Operation—Potential on Thyratrons—Armature Circuit—Stopping and Jogging—Speed Control by Thyratrons—Pushbutton Station—Forward Armature Direction—Reverse Armature Direction.

CHAPTER XXX

FLAME-FAILURE PROTECTION AND SMOKE-DENSITY INDICATORS. . . 435  
 Flame-detector—Detector Operation—Starting the Flame—Flame Failure—Flame Electrode—Ignition-coil Circuit—Main Gas-valve Circuit—Grounded Electrode—Smoke-density Indicators—Haze-indicator Operation—Dense-smoke Operation—Light-haze Operation—Thyratron Replaces Relays—Adjusting the Indicator—Indicator Circuits—Stack Haze Too Dense—Indicators with Two Thyratrons.

INDEX . . . . . 449